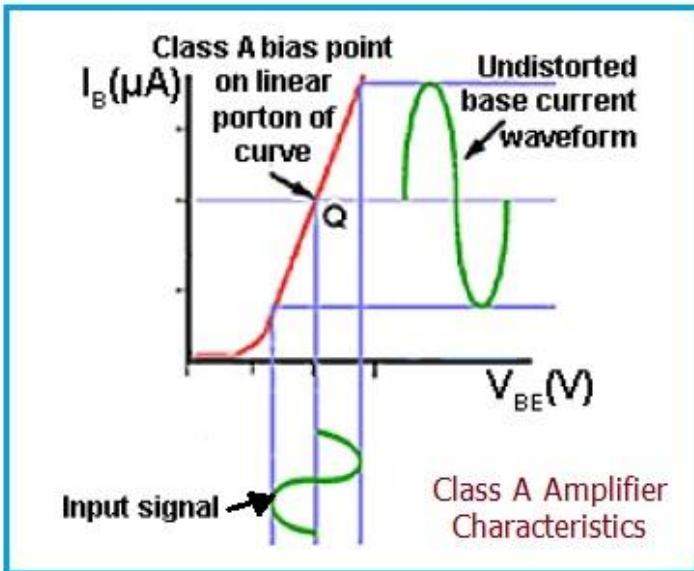


Class A Amplifier



The main role of class-A bias is to keep amplifier free from distortion by keeping signal waveform out of the non-linear region which exists between 0V and 0.6V. The figure-1 depicts class A amplifier bias characteristics.

Amplifier class-A operation

- In this **class-A**, amplifier operates in active region at all the times($2*\pi$).
- Stage efficiency = $P_{L(max)}/ P_S \times 100 \%$

Where P_S is DC input power.

- Load Power = $P_L = (V_L)^2 / R_L = (V_{PP})^2 / 8 * R_L$

Amplifier class-B operation


- In this **class-B**, current flows for half of the input cycle(π).
- Q point is located at cutoff the DC and AC load lines.

$$V_{CEQ} = V_{CC}/2$$

- AC load power of class-B push pull amplifier,

$$P_L = (V_{PP})^2/8 * R_L$$

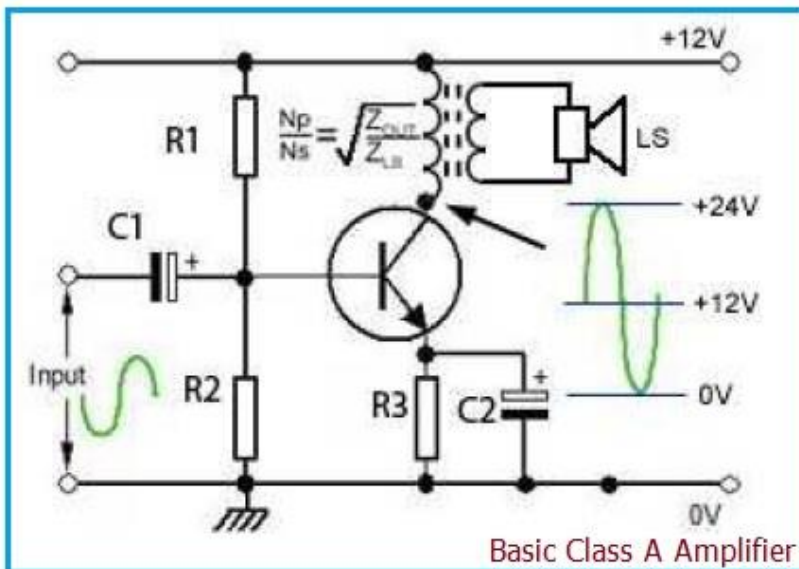
- Class A is used for low to medium power output stages.
- It is less used for high power output stages.
- It has poor efficiency compare to class B.
- They produce output power of 50% (theoretical) and about 25 to 30% (practical)



The figure-2 depicts basic class A Power amplifier. The efficiency of class-A PA is improved by placing output transformer instead of resistor as its load.

With no signal, the quiescent collector current of output transistor is about 50mA. When a signal is applied, the collector current will vary significantly above and below this specified level.


Class B Amplifier

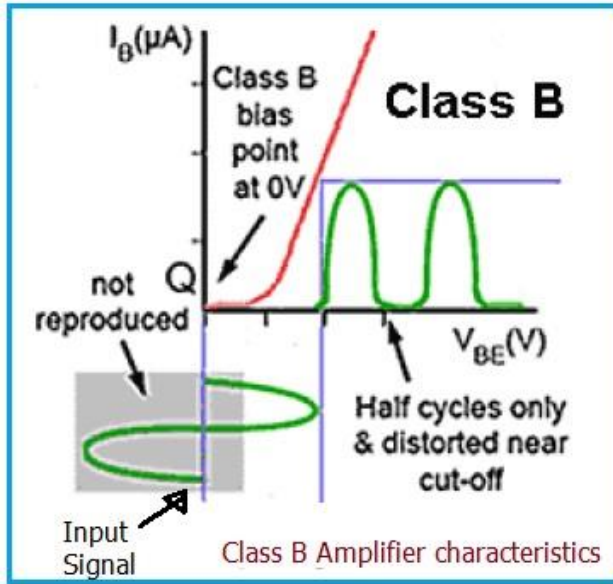

The figure-3 depicts class B amplifier bias characteristics.

- The transistor in the circuit conducts for only half of each cycle of signal waveform as there is no standing bias current (i.e. I_q is zero). Hence efficiency is increased significantly compare to class A PA.
- Efficiency of 80% is possible theoretically with this bias and about 50% to 60% are possible practically.
- It has better efficiency compare to class A.

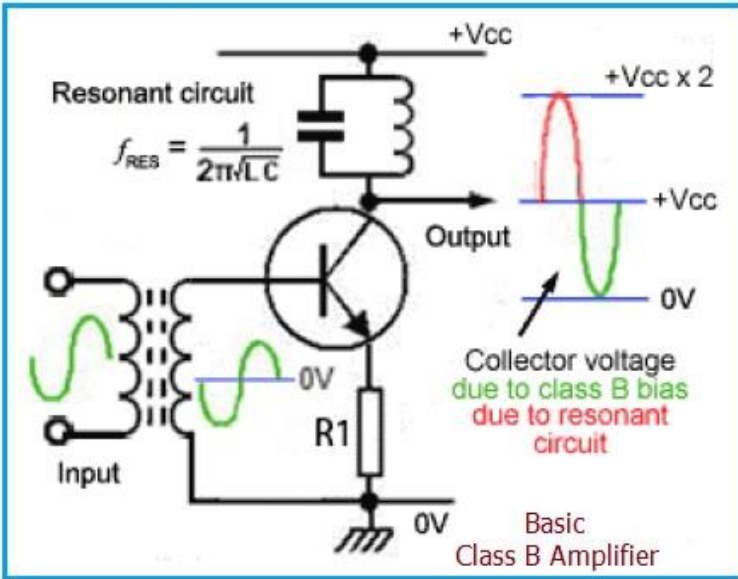Though the efficiency is higher, the downside is transistor amplifies only half of the waveform which produces severe distortion. To overcome this distortion, audio amplifiers use a push-pull circuit.



The figure-4 depicts basic class B power amplifier. In push-pull outout configuration, two identical but anti-phase signals from phase splitter are provided to bases of pair of transistors. Here each transistor feeds current to load for half cycle only. Later the two half cycles are re-combined via centre tapped transformer. This will produce complete sine wave in the secondary coil.