

(5) UG-2D (Hastley 05/11) vhr 5.04

Applying Thevenin's theorem at the terminals X, Y in Fig (2) and looking from terminals left, the current source  $h_e I_1$  in parallel with its resistance  $1/h_{oe}$  can be replaced by an equivalent Thevenin voltage source of generated voltage ( $h_e I_1 / h_{oe}$ ) and internal resistance  $1/h_{oe}$ . The Thevenin representation is shown in fig (3).

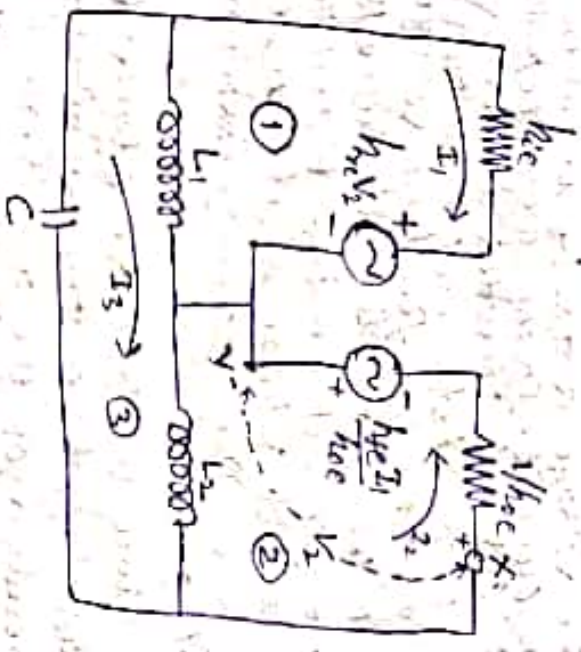


Fig (3)

For simplicity, the mutual inductance between  $L_1$  and  $L_2$  is neglected.

UG-22 (Hastley 05/11) vhr 5.04

From fig (3), we find that, the voltage across  $S_1, h_e I_1 = \frac{1}{h_{oe}} I_2 - \frac{h_e I_1}{h_{oe}} I_1$  (1)  
 Applying KVL in the voltage loop equations for loop (1), (2) and (3), we have three equations.  
 For loop-1, we obtain

$$(h_e + jX_{L1}) I_1 + h_e I_2 - jX_{L1} I_3 = 0$$

$$\text{or, } (h_e + jX_{L1}) I_1 + h_e \left( \frac{1}{h_{oe}} I_2 - \frac{h_e I_1}{h_{oe}} I_1 \right) - jX_{L1} I_3 = 0$$

[From (1)]

$$\text{or, } (h_e + jX_{L1}) I_1 - \frac{h_e h_e I_1}{h_{oe}} I_1 + \frac{h_e I_2}{h_{oe}} - jX_{L1} I_3 = 0 \quad \text{--- (2)}$$

For loop (2),

$$-\frac{h_e I_1}{h_{oe}} + \left( \frac{1}{h_{oe}} + jX_{L2} \right) I_2 + jX_{L2} I_3 = 0 \quad \text{--- (3)}$$

And for loop- (3),

$$-jX_{L1} I_1 + jX_{L2} I_2 + (jX_{L1} + jX_{L2} - jX_C) I_3 = 0 \quad \text{--- (4)}$$

where  $X_{L1} = \omega L_1, X_{L2} = \omega L_2$  and  $X_C = \frac{1}{\omega C}$  where  $\omega =$  angular frequency of oscillation.

The currents  $I_1, I_2$  and  $I_3$  are non-zero (non-trivial solution of equations (2), (3) and (4) exist if the determinant of Coefficients of  $I_1, I_2, I_3$  is zero.



Q6-III (partly solved)

that is

$$\begin{vmatrix} (h_{ie} + jX_{L1} - \frac{h_{fe} h_{re}}{h_{oe}}) & (\frac{h_{re}}{h_{oe}}) & (-jX_{L1}) \\ (-\frac{h_{fe}}{h_{oe}}) & (\frac{1}{h_{oe}} + jX_{L2}) & (jX_{L2}) \\ (-jX_{L1}) & (jX_{L2}) & (jX_{L1} + jX_{L2} - jX_C) \end{vmatrix} = 0 \quad (5)$$

At the frequency of oscillations it can be assumed that

$$jX_{L1} + jX_{L2} - jX_C = 0 \quad (6)$$

$$\left( h_{ie} + jX_{L1} - \frac{h_{fe} h_{re}}{h_{oe}} \right) \left[ \left( \frac{1}{h_{oe}} + jX_{L2} \right) (jX_{L1} + jX_{L2} - jX_C) + X_{L1}^2 \right]$$

$$+ \frac{h_{fe}}{h_{oe}} \left[ \frac{h_{fe}}{h_{oe}} (jX_{L1} + jX_{L2} - jX_C) + X_{L1} X_{L2} \right]$$

$$- \frac{h_{fe}}{h_{oe}} X_{L1} X_{L2} + \left( \frac{1}{h_{oe}} + jX_{L2} \right) X_{L1}^2 = 0 \quad (7)$$

on solving equation (7), we have

$$\left[ \frac{h_{ie}}{h_{oe}} - \frac{h_{fe} h_{re}}{h_{oe}^2} - X_{L1} X_{L2} \right] + j \left[ \frac{1}{h_{oe}} X_{L1} + h_{re} X_{L2} - \frac{h_{fe} h_{re} X_{L1}}{h_{oe}} \right]$$

$$\times (jX_{L1} + jX_{L2} - jX_C) + h_{ie} X_{L2}^2 + jX_{L1} X_{L2}^2 - \frac{h_{fe} h_{re} X_{L2}^2}{h_{oe}}$$

$$+ \frac{h_{fe} h_{re}}{h_{oe}^2} (jX_{L1} + jX_{L2} - jX_C) + \frac{h_{fe}}{h_{oe}} X_{L1} X_{L2}$$

$$- \frac{h_{fe}}{h_{oe}} X_{L1} X_{L2} + \frac{1}{h_{oe}} X_{L1}^2 + jX_{L2} X_{L1}^2 = 0$$

(8)

Q6-III (partly solved)

Equating real part of eqn (8) to zero and using equation (6), we have

$$h_{ie} X_{L2}^2 - \frac{h_{fe} h_{re}}{h_{oe}} X_{L2}^2 + \frac{h_{fe}}{h_{oe}} X_{L1} X_{L2} - \frac{h_{fe}}{h_{oe}} X_{L1} X_{L2}$$

$$+ \frac{1}{h_{oe}} X_{L1}^2 = 0$$

$$\Rightarrow \frac{(h_{ie} h_{oe} - h_{fe} h_{re})}{h_{oe}} X_{L2}^2 + \left( \frac{h_{fe} - h_{fe}}{h_{oe}} \right) X_{L1} X_{L2} + \frac{1}{h_{oe}} X_{L1}^2 = 0$$

$$\Rightarrow (h_{ie} h_{oe} - h_{fe} h_{re}) X_{L2}^2 + (h_{re} - h_{fe}) X_{L1} X_{L2} + X_{L1}^2 = 0$$

$$\Rightarrow \Delta_{ne} X_{L2}^2 + (h_{re} - h_{fe}) X_{L1} X_{L2} + X_{L1}^2 = 0$$

where  $\Delta_{ne} = h_{ie} h_{oe} - h_{fe} h_{re}$ . Since  $h_{re} \ll h_{fe}$ , we have

$$\Delta_{ne} X_{L2}^2 - h_{fe} X_{L1} X_{L2} + X_{L1}^2 = 0$$

This is quadratic in  $X_{L2}$ . Therefore,

$$X_{L2} = \left[ \frac{h_{fe} \pm \sqrt{h_{fe}^2 - 4 \Delta_{ne}}}{2 \Delta_{ne}} \right] X_{L1}$$

Again,  $4 \Delta_{ne} \ll h_{fe}^2$ , therefore,

$$X_{L2} = \frac{h_{fe}}{\Delta_{ne}} X_{L1}$$

$$\Rightarrow \omega_{L2} = \frac{h_{fe}}{\Delta_{ne}} \omega_{L1}$$

(7)  
UG-11 (Hartley Osc)

$$\text{or } L_2 = \frac{h_{fe}}{\Delta h_{fe}} L_1 \rightarrow (9)$$

This is the required condition for sustained oscillation.

### FREQUENCY OF OSCILLATOR

Equating imaginary part of eq<sup>n</sup> (8) to zero we have,

$$\frac{h_{fe}}{h_{oe}} (X_{L1} + X_{L2} - X_C) - \frac{h_{fe} h_{re}}{h_{oe}} (X_{L1} + X_{L2} - X_C) - X_{L1} X_{L2} (X_{L1} + X_{L2} - X_C) + X_{L1} X_{L2}^2 + \frac{h_{fe} h_{re}}{h_{oe}} (X_{L1} + X_{L2} - X_C) + X_{L2} X_{L1}^2 = 0$$

$$\text{or, } \frac{h_{fe}}{h_{oe}} (X_{L1} + X_{L2} - X_C) + X_{L1} X_{L2} X_C = 0$$

$$\text{or, } (X_{L1} + X_{L2} - X_C) + \frac{h_{oe}}{h_{fe}} X_{L1} X_{L2} X_C = 0$$

$$\text{or, } (\omega L_1 + \omega L_2 - \frac{1}{\omega C}) + \frac{h_{oe}}{h_{fe}} \cdot \omega^2 L_1 L_2 \cdot \frac{1}{\omega C} = 0$$

$$\text{or, } (L_1 + L_2 - \frac{1}{\omega^2 C}) + \frac{h_{oe}}{h_{fe}} \frac{L_1 L_2}{C} = 0$$

$$\text{or, } \frac{1}{\omega^2 C} = (L_1 + L_2) + \frac{h_{oe}}{h_{fe}} \frac{L_1 L_2}{C}$$

$$\text{or, } \frac{1}{\omega^2} = (L_1 + L_2) C + \frac{h_{oe}}{h_{fe}} L_1 L_2$$

(8)  
UG-11 (Hartley Osc)

$$\omega^2 = \frac{1}{\frac{h_{oe}}{h_{fe}} L_1 L_2 + (L_1 + L_2) C}$$

$$\therefore \omega = \frac{1}{\sqrt{\frac{h_{oe}}{h_{fe}} L_1 L_2 + (L_1 + L_2) C}}$$

$$\text{or, } f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \frac{1}{\sqrt{\frac{h_{oe}}{h_{fe}} L_1 L_2 + (L_1 + L_2) C}} \rightarrow (10)$$

In actual circuit,  $\frac{h_{oe}}{h_{fe}} L_1 L_2 \ll (L_1 + L_2) C$ .

$$\therefore f = \frac{1}{2\pi \sqrt{(L_1 + L_2) C}} = \frac{1}{2\pi \sqrt{LC}} \rightarrow (11)$$

where  $L = L_1 + L_2$  is the total inductance of the tank circuit. In deriving eq<sup>n</sup> (11), we have neglected the mutual inductance  $M$  of the coil  $L_1$  and  $L_2$ . If  $M$  is also taken into consideration the expression for frequency is obtained by replacing  $L_1$  by  $L_1 + M$  and  $L_2$  by  $L_2 + M$ . If this is done the frequency becomes

$$f = \frac{1}{2\pi \sqrt{(L_1 + L_2 + 2M) C}} \rightarrow (12)$$

Thus the frequency of the Hartley oscillator can be varied by changing  $L$  or  $C$ . This oscillator is a radio frequency generator and is usually used in radio receivers.