

TOPIC: - Rectification (Half Wave)

V.G. III

Rectification is the process by which an alternating current or voltage is converted into a direct current or voltage. Any electrical device, offering a low resistance to the current in one direction and a high resistance to the current in the opposite direction is called a "rectifier".

The vacuum diode and p-n junction diodes are commonly used as rectifiers. Here we will discuss the p-n junction diode rectifiers. There are two types of rectification; half wave rectification and full wave rectification, depending upon the period of conduction.

Half Wave Rectifier

A rectifier in which current conducts only during positive half cycle of input a.c. signal but not for negative half cycle, is called "half wave rectifier".

A half wave rectifier circuit is shown in fig (V). A transformer is used at the input to step up or step down the ac mains voltage connected to the primary. Here an a.c. signal $e = E_m \sin \omega t$ is applied across a circuit consisting of a p-n junction diode with load resistance R_L . Since diode has an unidirectional properties, it conducts only during positive half cycle of input a.c. signal, but not during ~~half cycle~~ negative half cycle.

(2)

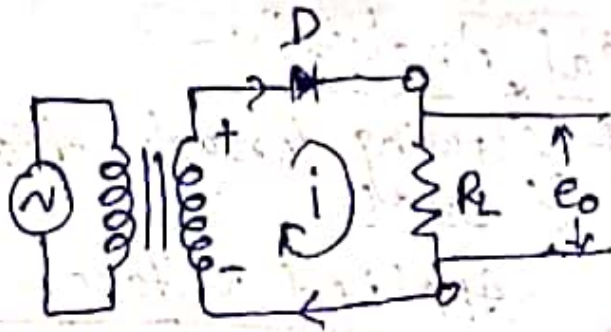


Fig (1)

The shape of the current through R_L consists of half sinusoidal wave is shown in fig (2).

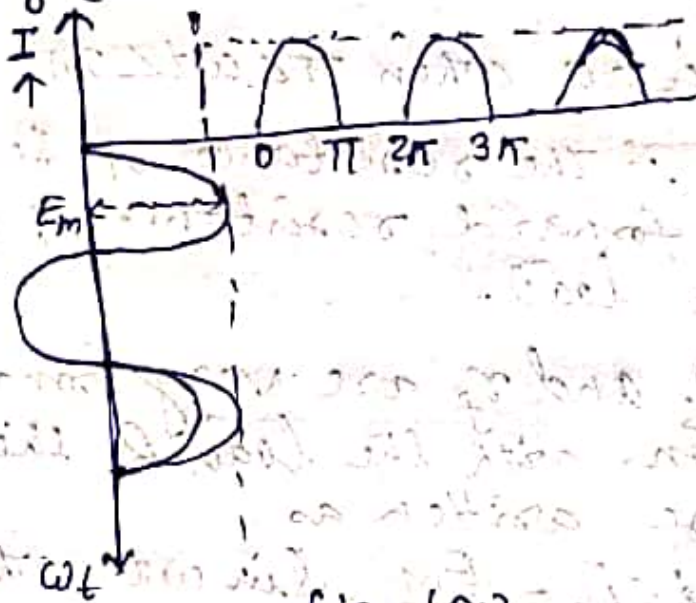


fig (2)

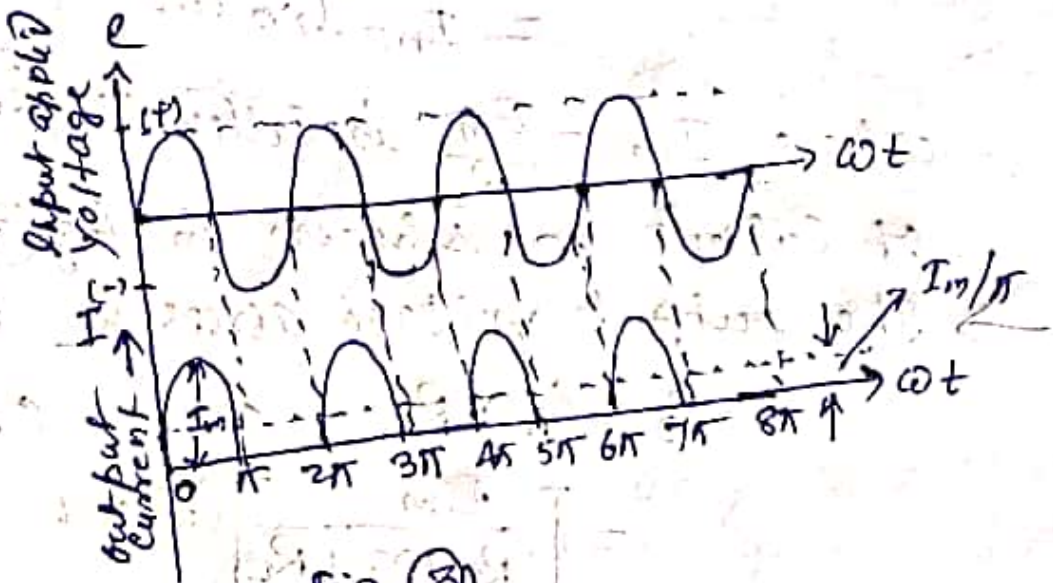


Fig (3)

(3)

Mathematical Analysis:-
The current flowing through diode during positive half cycle.

Applied voltage
 $i = i_b = \frac{E_m \sin \omega t}{R_s + r_f + R_L}$ when $0 < \omega t < \pi$

when $0 < \omega t < \pi$ → (1)
 $i = \frac{E_m \sin \omega t}{R_s + r_f + R_L}$ → (1)

and $i_b = 0$ when $\pi < \omega t < 2\pi$ → (2)

Here R_s is the resistance of secondary coil; r_f the forward resistance of diode and R_L the load.

If R_s and r_f are very small in comparison with the load R_L then eq (2) can be written as

$i = i_b = \frac{E_m}{R_L} \sin \omega t$ when $0 < \omega t < \pi$
 $= I_m \sin \omega t$ → (3)

where $I_m = \frac{E_m}{R_L}$ is called the peak value of current as shown in fig (3)

→ The output voltage across R_L is given by

$E_o = i_b \times R_L$ when $0 < \omega t < \pi$
 $= \left[\frac{E_m}{R_s + r_f + R_L} \right] \sin \omega t$ → (4)
 $= (I_m R_L) \sin \omega t$ → (5)

(4)

→ The d.c. or average current I_{dc} is given by

$I_{dc} = \frac{1}{2\pi} \left[\int_0^\pi i_b dt + \int_\pi^{2\pi} i_b dt \right]$ → (5)

The second term in the bracket is zero since there is no conduction during negative half or π to 2π interval of input. C_o

$I_{dc} = \frac{1}{2\pi} \int_0^\pi i_b dt$ → (6)

Substituting for i from eq (3), we have

$I_{dc} = \frac{1}{2\pi} \int_0^\pi \frac{E_m}{R_L} \sin \omega t dt$
 $= \frac{(-1) E_m}{2\pi R_L} [\cos \omega t]_0^\pi$

$= \frac{E_m}{\pi R_L} = \frac{I_m}{\pi}$ → (7)

This current has been shown as a dashed straight-line in fig (3).

→ The effective value or the current in the load (output) is the R.M.S value of current and is given by

$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 dt}$
 $= \sqrt{\frac{1}{2\pi} \left[\int_0^\pi i^2 dt + \int_\pi^{2\pi} i^2 dt \right]}$

Substituting for i and noting that there is no conduction for the interval π to 2π i.e. second term is zero, we have

$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^\pi i^2 dt} = \sqrt{\frac{1}{2\pi} \int_0^\pi I_m^2 \sin^2 \omega t dt}$
 $= \frac{I_m}{\sqrt{2}}$ → (8)

(5)

→ Efficiency of Rectifier:—

The efficiency of rectifier is defined as the ratio of the d.c. output power to the a.c. input power.

$$\text{i.e. } \eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{dc}^2 R_L}{(I_{rms})^2 (r_f + R_L)}$$

$$= \frac{(I_m/\pi)^2 R_L}{(I_m/2)^2 (r_f + R_L)} = \frac{4}{\pi^2} \left[\frac{1}{\frac{r_f}{R_L} + 1} \right]$$

$$\approx \frac{4}{\pi^2} = 0.406 \quad \text{as } r_f \ll R_L$$

Thus the maximum efficiency of a half wave rectifier is 40.6% i.e. under this condition only 40.6% of input a.c. input power is converted into d.c. power in load.

→ Ripple factor

The output of the rectifier is composed of both a.c. & d.c. power so the ratio of effective or r.m.s value of a.c. component to d.c. component is called ripple factor.

$$\text{i.e. } r = \frac{\text{effective or r.m.s value of a.c. compo.}}{\text{d.c. component}}$$

$$= \frac{(I_r)_{rms}}{I_{dc}}$$

$$\text{Also, } I_{rms}^2 = I_{dc}^2 + (I_r)_{rms}^2 \quad \therefore (I_r)_{rms}^2 = I_{rms}^2 - I_{dc}^2$$

$$\therefore r = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}} = \sqrt{\frac{I_{rms}}{I_{dc}} - 1} = \sqrt{\eta - 1}$$

$$= \sqrt{\frac{\pi^2}{4} - 1} = 1.21$$

This indicates that the amount of a.c. voltage present in the output is 121% of the d.c. voltage.