

# (1) ASTABLE MULTIVIBRATOR

Astable multivibrator has two states which remain momentarily stable and is also known as "free running multivibrator". An operational amplifier can be used as an astable multivibrator as shown in fig (1)

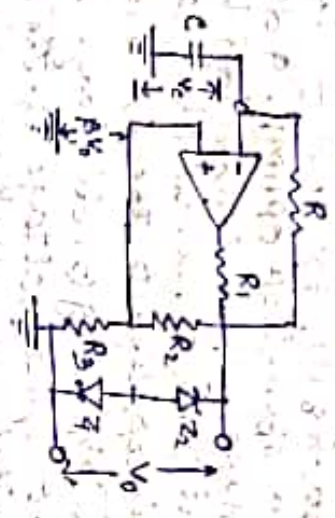


Fig (1)

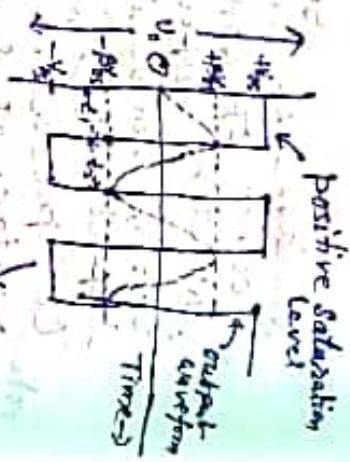


Fig (2)

This circuit switches respectively between two states. The OP-AMP operates both positive and negative feedback and contains a timing capacitor, at its inverting input terminals. The output voltage  $V_0$  is limited by the break down voltage  $+V_{os}$  and  $-V_{os}$  of the two zener diodes  $Z_1$  &  $Z_2$ . Connected back to back across the output terminal of the OP-AMP. Thus  $V_0$  will be either  $+V_{os}$  or  $-V_{os}$ . A fraction of  $V_0$  i.e.  $\beta = \frac{R_2 + R_3}{R_2 + R_3}$  is feedback to the non-inverting input. Thus in one state the amplifiers output reaches a positive saturation level

(2)

$V_0 = +V_{os}$  (diode  $Z_2$ ) and in the other state the amplifier output reaches a negative saturation level  $V_0 = -V_{os}$  (diode  $Z_1$ ). The output waveform is thus a square wave as shown in fig (2).

Expression for Frequency of the

Oscillation:

The input voltage  $V_i$  to the amplifier is  $V_i = V_0 - \beta V_0$

when  $V_i < 0$  i.e.  $V_0 < \beta V_0$  or  $V_0 < \beta(+V_{os})$

or,  $V_0 < \beta V_{os}$  and therefore the capacitor charges exponentially towards  $+V_{os}$  through a time constant  $R_1 C$ . The output remains constant at  $+V_{os}$  until  $V_0 = +\beta V_{os}$  so that

$V_0 = V_0 - \beta V_{os} = 0$  i.e. the potential difference between the two input terminals approaches zero, and the amplifier output reverses to  $-V_{os}$ .

Note:  $C$  changes exponentially towards  $-V_{os}$ . Then


$$V_0 - V_0 = V_0 - \beta V_0 = V_0 + \beta V_{os} \quad \text{--- (3)}$$

The output  $V_0$  remains constant

until  $V_0 = -\beta V_{os}$  at which  $V_i = 0$

and the reversal of state takes place.

The waveforms are shown in fig (2)

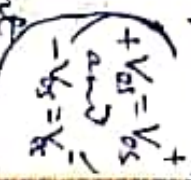



(3)

charging of capacitor starts from an initial voltage  $\beta V_{os}^-$ . This continues upto a voltage level  $\beta V_{os}^+$ . If we charging could have continued it would have reached a fixed level of  $V_{os}^+$ , but as the charging terminates at  $\beta V_{os}^+$ , the charging period,  $t_1$ , is given by

$$t_1 = RC \log \frac{V_{os}^+ - \beta V_{os}^-}{V_{os}^+ - \beta V_{os}^+}$$

$$= RC \log \frac{V_{os}^+ - \beta V_{os}^-}{V_{os}^+ (1 - \beta)} \quad \text{--- (3)}$$

The second charging time from  $\beta V_{os}^+$  to  $-\beta V_{os}^-$  will be

$$t_2 = RC \log \frac{V_{os}^- - \beta V_{os}^+}{V_{os}^- (1 - \beta)} \quad \text{--- (4)}$$

If  $V_{os}^+ = V$  and  $V_{os}^- = -V$  then  $t_1 = t_2$ . So that the period of an oscillation or time period is

$$T = t_1 + t_2 = RC \log \frac{V + \beta V}{V(1 - \beta)} + RC \log \frac{-V - \beta V}{-V(1 - \beta)}$$

$$= RC \log \frac{(1 + \beta)}{(1 - \beta)} + RC \log \frac{(1 + \beta)}{(1 - \beta)}$$

$$(4) = RC \log \left\{ \left( \frac{1 + \beta}{1 - \beta} \right) \cdot \left( \frac{1 + \beta}{1 - \beta} \right) \right\}$$

$$= RC \log \left( \frac{1 + \beta}{1 - \beta} \right)^2$$

$$= 2 RC \log \left( \frac{1 + \beta}{1 - \beta} \right) \quad \text{--- (5)}$$

$$= 2 RC \log \left( \frac{R_2 + 2R_3}{R_2} \right)$$

$$= 2 RC \log \left( 1 + \frac{2R_3}{R_2} \right)$$

This is the expression for time period of the oscillation. Now frequency of the oscillation is given by

$$f = \frac{1}{T} = \frac{1}{2 RC \log \left( 1 + \frac{2R_3}{R_2} \right)} \quad \text{--- (6)}$$

$$\text{If } \frac{2R_3}{R_2} \ll 1 \therefore f = \frac{1}{2RC} \quad \text{--- (7)}$$

From eqn (5), we conclude that time period is independent of saturation level  $V_{os}^+$  and  $V_{os}^-$  and depends only on time constant  $RC$  and feedback factor  $\beta$ .

Use: — As stable multivibrator is very useful for fixed frequency oscillation in audio frequency range (100 Hz - 10 kHz).

$$\therefore \beta = \frac{R_3}{R_2 + R_3}$$

$$\therefore 1 + \beta = \frac{R_2 + 2R_3}{R_2 + R_3}$$

$$2(1 - \beta) = \frac{R_2}{R_2 + R_3}$$