

(1)

## TOPIC :- Expression for Voltage Gain in Different Frequency Ranges in R-C Coupled Amplifiers

UG-72

In order to derive the approximate expression for the voltage gain of a single stage R-C Coupled amplifier, employing the following let us assume that-

- (i) the bias resistors are of sufficient large value so that they do not affect the a-c operation of the circuit.
- (ii) the reactance of the emitter bypass capacitor is zero.
- (iii) the two transistors are identical.
- (iv) the h<sub>ie</sub> and h<sub>oe</sub> of each transistor are negligibly small.
- (v) the h<sub>ie</sub> and h<sub>oe</sub> of the transistors do not vary with frequency.

Mid-frequency Range: → In this frequency range, the reactance of the coupling capacitor C is assumed to be zero, and the collector output capacitor and any shunt capacitor, which appear in shunt across the output, are considered open-circuited. Hence if the transistor is replaced by its approximate h-parameter model, the equivalent circuit of the first stage of the R-C Coupled amplifier appears in fig(1). In this equivalent circuit h<sub>re</sub> and h<sub>oe</sub> are put to zero.

(2)

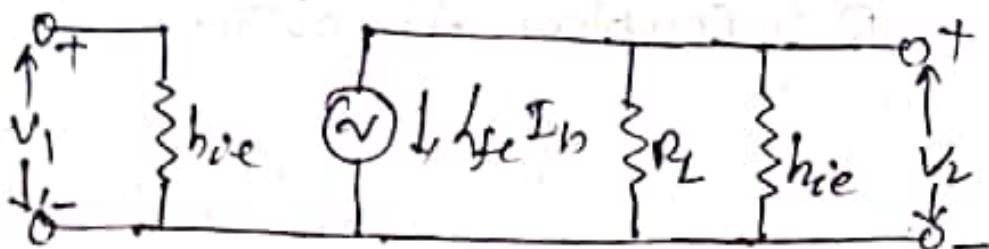


Fig 8(1)

The effective load resistance  $Z_L$  of the first stage of the amplifier is obtained from the relationship

$$\frac{1}{Z_L} = \frac{1}{R_L} + \frac{1}{h_{ce}}$$

$$\text{or, } Z_L = \frac{h_{ce} R_L}{h_{ce} + R_L} \longrightarrow \textcircled{1}$$

Therefore, the output voltage  $V_2$  is

$$V_2 = -h_{fe} I_B Z_L \longrightarrow \textcircled{2}$$

and the input voltage  $V_1$  is

$$V_1 = h_{ce} I_B \longrightarrow \textcircled{3}$$

∴ The voltage gain in the mid-frequency range is given by

$$A_{vm} = \frac{V_2}{V_1} = -\frac{h_{fe} Z_L}{h_{ce}} = -\frac{h_{fe} R_L}{h_{ce} + R_L} \longrightarrow \textcircled{4}$$

The negative sign in eq<sup>n</sup> ④ indicates that there is a phase shift of  $\pi$  radians between the output and the input signal voltage.