

(3)
 Continued to - Expression for voltage gain in R.C. Coupled
 Amplifier. 1/3-III

Low frequency gain

In this range, the reactance of the coupling capacitor is appreciable and cannot be neglected. In fact, this capacitor is primarily responsible for the fall of the gain of frequencies below the mid-band range. However, the reactance of the shunt capacitor may still be assumed infinite. Hence the ac equivalent circuit of an RC Coupled transistor amplifier in the low frequency range is as shown in fig (2)

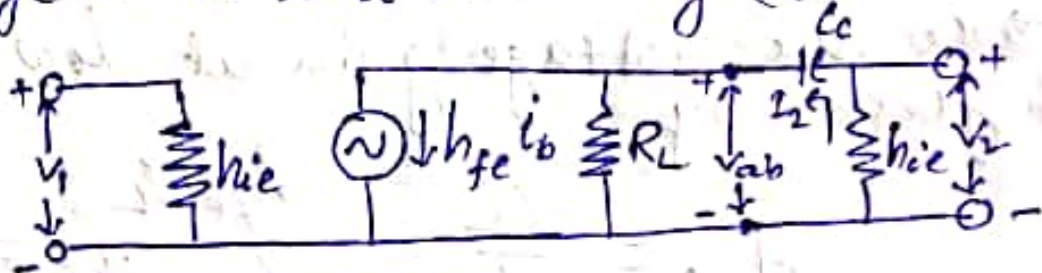


Fig (2)

The effective load impedance Z_L of the amplifier is given by

$$\frac{1}{Z_L} = \frac{1}{R_L} + \frac{1}{h_{ie} - j/\omega C_c} \quad \text{--- (5)}$$

where $\omega = 2\pi f$, f being a frequency in the low-frequency range. From equation (5), we get

$$Z_L = \frac{R_L (h_{ie} - j/\omega C_c)}{h_{ie} + R_L - j/\omega C_c} \quad \text{--- (6)}$$

Therefore, the potential ~~difference~~ difference between the points a and b is

$$V_{ab} = -h_{fe} I_b Z_L \quad \text{--- (7)}$$

(4) If I_2 be the current through h_{ie} and C_e , then

$$E_2 = -\frac{V}{h_{ie} - j\omega C_e} = \frac{h_{ie} I_b Z_L}{h_{ie} - j\omega C_e} \quad \text{--- (8)}$$

Therefore, the output voltage V_2 is given by

$$V_2 = -h_{ie} I_2 = -\frac{h_{ie} h_{fe} I_b Z_L}{h_{ie} - j\omega C_e} \quad \text{--- (9)}$$

The input voltage is

$$V_1 = h_{ie} I_b \quad \text{--- (10)}$$

Hence the voltage gain at low frequencies is given by

$$A_{vL} = \frac{V_2}{V_1} = -\frac{h_{fe} Z_L}{h_{ie} - j\omega C_e} \quad \text{--- (11)}$$

This equation shows that the gain is a complex quantity having a magnitude and a phase angle given by respectively

$$|A_{vL}| = \frac{h_{fe} R_L}{\sqrt{(h_{ie} + R_L)^2 + 1/\omega^2 C_e^2}} \quad \text{--- (12)}$$

$$\text{and } \phi = \pi + \tan^{-1} \frac{1/\omega C_e}{(h_{ie} + R_L)} \quad \text{--- (13)}$$

Eqⁿ (11) may be written as

$$A_{vL} = \frac{(-h_{fe} R_L) / (h_{ie} + R_L)}{1 - j\omega C_e (h_{ie} + R_L)} \quad \text{--- (14)}$$

$$= \frac{1}{1 - j 2\pi f C_e (h_{ie} + R_L)} \quad \text{--- (14)}$$

Eqⁿ (14) gives the variation of A_{vL} with frequency in the low-frequency range, relative to the mid-band gain A_{vm} . At the lower half-power frequency f_L , the magnitude of the low-frequency voltage gain is $1/\sqrt{2}$ or 0.707 times the magnitude of the mid-frequency gain. Therefore, at $f = f_L$ we get

$$\frac{|A_{vL}|}{|A_{vm}|} = \frac{1}{\sqrt{1 + 1/\{2\pi f_L C_e (h_{ie} + R_L)\}^2}} \quad \text{--- (15)}$$

$$\text{or } 2 = 1 + 1/\{2\pi f_L C_e (h_{ie} + R_L)\}^2$$

$$\text{or } 2\pi f_L C_e (h_{ie} + R_L)^2 = 1$$

$$\therefore f_L = \frac{1}{2\pi C_e (h_{ie} + R_L)} \quad \text{--- (16)}$$

Putting eqⁿ (16) in eqⁿ (14), we have

$$A_{vL} = \frac{A_{vm}}{1 - j(f/f_L)} \quad \text{--- (17)}$$

$$\therefore |A_{vL}| = \frac{|A_{vm}|}{1 + (f/f_L)^2} \quad \text{--- (18)}$$

(6) Show in this range of frequency, as f decreases, $|A_{vH}|$ decreases and ϕ increases.

(c) High-Frequency gain

In this frequency range, the effect of the coupling capacitor is negligible. Hence its reactance is assumed to be zero. Show the equivalent circuit of an RC coupled transistor amplifier. Can be shown in fig (3). Here C_{oc} represents the collector capacitance of the transistor and C_{ob} represents the stray wiring capacitance. The value of C_{oc} and C_{ob} is related to that of C_{ob} specified in the data sheet by the relation:

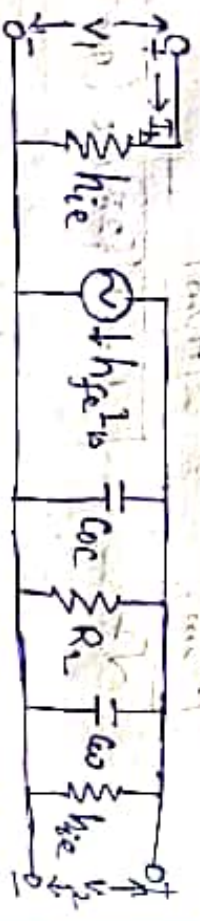


Fig (3)

$$C_{oc} = \frac{C_{ob}}{1 + h_{fb}}$$

Let $C_{os} = C_{oc} + C_{ob}$, where C_{os} is the total capacitance in shunt across the output. The effective

(7) load impedance Z_L of an amplifier is then given by

$$\frac{1}{Z_L} = \frac{1}{R_L} + \frac{1}{h_{ie}} + j\omega C_{os}$$

$$\text{or } Z_L = \frac{h_{ie} R_L}{h_{ie} + R_L + j\omega C_{os} h_{ie} R_L} \quad \text{--- (8)}$$

Therefore, $V_2 = -h_{fe} I_b Z_L$
The gain in the high frequency range is

$$A_{vH} = \frac{V_2}{V_1} = -\frac{h_{fe} I_b Z_L}{I_b} = -\frac{h_{fe} Z_L}{h_{ie}}$$

Substituting the value of Z_L in equation (8), we get

$$A_{vH} = -\frac{h_{fe} R_L}{h_{ie} + R_L + j\omega C_{os} h_{ie} R_L}$$

$$= \frac{(-h_{fe} R_L) / (R_L + h_{ie})}{1 + j\omega C_{os} h_{ie} R_L / (h_{ie} + R_L)}$$

$$= \frac{A_{vHm}}{1 + j 2\pi f C_{os} h_{ie} R_L / (h_{ie} + R_L)}$$

This equation gives the variation of A_{vH} with frequency in the high frequency range, relative to mid band gain A_{vHm} .