

# ⇒ Conversion of NAND ckt. into OR, AND

## & NOT Circuits:

A NAND-gate can be used to build an OR, AND, or a NOT ckt. when all inputs of a NAND gates are connected together. A NOT-gate results shown in fig. 6(a), because if  $A=1$ , the output of a NAND gate is  $\bar{A} \cdot \bar{A} = \bar{1} \cdot \bar{1} = \bar{1} = 0$  and if  $A=0$ , the output is  $\bar{A} \cdot \bar{A} = \bar{0} \cdot \bar{0} = \bar{0} = 1$ .



Fig. 6(a) NOT-gate from NAND gate.

→ AND ckt:- A NAND-gate followed by NOT ckt is an AND gate. shown in fig. 6(b).

 


Fig. 6(b): AND from NAND & NOT.

AND-gate can also be obtained by using two NAND-gates repeatedly fig. 6(c). The output of two inputs NAND-gate is fed to single input.

 


Fig. 6(c) Double NAND's is a AND.

In NAND-gate, Hence

$\overline{A \cdot B} = A \cdot B$  which is output of an AND gate

→ OR-GATE: OR-gate. Fig 6-(d) from NAND gate is obtained by using two single input NAND gates and one, two inputs NAND gate.

 


Fig- 6-(d).

First two NAND's convert  $A$  &  $B$  into  $\overline{A}$  &  $\overline{B}$ .  
 The 2nd two inputs NAND gives  $\overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A+B}} = A+B$ , which is OR-gate. OR-gate can also be obtained by connecting two NOT-output to two inputs of a NAND shown fig. 6(e).

 


Fig- 6-(e) OR-gate from 1 NAND

two NOT