

# **Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)**

## **Lecture – 5**

**TDC PART – II  
Paper - III (Group - A)  
Chapter - 4**

**by:**

**Dr. Niraj Kumar,**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,  
Muzaffarpur.**

# Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)

## Lecture – 5

TDC PART – II

Paper - III (Group - A)

Chapter - 4

### ■ (Uni Junction Transistor)

### ■ Lecture Content :-

#### ➤ UJT Parameters

➤ (2) Intrinsic Stand-off Ratio ( $\eta$ ) by 2nd Method

➤ (2) Intrinsic Stand-off Ratio ( $\eta$ ) by 3rd Method

# UJT Parameters

## (2) Intrinsic Stand off Ratio ( $\eta$ ) by 2nd Method

- **Figure (13)** Shown below, a battery  $V_{BB}$  connected across Base  $B_2$  and  $B_1$  of equivalent circuit of UJT. Here emitter point  $E$  acts as a Voltage Divider Tap on the fixed resistance  $R_{BB}$ . It is obvious that part of  $V_{BB}$  is dropped over  $R_{B2}$  and part on  $R_{B1}$ . Let the voltage drop across  $R_{B1}$  is  $V_{RB1}$ , then the magnitude of  $V_{RB1}$  (with  $I_E = 0$ ) is equal to  $V_A$ .

■  $V_{RB1} = V_A = V_{BB} ( R_{B1} / R_{B1} + R_{B2} )$   
where,  $I_E = 0$  ..... (1)

■ Where,  $R_{BB} = R_{B1} + R_{B2}$

■ ( **$R_{BB}$  Inter Base Resistance** when no voltage is applied to the Emitter (E) ).

■ From equation (1), we have,


$$\text{■ } V_A / V_{BB} = R_{B1} / (R_{B1} + R_{B2}) \quad \dots\dots\dots (2)$$

■ The ratio  $V_A / V_{BB}$  is called the **Intrinsic-  
Stand off Ratio** and is represented by  $\eta$ .

■ Hence ,

■  $\eta = R_{B1} / (R_{B1} + R_{B2}) = R_{B1} / R_{BB}$   
where,  $I_E = 0$  ..... (3)

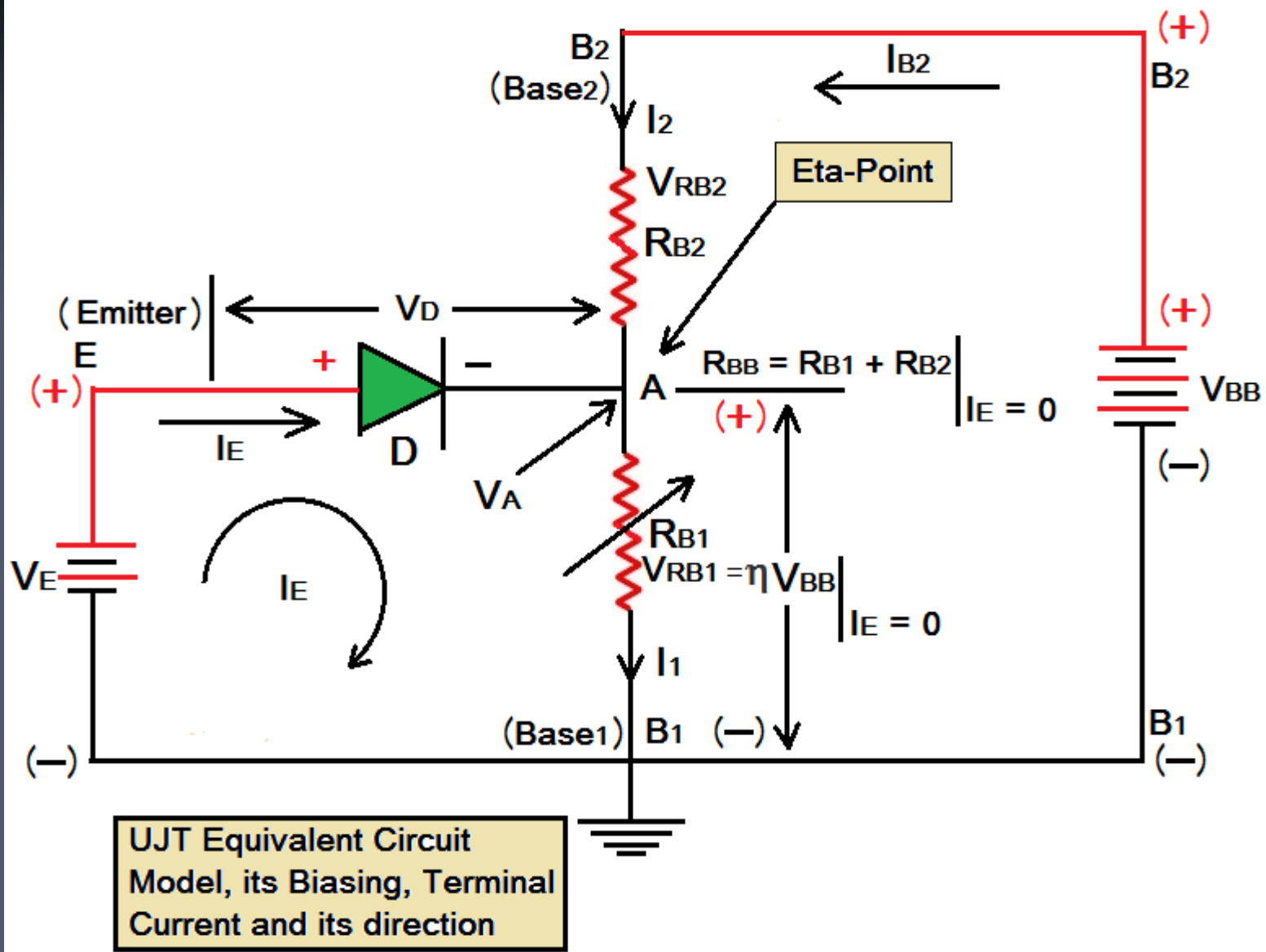■ The **Intrinsic Stand-off Ratio** ( $\eta$ ) is the property of the **UJT** and is always **less than unity(0.4 to 0.85)**. Voltage across  **$R_{B1}$**  is,



■ Fig (13) Shown Typical UJT Equivalent Circuit Diagram.

■  $V_{RB1} = V_A = (R_{B1} / R_{BB}) V_{BB}$   
where,  $I_E = 0$  ..... (4)


■  $V_{RB1} = V_A = \eta V_{BB}$   
where,  $I_E = 0$  ..... (5)

■ The voltage  $\eta V_{BB}$  appearing across  $R_{B1}$  Reverse-Biases the diode and hence the Emitter Current  $I_E = 0$


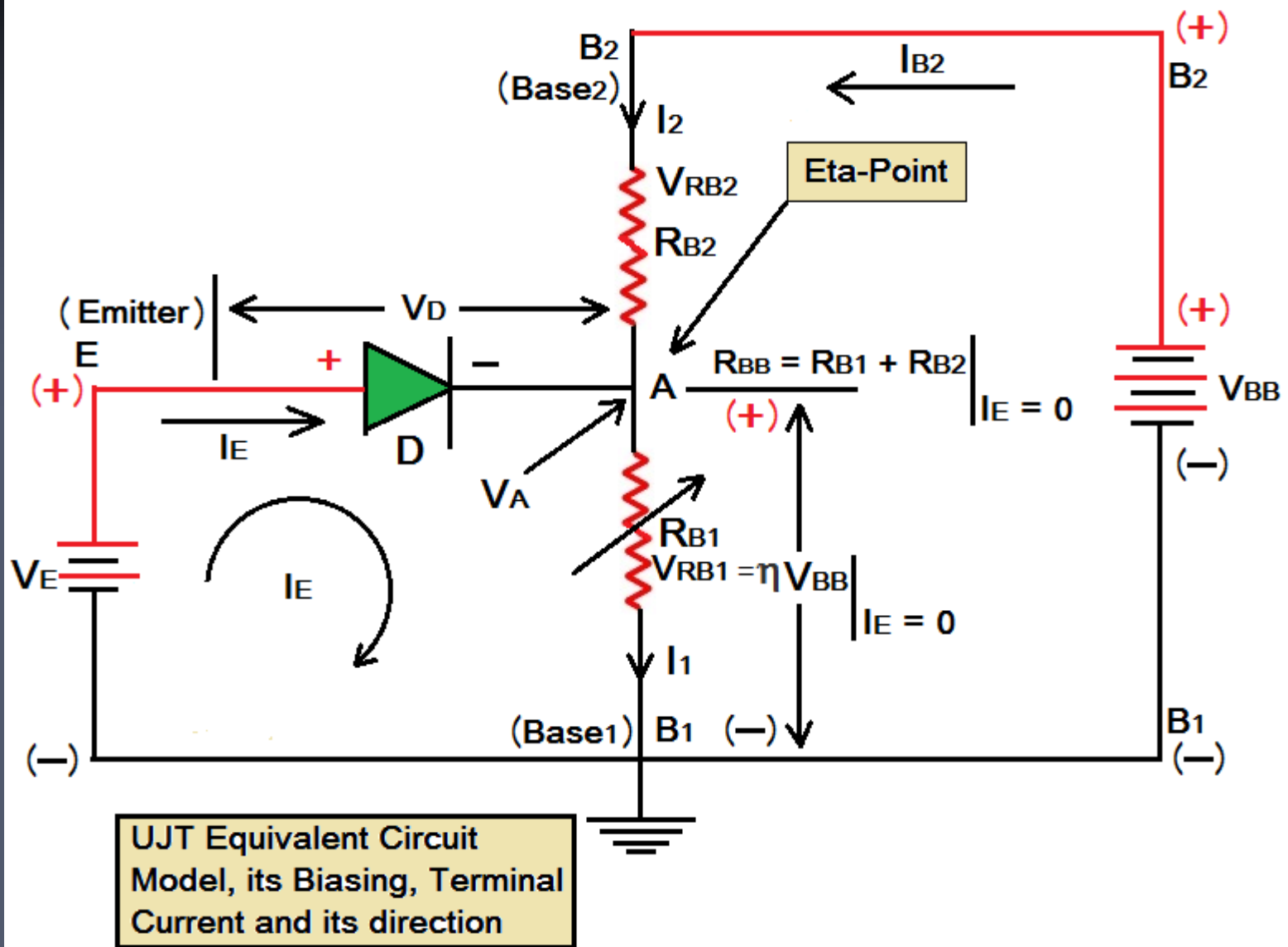
## (2) Intrinsic Stand off Ratio ( $\eta$ ) by 3rd Method

- Intrinsic Stand-off Ratio (  $\eta$  ) can be describe as,
- When Inter Base Voltage (  $V_{BB}$  ) is applied across the Two Base terminals **B1** and **B2** shown in below **Figure (14)**, the potential of **Point A** with respect to **B1** is given by
- $V_{AB1} = ( V_{BB} / R_{B1} + R_{B2} ) R_{B1}$
- $V_{BA1} = ( R_{B1} / R_{B1} + R_{B2} ) V_{BB}$



■ Fig (14) Shown Typical UJT Equivalent Circuit Diagram.

- $V_{AB1} = \eta V_{BB}$

- Where,  $\eta = R_{B1} / R_{B1} + R_{B2}$

- $\eta$  (nita) is called the **Intrinsic Stand off Ratio** ( $\eta$ ).

- The **Intrinsic Stand off Ratio** is the property of the **UJT** and is always **Less than Unity**. The typical value of  $\eta$  are **.51 to .82**.

**to be continued .....**