

Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)

Lecture – 6

TDC PART – II

Paper - III (Group - A)

Chapter - 4

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L.S. College, BRA Bihar University,
Muzaffarpur.**

Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)

Lecture – 6

TDC PART – II


Paper - III (Group - A)

Chapter - 4

- (Uni Junction Transistor)
- Lecture Content :-
 - UJT Parameters
 - (3) Circuit Arrangement for UJT V-I Characteristics

UJT Parameters

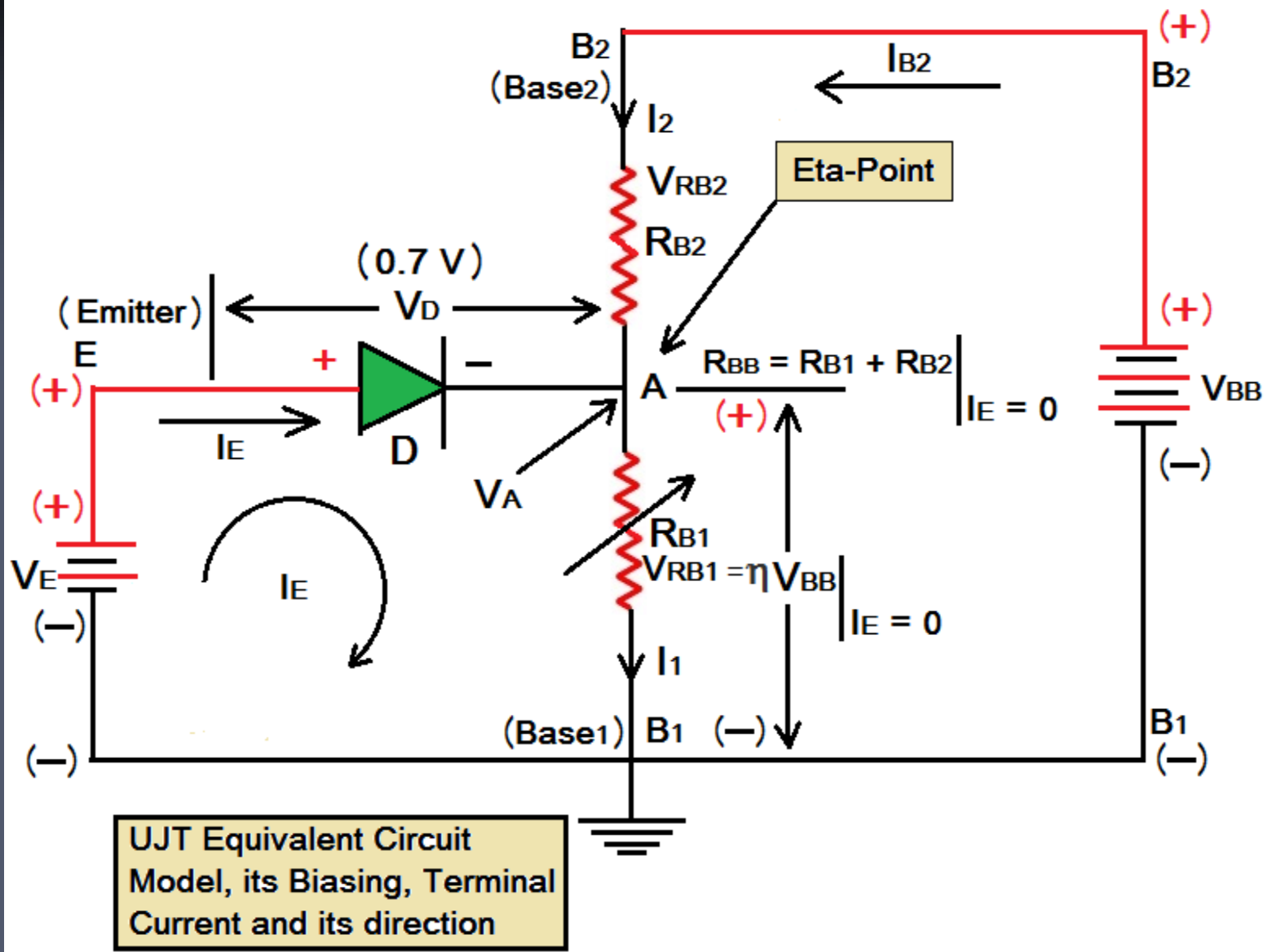- (3) Circuit Arrangement for UJT V-I Characteristics
- For ease of understanding, the internal model of the UJT is used in the circuit shown below in **Figure (14)**. (Base2) B2 terminal of the UJT is made Positive (+) with respect to (Base1) B1 terminal using the Voltage Source V_{BB} . Emitter Terminal E of the UJT is Forward Biased using the Voltage Source V_E .



■ Fig (14) Shown Typical Circuit Diagram for UJT V – I Characteristics.

- **Current starts flowing** into the **Emitter only** when the **Bias Voltage V_E** has exceeded the **Forward Voltage drop of the Internal Diode (V_D) (0.7 V)** plus the **Voltage drop across R_{B1} ($V_{R_{B1}}$)**. This condition can be expressed using the following equation given below.

- $V_E = V_D + V_{RB1}$

- Considering the **Intrinsic Stand off Ratio** $\eta = R_{B1} / (R_{B1} + R_{B2})$, then the equation becomes,

- $V_E = V_D + \eta V_{BB}$

- A typical Silicon Diode has a Forward Voltage drop of $V_D = 0.7 \text{ V}$. When this factor is considered, the equation can be re written as,
- $V_E = 0.7 \text{ V} + \eta V_{BB}$
- This minimum value of the Emitter Voltage V_E for which the Emitter Current I_E starts to flow is called the Firing Voltage of UJT.


- As the **Emitter Voltage V_E** is increased the **Emitter Current I_E** is also **Increased** and the **junction behaves like a typical P-N Junction**. But the **Emitter Voltage V_E** can be only **Increased Up** to a **particular point called V_P (Peak Voltage)**.

- At this **Peak Point V_P** , a considerable amount of **Emitter Current I_E** flows and a significant number of **Holes** are **Injected into the Junction**. These **Holes** are **repelled by (Base2) B_2** and attracted by **(Base1) B_1** .

- As a result, the region between Emitter (E) and (Base1) B1 terminal starts Saturating by Holes and the Conductivity of this region starts to Increase. This phenomenon of Increasing Conductivity by the Insertion of Holes is called **Conductivity Modulation**.

- **This Increased Conductivity Reduces R_{B1} and Intrinsic Stand of Ratio (η). This results in a condition where Emitter Current I_E Increases and the Emitter Voltage V_E Decrease. This situation is similar to a Negative Resistance Scenario.**

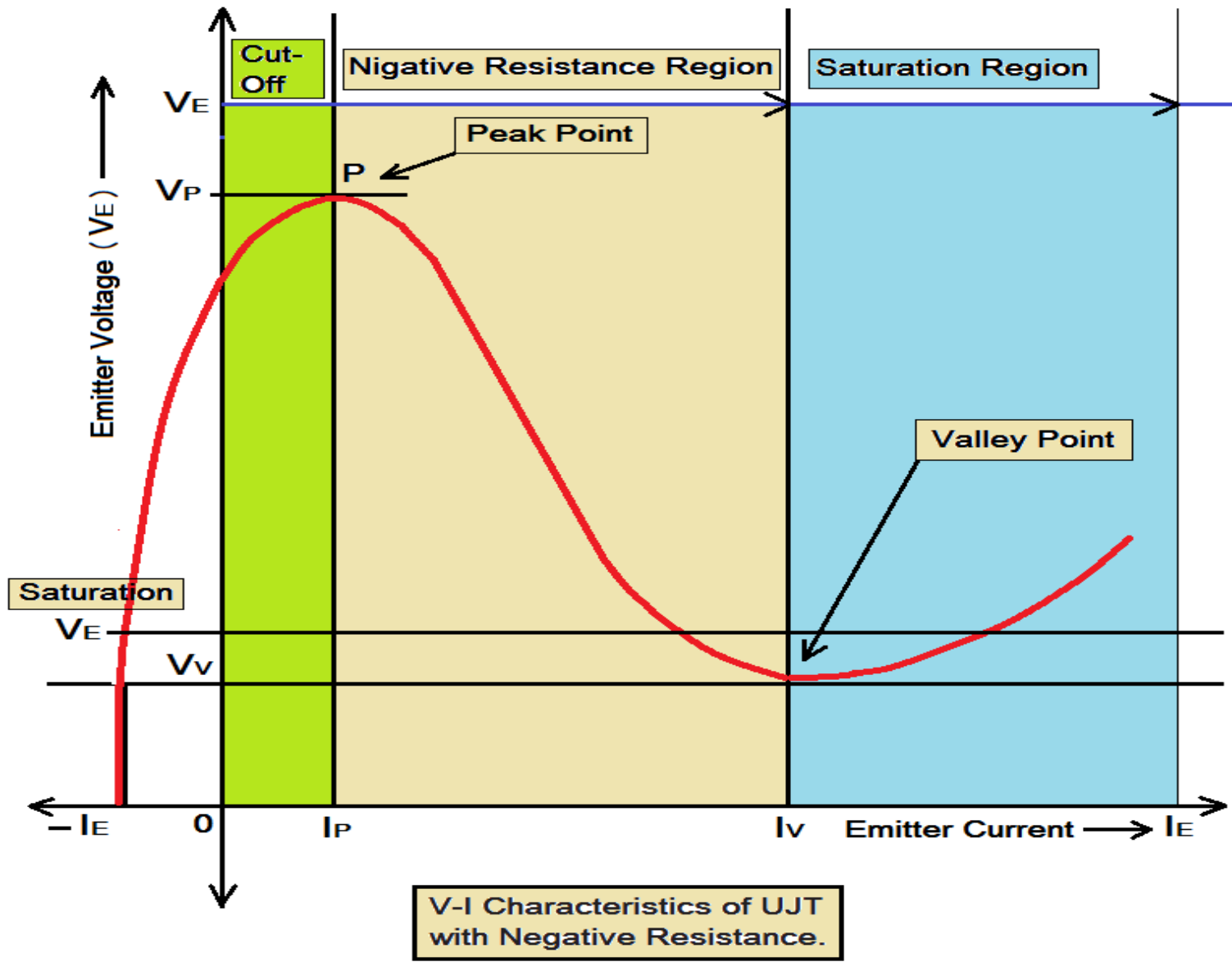- In the **V-I Characteristic** of UJT, which is shown in below **Figure (15)**, we can see that the regions between V_P (**Peak Voltage Point**) and V_V (**Valley Voltage**) have a **Negative Slope**. This **Negative Resistance Region** in the UJT Characteristics is employed in **Oscillator Circuit**.



■ Fig (15) Shown V-I Characteristics of UJT with Negative Resistance Region.

- At last the **Emitter Current I_E** will be **Increased** to a point that no more **Increase in Conductivity** is possible. This point is called **“Valley Point”**.
- The **Emitter Current I_E** corresponding to **Valley Point** is denoted as **I_V** and the corresponding **Emitter Voltage V_E** are denoted as **V_V** . Beyond the **Valley Point**, the **UJT** is **Fully Saturated** and the **Junction** behaves like a **Fully Saturated P-N junction**.

to be continued