

**Paper 7, TDC Part-3**  
**Chapter– 1, Fundamental Concept of Digital**  
**Electronics**  
**Lecture - 4**

**By:**

**Mayank Mausam**  
**Assistant Professor (Guest Faculty)**  
**Department of Electronics**  
**L.S. College, BRA Bihar University,**  
**Muzaffarpur, Bihar**

# Fundamental Concepts of Digital Electronics

In 3rd lectures we have discussed about “NAND” Gate and realization of basic gates using “NAND” gate.

In this lecture we will discuss about “NOR” gates and realization of basic gates using “NOR” gate.

# Fundamental Concepts of Digital Electronics

- **The NOR Logic : -**

The NOR logic (operation) is a combination of two basic logics, the NOT & OR logics. This means that the output of the NOR gate is the inverted (complement) output of OR gate.

The NOR operation is defined as:- When all the inputs are at logic “0” then the output is at logic “1” else the output is at logic “0”. The NOR Gate can have N numbers of inputs ( $N \geq 2$ ) and One output.


# Fundamental Concepts of Digital Electronics

The logical expression of NOR operation is given by

$$Y = \overline{A \text{ OR } B \text{ OR } C \text{ OR } \dots \text{ OR } N}$$


$$Y = A + B + C + \dots + N$$

- **Symbol for NOR Gate :-**

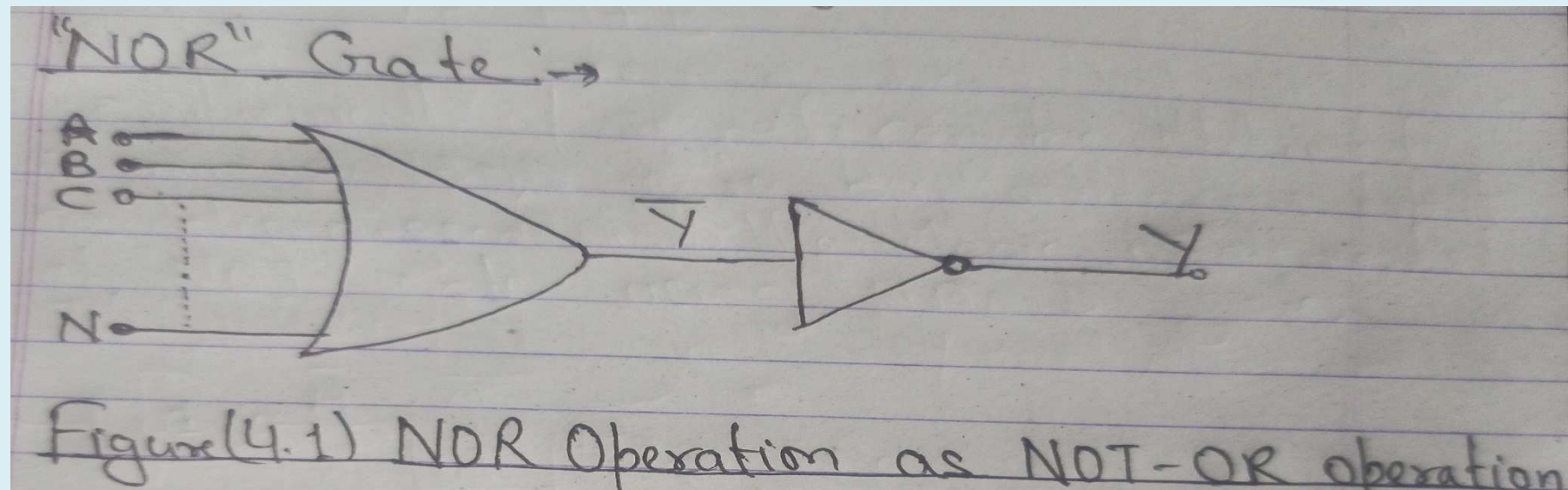

# Fundamental Concepts of Digital Electronics

- **Symbol for NOR Gate : -**

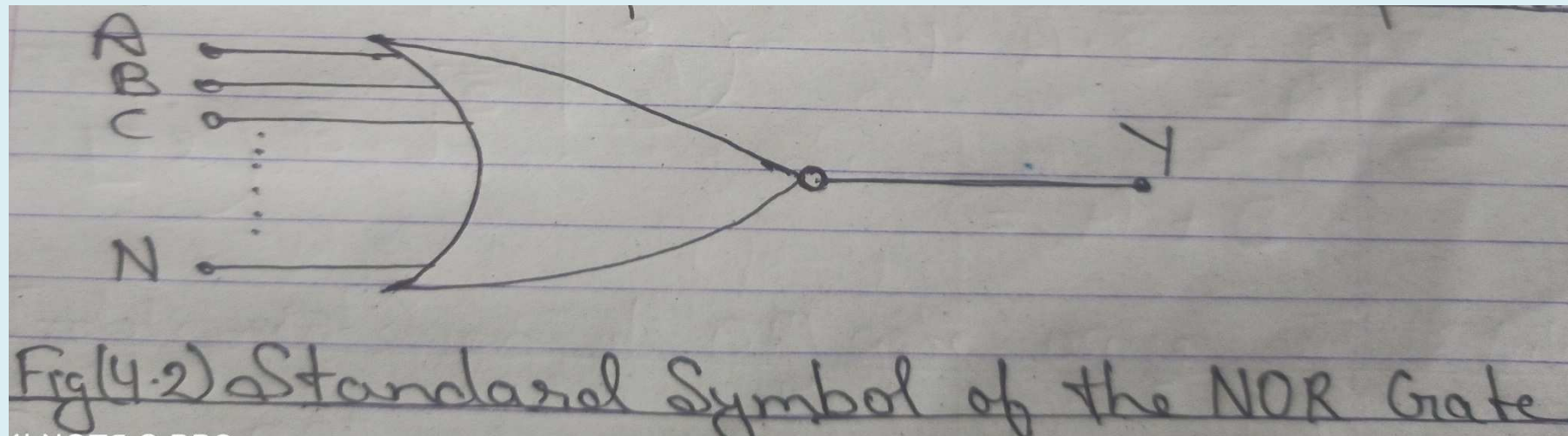

Symbol shown in above figure is usually used to represent “NOR” gate.

A bubble on the output side of the “NOR” gate represent “NOT” operation.

# Fundamental Concepts of Digital Electronics

- **Logic Equation & Truth Table for NOR Gate :-**

- **2 input NOR Gate**

Logic equation for 2 input NOR gate is:-

$$Y = \overline{A + B}$$

Input (A)	Input (B)	Output (Y)
0	0	1
0	1	0
1	0	0
1	1	0

**Truth Table for 2- Input NOR Gate**

# Fundamental Concepts of Digital Electronics

## ➤ 3 input NOR Gate

Logic equation for 3 input NOR gate is:-

$$Y = \overline{A + B + C}$$

Input (A)	Input (B)	Input (C)	Output (Y)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0
Truth Table for 3 Input NOR Gate			

## Fundamental Concepts of Digital Electronics

Similarly the truth table of a NOR Gate with any numbers of input signals can be written. The output of a NOR Gate will be at logic “1 (High)” when all the input signals are at logic “0 (Low)” otherwise for any other combinations of inputs signal, the output will be at logic “0 (Low).

All three basic gates, “NOT”, “OR” & “AND” gate can also be realized using “NOR” Gate



## Fundamental Concepts of Digital Electronics

Similarly the truth table of a NOR Gate with any numbers of input signals can be written. The output of a NOR Gate will be at logic “1 (High)” when all the input signals are at logic “0 (Low)” otherwise for any other combinations of inputs signal, the output will be at logic “0 (Low).

All three basic gates, “NOT”, “OR” & “AND” gate can also be realized using “NOR” Gate

# Fundamental Concepts of Digital Electronics

## Realization of "OR" Gate using "NOR" Gate's

Since the output of "NOR" gate is complement of "OR" gate so to realize ~~NOR~~ "OR" Gate using "NOR" gate can be done by, complementing the output of "NOR" gate, as shown in below figure

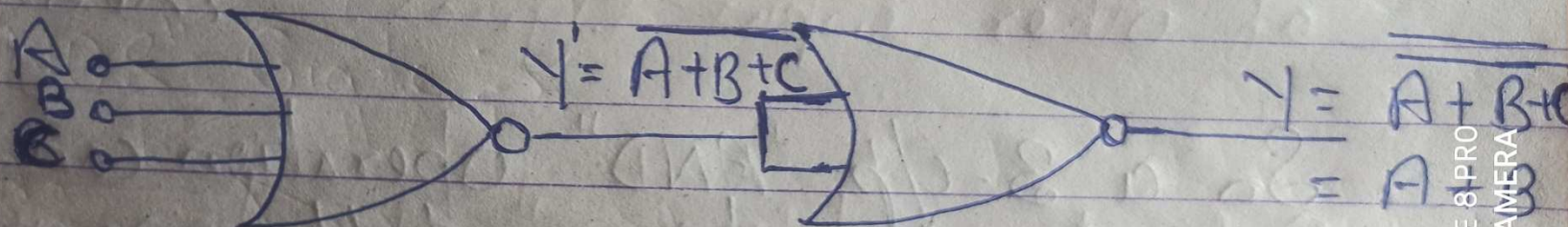


Figure (4.4) → "OR" Gate using "NOR" Gate



# Fundamental Concepts of Digital Electronics

The above operation can be understood from the truth table of above diagram.

$\overline{A}$	B	C	$Y' = \overline{Y}$	$Y = A + B + C$
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1



# Fundamental Concepts of Digital Electronics

Realization of "AND" Gate using "NOR" Gate

Realization of 3-I/P "AND" operation

Output of 3-I/P AND operation is

$$Y = ABC$$

$$\text{or } Y = \overline{\overline{ABC}}$$

$$Y = \overline{\overline{A} + \overline{B} + \overline{C}}$$

[As Per Demorgan's Theorem]

So a 3-i/p "AND" operation can be realized using "NOR" gate in following manner:-



# Fundamental Concepts of Digital Electronics

i) Complement all the input signals <sup>seperately</sup> using "NOR" gate.

(ii) Now apply these signals at the input of next "NOR" gate.

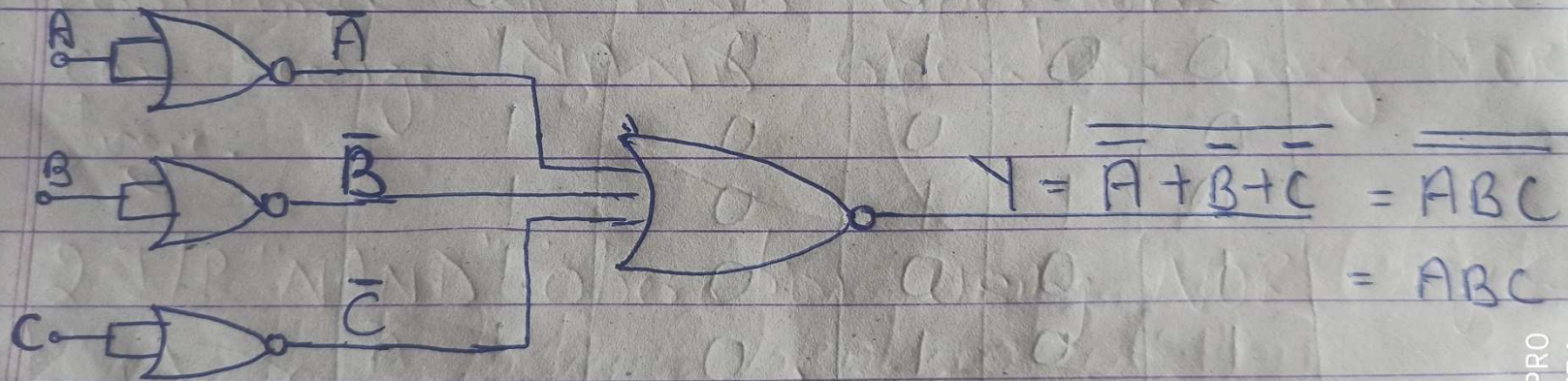


Figure (4.5) Realization 3 i/p "AND" Operation using "NOR" Gate




# Fundamental Concepts of Digital Electronics

In similar manner "AND" operation with any no. of input signal can be realized using "NOR" gate.

Example 1.9) If one of the <sup>input</sup> of a "NOR" gate is connected to logic 0 voltage, find the output voltage in terms of the other input.

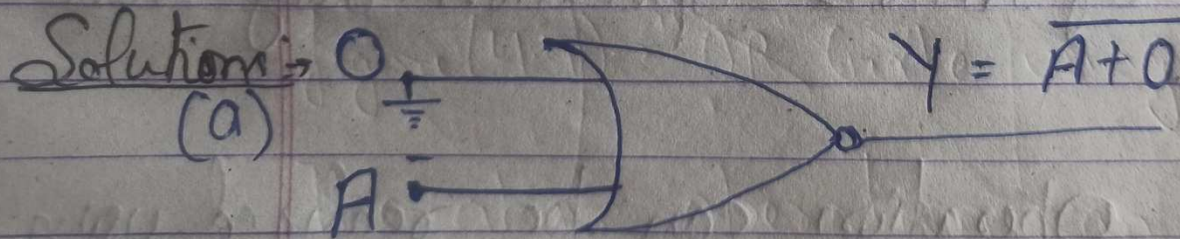
(b) Repeat (a) if one of the inputs is connected to logic 1 voltage.






# Fundamental Concepts of Digital Electronics

Solution:

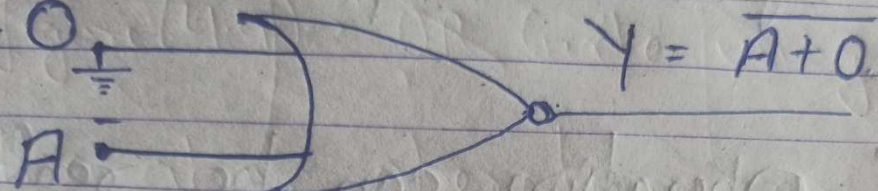(a)   $Y = A + 0$

Now when  $A = 0$  then  $Y = \overline{0 + 0} = \overline{0} = 1$   
" "  $A = 1$  "  $Y = \overline{1 + 0} = \overline{1} = 0$

So the o/p voltage in terms of the input A is,  
 $Y = \overline{A}$

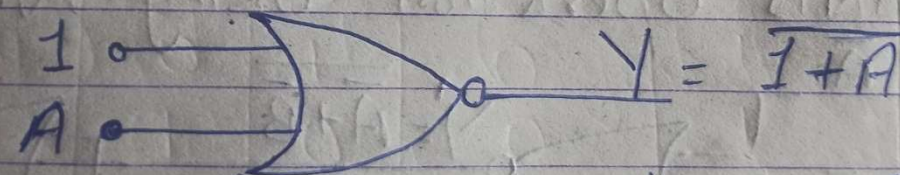(b)   $Y = 1 + A$

Now when  $A = 0$  then  $Y = \overline{1 + 0} = \overline{1} = 0$   
" "  $A = 1$  "  $Y = \overline{1 + 1} = \overline{0} = 1$

# Fundamental Concepts of Digital Electronics

So If one of the input is connected to logic '1' (High) then the output is always at logic "0" (Low) irrespective of the state of input signal, for a "NOR" Gate

In case of 2 input "NOR" gate if one of the input is connected to logic "0" (Low) then the output is always at inversion of other input signal.



# Fundamental Concepts of Digital Electronics

- **Realization of NAND Logic using NOR Logic :-**

A "NAND" Operation can be realized using "NOR" logic. We have ~~seen~~ that ~~we~~ realize the "AND" & "NOT" operation using "NOR" operation. "NAND" operation is inversion/complement of "AND" operation. Hence we can realize "NAND" operation using "NOR" logic.

2 I/P "NAND" operation using "NOR" logic

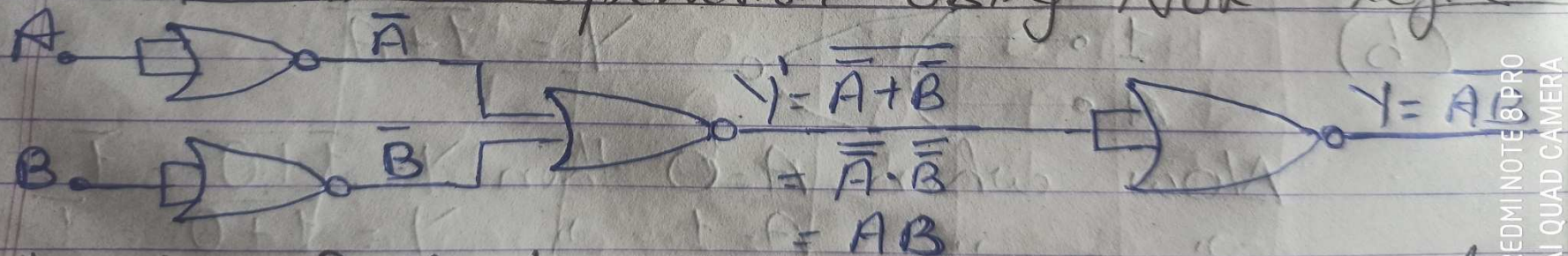


figure (4.6) Realization of NAND Operation using NOR logic

## Fundamental Concepts of Digital Electronics

In a similar manner NOR operation can be realized using the NAND logic. Implementation of NOR logic using NAND logic has been left as a task.

We have realize all types of logic gate through either “NAND” or “NOR” logic. So we can design any type of digital circuit through only either NAND or NOR logic. Due to this reason NAND and NOR gate are also referred as universal gate.