

Waveform Generation

Lecture - 11

(22/04/2021)

B.Sc (Electronics)

TDC PART - III

Paper – 6

Unit – 8

by:

Dr. Niraj Kumar

Assistant Professor (Guest Faculty)



Department of Electronics

L. S. College, BRA Bihar University, Muzaffarpur.

➤ **Introduction of Transistor Mono-Stable Multivibrator (PART – 1)**

⇒ It is also called a **Single-Shot** or **Single Swing** or a **One-Shot Multivibrator**. Other names are: **Delay Multivibrator** and **Univibrator**. It has

- (i) One absolutely stable (stand-by) state i.e., permanent and
- (ii) One quasi-stable state i.e., temporary.

⇒ The **Mono-Stable** or **One-Shot Multivibrator** has **One Stable State** i.e., permanent and **One Quasi-Stable (i.e. half-stable) State** i.e., temporary. When an external trigger pulse is applied to the input, the multivibrator changes the state from stable state to quasi-stable state.

⇒ The application of **external input pulse** triggers the circuit into its **Quasi-Stable State**, in which it **remains for a period of time** determined by circuit constants.

⇒ After this **period of time**, the **circuit returns** to its **Initial Stable State**, the process is repeated upon the application of each **external trigger pulse**.

⇒ Since the **Mono-Stable Multivibrator** produces a **single output pulse** for each **input trigger pulse**, it is generally called **One-Shot Multivibrator**. It has one **energy-storing element** i.e. **one-capacitor**.

=

⇒ The **mono stable multivibrator** (sometimes called a **One-Shot Multivibrator**) is a **square or rectangular wave generator** with have just **one stable condition** and one **quasi stable condition**. With no input signal (quiescent condition) one **Transistor** (transistor as a switch) **Conducts** and the **other Transistor** (transistor as a switch) is in **Cut-OFF**. A **multivibrator** in which **one transistor is always conducting** (i.e. in the **ON State**) and the **other is non-conducting** (i.e. in the **OFF State**) is called a **Mono-Stable Multivibrator**.

⇒ The **operation** of the **Mono-Stable Multivibrator** is relatively simple. The **input is triggered with a pulse of voltage**. The **output changes** from **one voltage level** to a **different voltage level**. The **output remains** at this **new voltage level** for a definite period of time **determined by RC circuit component**. After this **period of time**, the **circuit automatically return** to its **initial original voltage level** and remains there **until another trigger pulse** is applied to the input.

⇒ **Mono-Stable Multivibrator** is also called a **Single-Shot** or **Single Swing** or a **One-Shot Multivibrator**. Other names are: **Delay Multivibrator** and **Univibrator**. The monostable or **one-shot multivibrator** has

- (i) one **absolutely stable** (stand-by) state and
- (ii) one **quasi-stable state** i.e. half-stable state

⇒ The application of **External input triggers pulse** the circuit can be **switched** from **Stable State** to the **Quasi-Stable state**, in which it **remains for a time period determined by RC circuit component**. After this period of time, the circuit **returns to its initial Stable state**. This process is repeated upon the application of each trigger pulse. Since the **Mono-Stable Multivibrator** produces a single output pulse for each input trigger pulse, it is generally called One-Shot multivibrator.

⇒ A **Mon-Stable** (mono means single or one) **Multivibrator** has only **One State Stable** and **One Quasi-Stable State** i.e. **half-stable state**. In other words, if one transistor is **Conducting (ON)** and the other one is **Non-Conducting (Cut-OFF)**, the circuit will remain in this position. It is only with the **application of external input triggers pulse** that the circuit will interchange the states. The application of **External input triggers pulse** the circuit can be **switched from Stable State** to the **Quasi-Stable State**, in which it **remains in this position for a time period determined by RC circuit component**. After this period of time, the circuit will automatically switch back to the **Original Stable State** and remains there until another input triggers pulse is applied. Thus a **Mono-Stable Multivibrator** cannot generate square waves of its own like an **Astable Multivibrator**. It produces a **single output pulse of a desired duration for every input trigger pulse**. Only **external pulse will cause** it to generate the **square wave**.

⇒ The basic Transistor Version **Mono-Stable Multivibrator** circuit diagram is shown below in **Figure (1)**. For instance, suppose at any particular instant, **Transistor Q1** is **CONDUCTING (ON)** and **Transistor Q2** is at **CUT-OFF**. It is **First Initial Stable State**. If left to itself, the **Mono-Stable Multivibrator** will stay in this position forever.

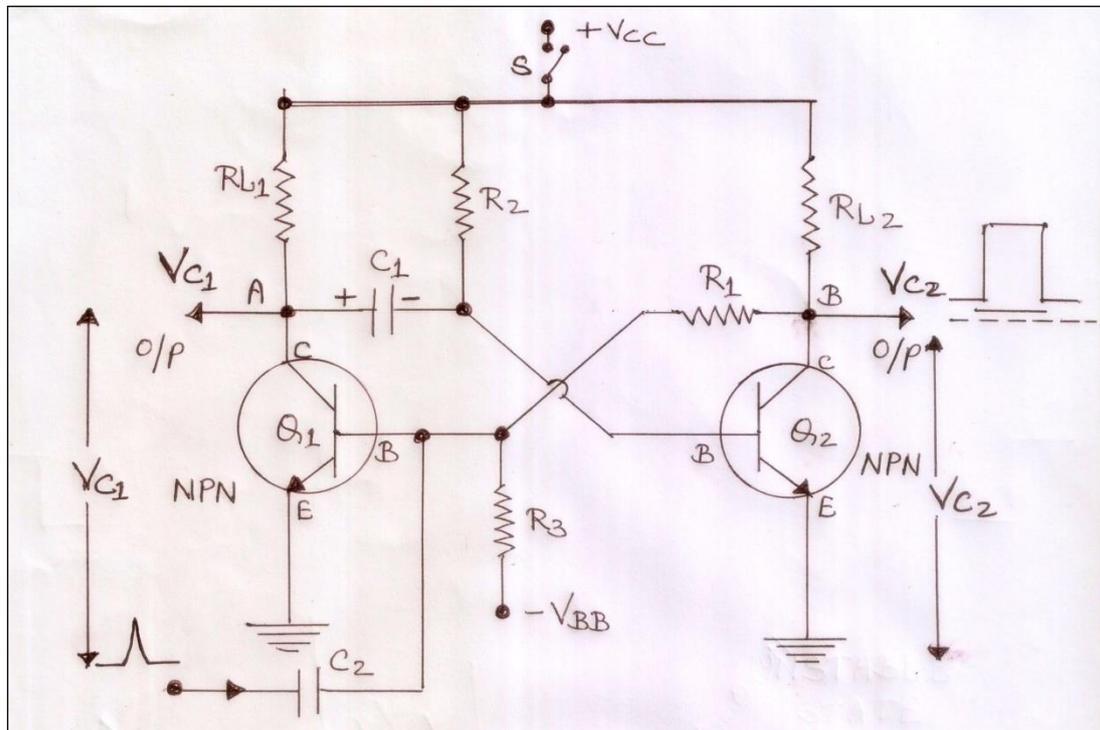


Fig. (1) Shown the Circuit Diagram of a Transistor Mono-Stable Multivibrator.

⇒ However, if an **external trigger pulse** is applied to the circuit in such a way that **Transistor Q1** is **CUT-OFF** and **Transistor Q2** is turned **CONDUCTING (ON)**. It is **second state** which is known as **Quasi-Stable State**. Again, if left to itself, the circuit will stay in the new position (**Quasi-Stable State**). It remains in this position for a time period determined by **RC circuit component**. After this period of time, the circuit will automatically switch back to the **Initial Stable State** and remains there until another input triggers pulse is applied.

⇒ This process is repeated upon the application of each trigger pulse. Since the **Mono-Stable Multivibrator** produces a single output pulse for each input trigger pulse, it is generally called One-Shot multivibrator. Thus a **Mono-Stable Multivibrator** cannot generate square waves of its own like an **Astable Multivibrator**. It produces a **single output pulse** of a desired duration for every **input trigger pulse**.

⇒ The **Mono-Stable Multivibrator** actually takes series of input triggers and converts them to **Uniform Square Pulses**, as shown below in **Figure (2)**. All of the **square output pulses** are of the same amplitude and time duration.

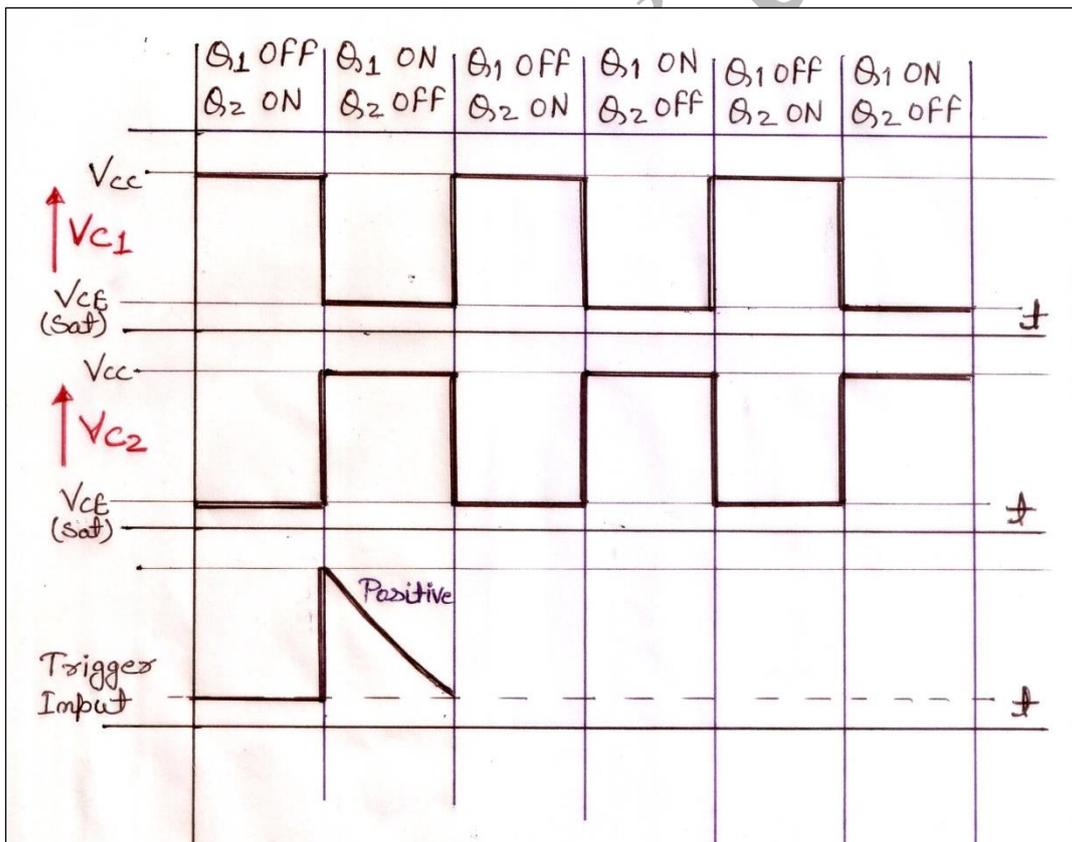


Fig. (2) Shown MMV Output Square Wave Forms at the both Transistor Q_1 and Q_2 Output Terminal Voltage V_{c1} and V_{c2} along with Positive Input Trigger Pulse.

⇒ Detailed of the Transistor Mono-Stable Multivibrator Circuit Diagram is discussed in next **Lecture – 12.**

to be continued

Dr. Niraj Kumar