

# **Silicon Controlled Rectifier (SCR)**

## **Lecture – 15**

**TDC PART – I**

**Paper - II (Group - B)**

**Chapter - 5**

**by:**

**Dr. Niraj Kumar,**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,  
Muzaffarpur.**

# Silicon Controlled Rectifier (SCR)

## Lecture – 15

TDC PART – I

Paper - II (Group - B)

Chapter - 5

- **SCR Turning-OFF Methods (PART – 3)**
- **Lecture Content :-**
  - **(2) Forced Commutation**
  - **(a) Anode Current Interruption Technique**
  - **(b) Basic Forced Commutation Technique**

## (2) Forced Commutation

- “In case of **DC circuits**, there is no natural current zero to **Turn OFF** the **SCR**. In such circuits, **forward current** or **Anode Current** must be **forced to zero** with an **external circuit** to **commutate the SCR** hence named as **forced commutation**”.
- The process of **Turning OFF** a SCR (thyristor) by using **External Circuits** is known as **Forced Commutation**. This method of commutation is used for **DC Commutation**.

- When using **DC supply**, we make use of **External Circuit** and other **Active/Passive Components** to reduce the **Passing current's** value below **Holding Current**. That means we force the **Forward Current** to come to **Zero** value. Therefore it is called **Forced Commutation**. The circuit used for **Forced Commutation Method** is known as **Forced Commutation Circuit** and the components that are used in the circuitry are known as **Forced Commutating Components**.

- Unlike **Natural Commutation**, an external circuitry is required to forcibly bring the **SCR Anode Current below Holding Current or almost to Zero** and keeping SCR **Reversed Biased or Unbiased** for a period more than the **SCR (thyristor) Turn-OFF Time**. This technique is applied for **DC circuit**. The commutation circuitry for **Anode Current Interruption and Forced Commutation** comprises of **Transistor, Battery and Battery**.

- This Forced Commutating Circuit consist of components like **Transistor, Battery and Switch** called as **Commutating Components**. These **Commutating Components** cause to apply a **Reverse Voltage** across the **SCR** or **Interrupt Anode Current** of the **SCR**, that immediately bring the current in the **SCR** to **Zero** then **SCR Turn OFF**.

■ Here next question of concern is; how long it's the **Turn-OFF time** and how is **Turn-OFF accomplished?** An **SCR** cannot be **Turned-OFF** by simply removing the **Gate Signal** at the **Gate Terminal** and only a special few can be **Turned-OFF** by applying a **Negative Gate Pulse ( $I_g$ )** to the **Gate Terminal**. In **Forced Commutation** there are **Two General Methods** for **Turning OFF the SCR**. Those are :-


- (a) **Anode Current Interruption Technique**
- (b) **Basic Forced Commutation Technique**
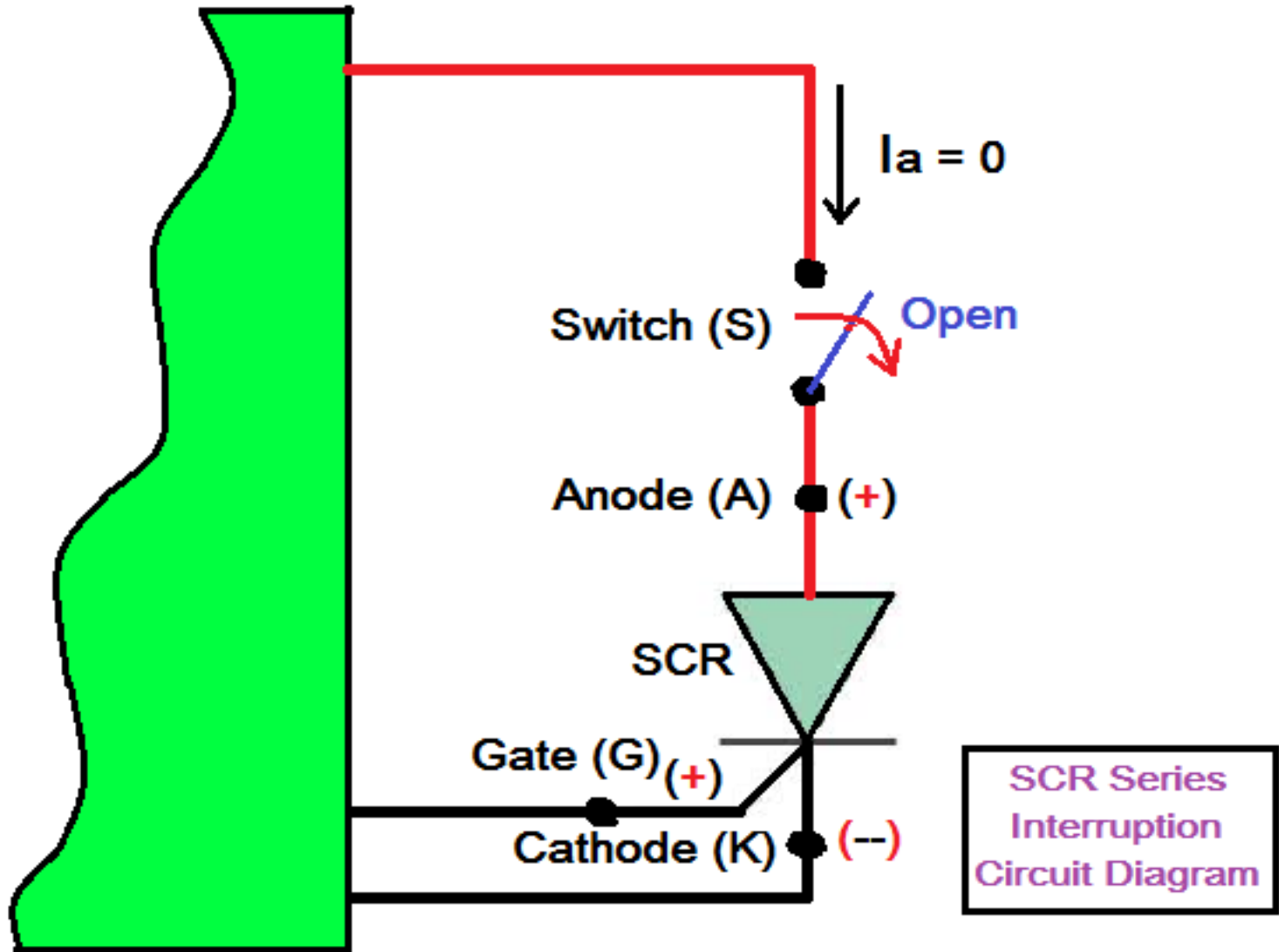
## (a) Anode Current Interruption Technique

- When the Anode Current ( $I_a$ ) is reduced below the level of the Holding Current ( $I_H$ ) or almost to Zero, the SCR Turns-OFF. However, it must be noted that rated Anode Current ( $I_a$ ) is usually larger than 1,000 times the Holding Current ( $I_H$ ). Since the Anode Voltage ( $V_a$ ) remains Positive with respect to the Cathode (K) in a DC Circuit, the Anode Current ( $I_a$ ) can only be reduced to Zero by Anode Current Interruption Technique”.




- **Anode Current Interruption Technique of SCR** commutation is also called **Forced Commutation**. **Anode Current Interruption Technique of SCR Commutation** is the process of **Turning-OFF** an SCR using **Additional External Commutation Circuitry**. This commutation technique only occurs in **DC Circuit**. For better understanding, let us consider an **SCR circuit** energized from **DC source**. The two possibilities for current interruption are shown in **Fig (77)** and **Fig (78)** below.



- **Fig (77)** Shown a Series Interruption Technique in which Anode Current ( $I_a$ ) of SCR is interrupted to become Zero when the circuit Switch S is Opened.

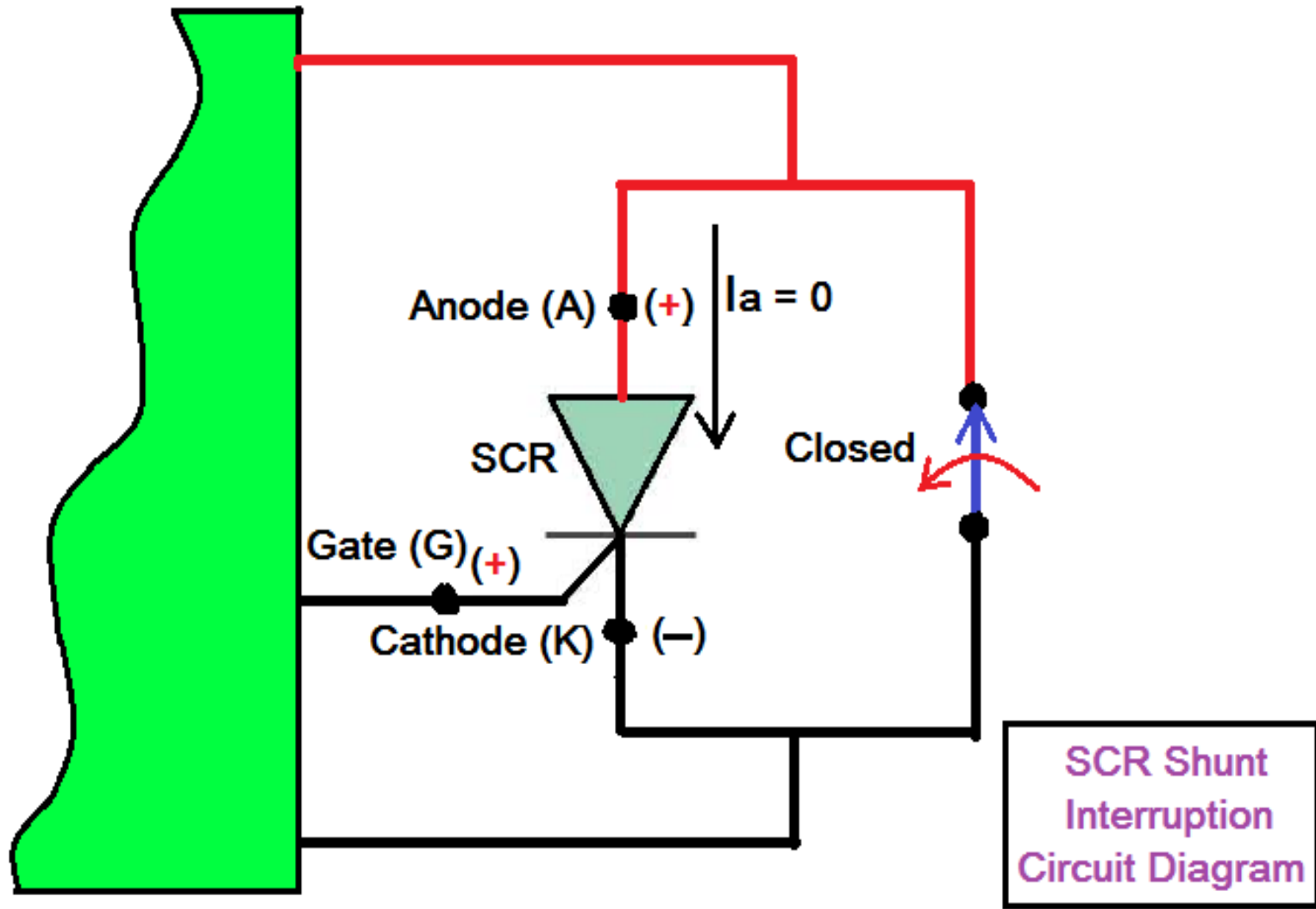
- In **Fig (77)** Shown, Anode Current ( $I_a$ ) of SCR is interrupted to make it to Zero when the circuit Switch S is Opened, called **Series Interruption Technique**. While in **Fig (78)**, the same condition is established when the circuit Switch S is Closed called **Shunt Interruption Technique**.



- Fig (78) Shown a Shunt Interruption Technique in which Anode Current ( $I_a$ ) of SCR is interrupted to become Zero when the circuit Switch S is Closed.

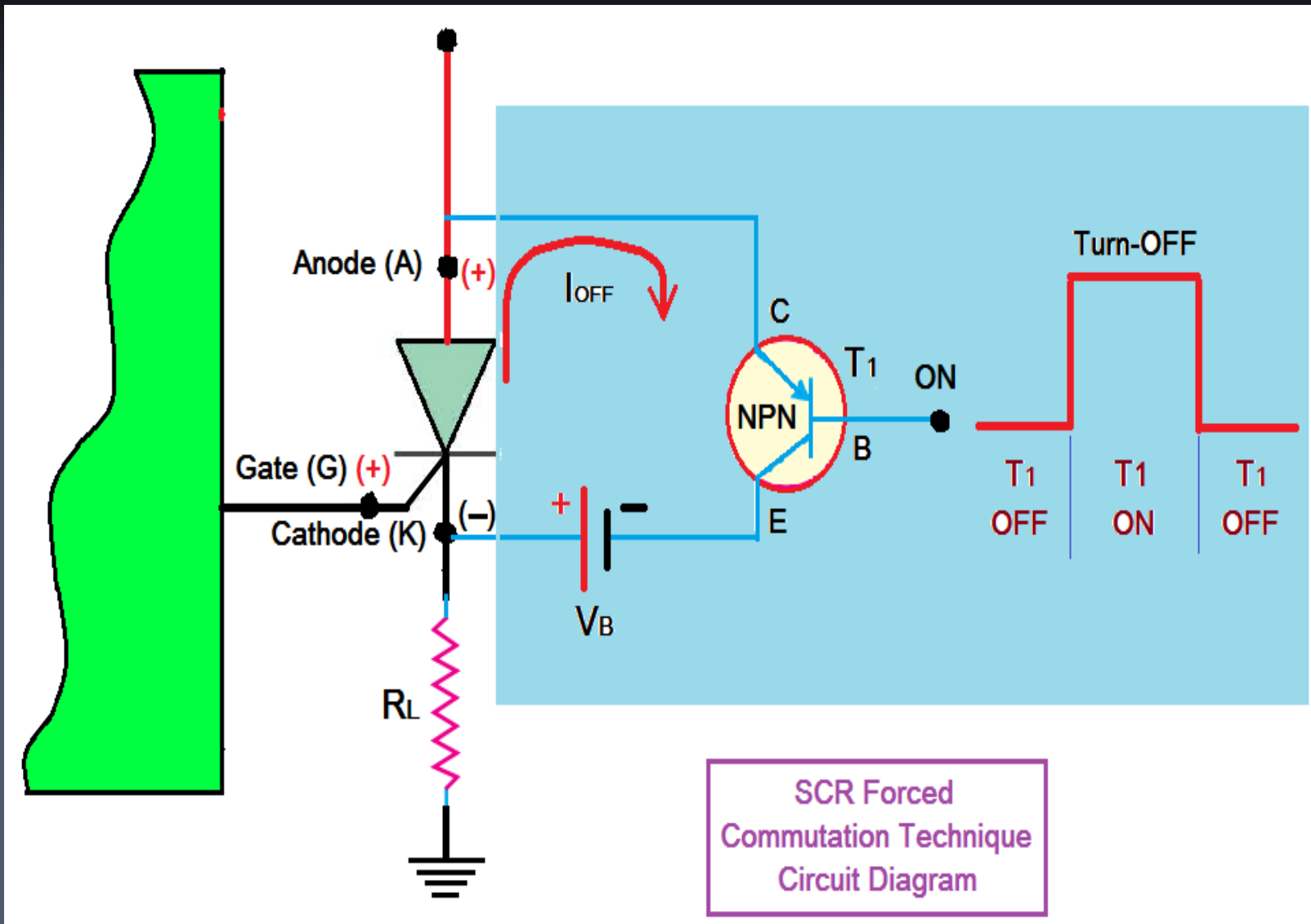
## (b) Basic Forced Commutation Technique

- **Forced Commutation** is the **Forcing** of current through the **SCR** is the direction opposite to **Forward Conduction**. There are wide varieties of circuits for performing this function. One of the most **basic types** is shown in **Fig (79)** below. As indicated in the **Fig (79)** below, the **Turn-OFF Circuit** consists of a **NPN Transistor**, a **DC Battery  $V_B$** , and a **Pulse Generator**. During **SCR Conduction**, the **Transistor** is in the **OFF-State** that is **Base Current  $I_B = 0$**  and the **Collector-to-Emitter Impedance is Very High** (for all practical purposes an open circuit).



- Fig (79) Shown a Basic Type of Force Commutation Circuit Diagram using NPN Transistor and a Battery.

- This **high impedance** will isolate the **Turn-OFF Circuitry** from affecting the operation of the **SCR**. For **Turn-OFF conditions**, a **Positive Pulse** is applied to the Base Terminal of the transistor, turning it heavily **ON**, resulting in very low impedance from **Collector-to-Emitter** (short circuit representation). The battery potential will then appear directly across the **SCR** as shown in **Fig (80)** below, forcing current through it in the **reverse direction** for **Turn-OFF**. Turn-OFF times of SCRs are typically **5 to 30 micro second**.

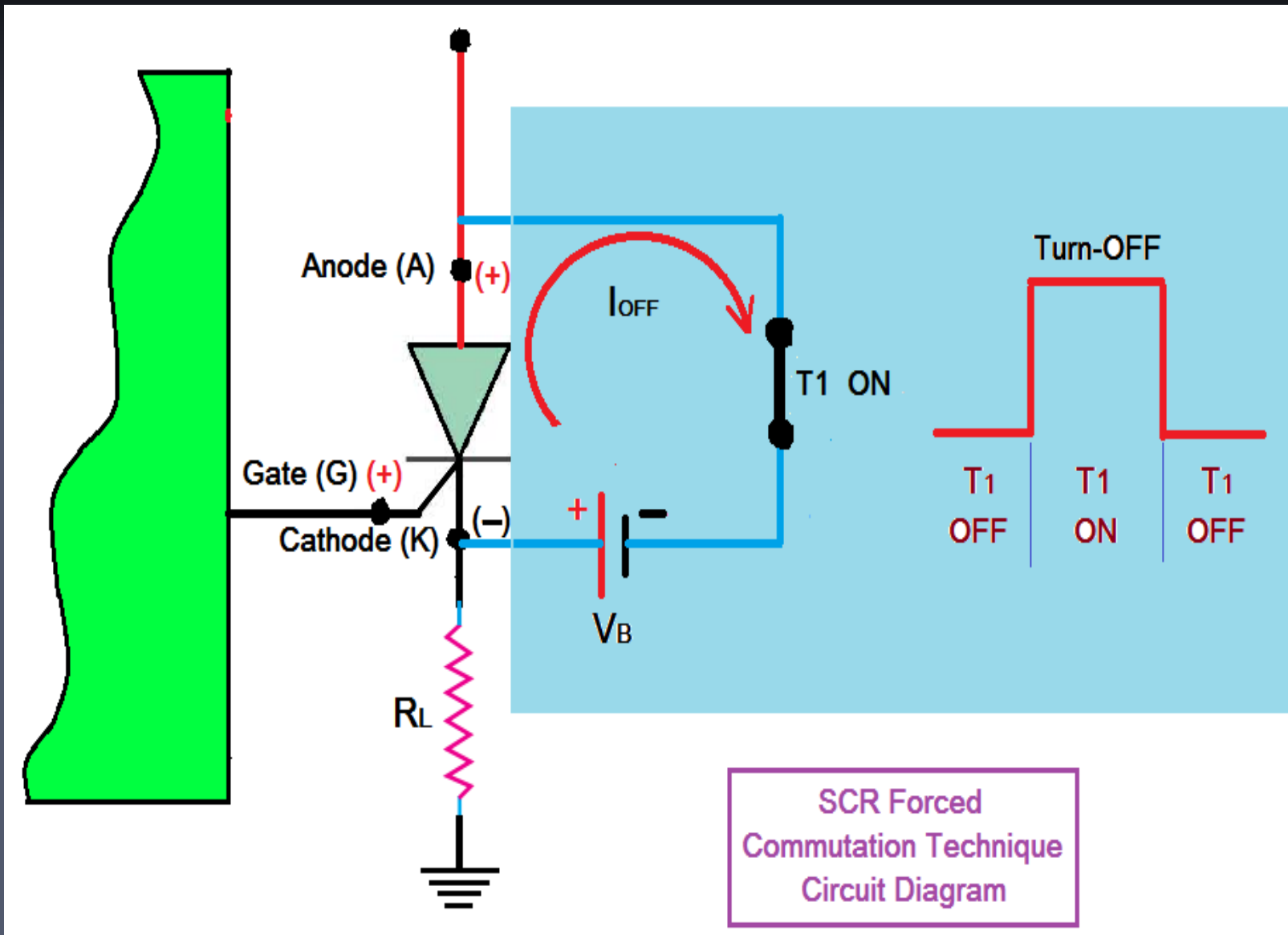

- **Fig (80)** Shown a Basic Type of Force Commutation Circuit Diagram using NPN Transistor and a Battery for applying Reverse Biasing across SCR.



**to be continued .....**