

# **Silicon Controlled Rectifier (SCR)**

## **Lecture – 17**

**TDC PART – I**

**Paper - II (Group - B)**

**Chapter - 5**

**by:**

**Dr. Niraj Kumar,**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,  
Muzaffarpur.**

# Silicon Controlled Rectifier (SCR)

## Lecture – 17

TDC PART – I

Paper - II (Group - B)

Chapter - 5


- **SCR Turning-OFF Methods (PART – 5)**
- **Lecture Content :-**
  - **(2) Forced Commutation**
  - **(II) Class-B Commutation - (also known as Resonant Pulse Commutation)**

## **(II) Class-B Commutation - (also known as Resonant Pulse Commutation)**

- **Class-B Commutation or Resonant Pulse Commutation is a Forced Commutation Technique to Turn OFF an SCR (thyristor). In this technique, SCR is Turned OFF by gradual build-up of Resonant Current in the Reverse Direction i.e. from Cathode to Anode of SCR. This technique is also known as Current Commutation and occurs in DC circuit not in AC circuit.**

- This is also a **Self Commutation** circuit in which commutation of **SCR** is achieved automatically by **L and C components**, once the **SCR (thyristor)** is **Turned ON**. The major difference between the **Class-A and Class-B SCR Commutation techniques** is that in case of **Class-B Commutation**, the **LC Resonant Circuit** is connected across (**Parallel**) the **SCR** but not in series with **Load Resistor (R)** as in case of **Class-A Commutation** and hence the **L and C components** do not carry the **Load Current ( $I_L$ )**.

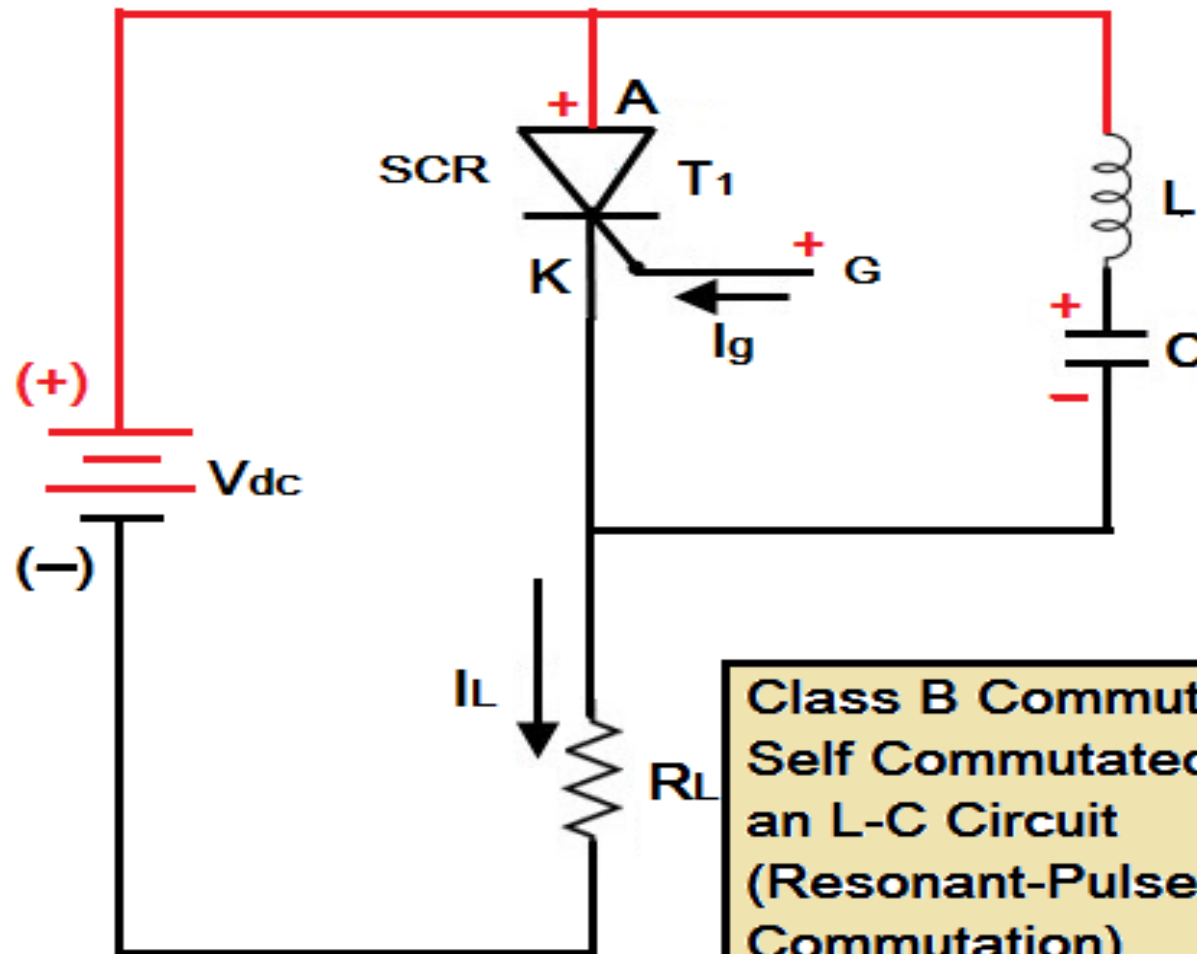- **Figure (86)** shows below the **Class-B Commutation circuit** which consist of **SCR (thyristor) T1** and **L-C circuit**. **Class-B Commutation** is a **Self-Commutation process** by an **L-C circuit**. The **L-C Resonating Circuit** is connected across the **SCR (thyristor)**. This circuit is also known as **Resonant Pulse Commutation**.



- **Fig (86) Shown Circuit Diagram of Class-B Commutation or Resonant-Pulse Commutation.**


- In **Class-B Commutation** circuit diagram shown in **Figure (86)** above, the **LC Resonant Circuit** is not directly connected with a load. It is connected **Parallel with the SCR**. Hence, the full **Load Current ( $I_L$ )** will not pass through the **SCR**. The circuit diagram of **Resonant-Pulse Commutation** is as shown in the **Figure (86)** above with waveforms of **SCR Current ( $I_{SCR}$ )**, **SCR Voltage ( $V_{SCR}$ )**, **Gate Current ( $I_g$ )** and **Load Current ( $I_L$ )** shown in **Figure (89)** below.

## MODE – 1 :-

- Initially the **Supply Voltage  $V_{dc}$**  is applied to the circuit  $t = 0$  and the **Capacitor Starts to Charge** and it finally charged to **Voltage  $V_{dc}$**  with **Upper Plate Positive** and **Lower Plate Negative**, shown in **Figure (87)** below. The **Charging of Capacitor** is done by **Capacitor Charging Current  $I_c$**  flowing through the following path,

$V_{dc+} - L - C+ - R_L - V_{dc-}$



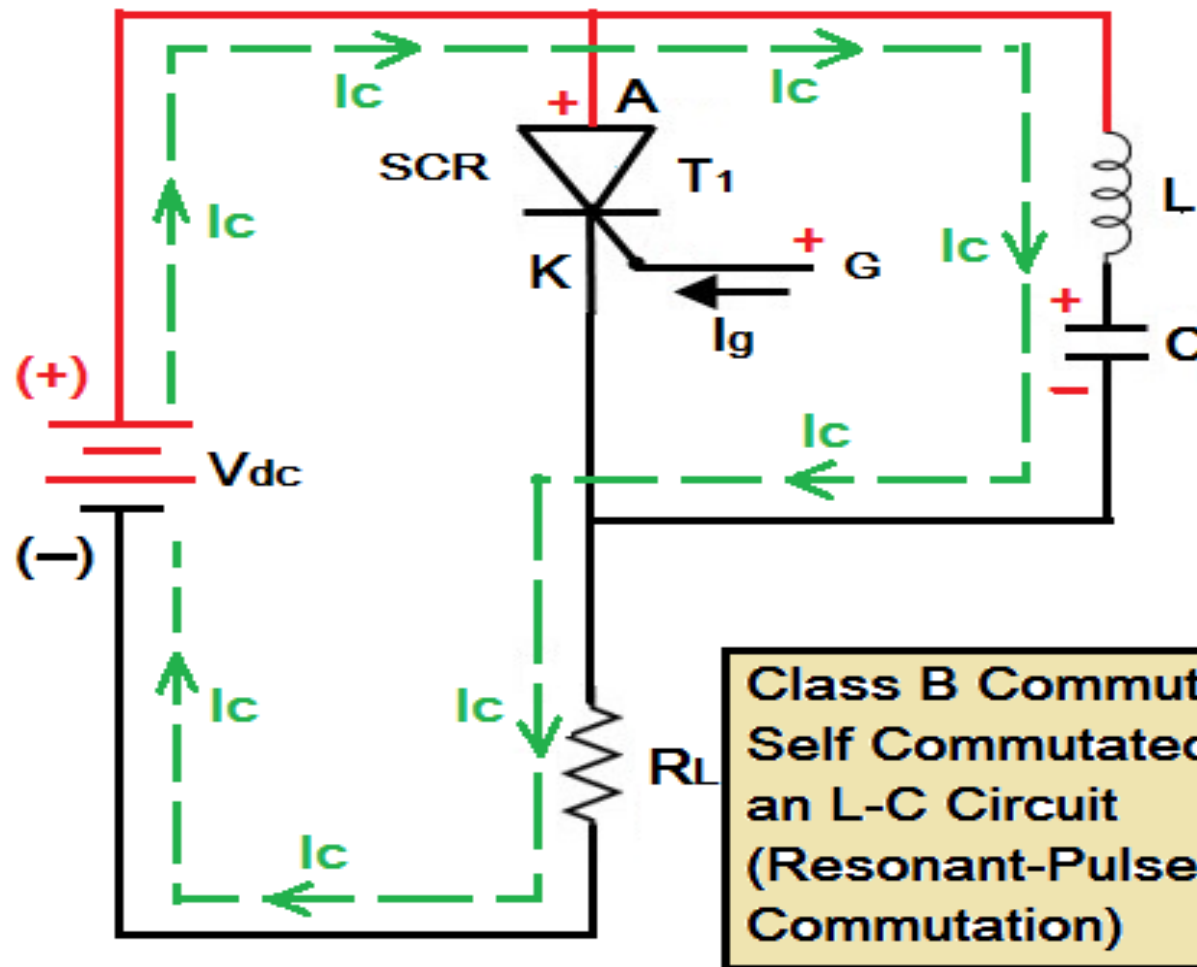

- Fig (87) Shown Class-B Commutation **MODE – 1** Condition of Capacitor Charging Current  $I_c$  .


## MODE – 2 :-

- When the **Gate Pulse** is applied to **SCR (thyristor) T1** at  $t = t_1$  than **SCR (thyristor) T1** will be **Turned ON**, a **Constant Load Current  $I_L$**  or **Anode Current  $I_A$**  flows through **Load  $R_L$**  and **Capacitor Discharging Current  $I_c$**  flows through **Capacitor  $C$**  which is shown in **Figure (88)** below. The **Load Current  $I_L$**  flowing through the following path,

$V_{dc+} - T_1 - R_L - V_{dc-}$

- And once the **SCR** is **Turned ON**, the **Capacitor (C)** is starts **Discharging** through the path,

$C+ - L - T_1 - C-$

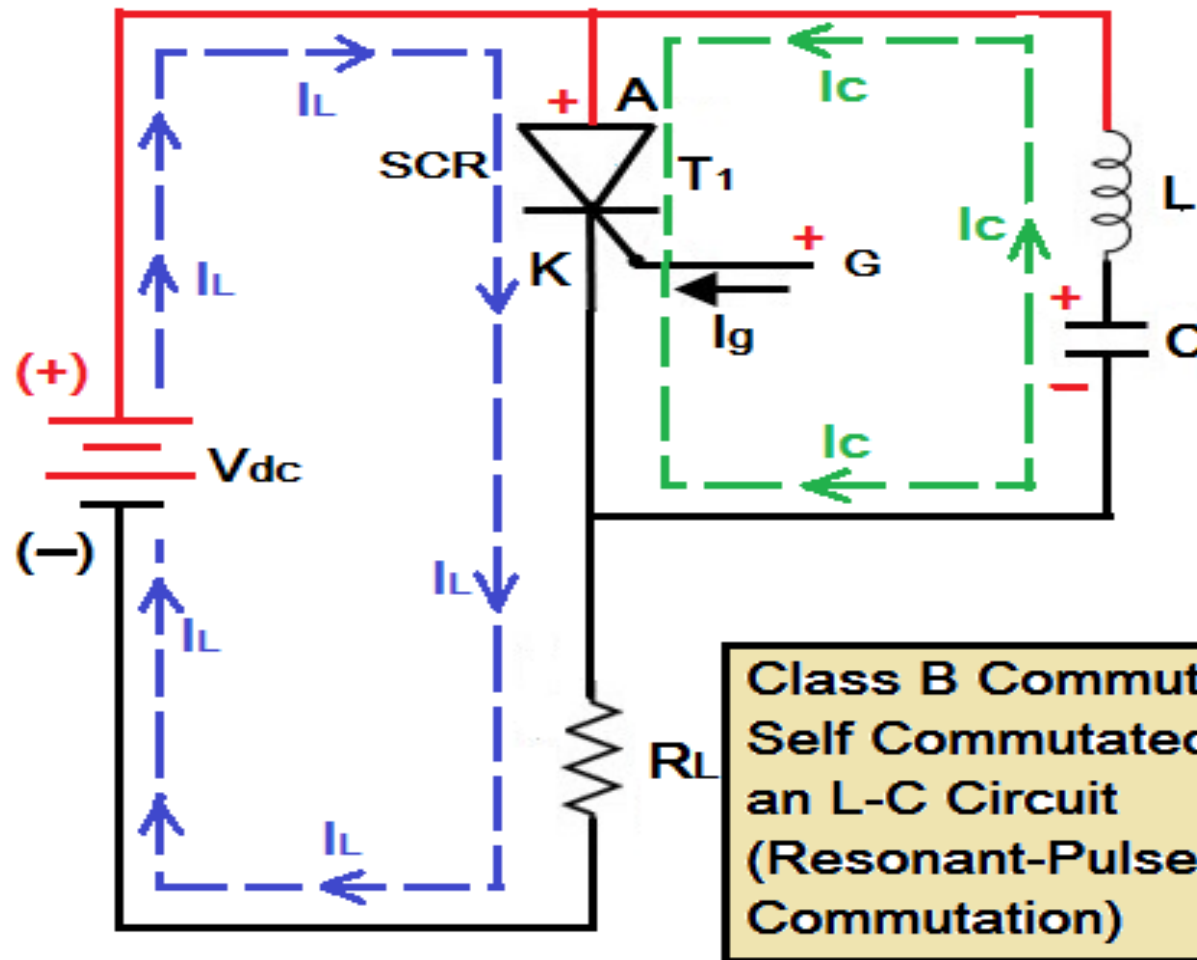

- **Fig (88)** Shown Class-B Commutation **MODE – 2** Condition of flowing of Load Current  $I_L$  and Capacitor Discharging Current  $I_c$  .

## MODE – 3 :-

- When the Capacitor **C** is completely discharged, it starts to charge with Reverse Polarity. Due to Reverse Polarity of capacitor voltage, the Commutating Current  $I_c$  opposes the flow of the Load Current  $I_L$  or Anode Current ( $I_A$ ). Since SCR (thyristor)  $T_1$  is a unidirectional device, the Net Current  $I_{T1}$  flows through SCR (Thyrisor)  $T_1$  is,


$$I_{T1} = I_L - I_c$$

- When the **Commutating Current ( $I_c$ )** is higher than the **Anode Current ( $I_A$ )** or **Load Current ( $I_L$ )** causes **Anode Current ( $I_A$ )** of **SCR** is decreases and when the **Anode Current ( $I_A$ )** is less than the  **Holding Current ( $I_H$ )** the **SCR** will automatically **Turn OFF** and the **Capacitor ( $C$ )** charges with original polarity.
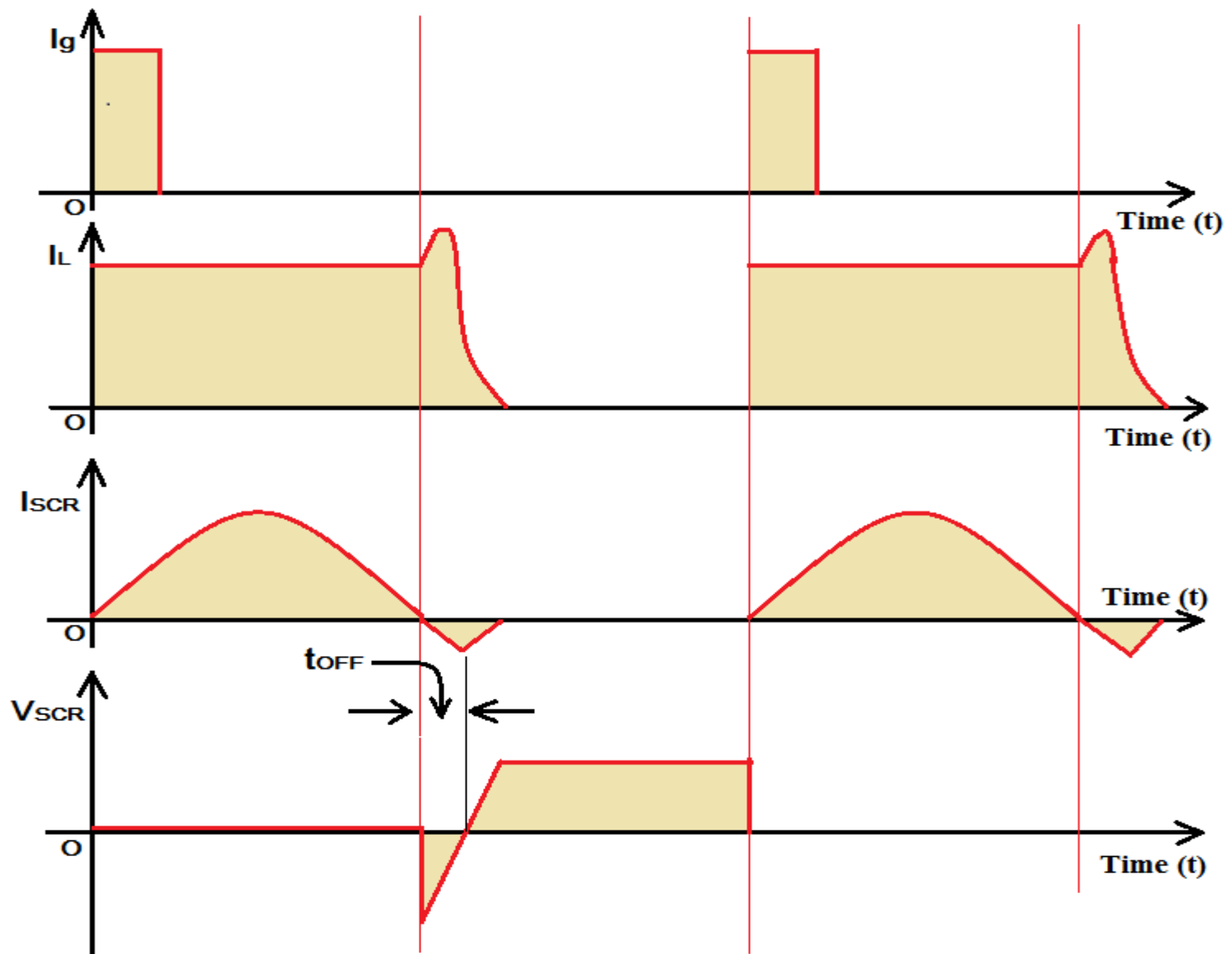
## **MODE – 4 :-**

- When SCR (thyristor) T<sub>1</sub> is Turned OFF, Capacitor C again starts to charge with Upper Plate Positive and Lower Plate Negative. Whenever Capacitor C is fully charged, SCR (thyristor) T<sub>1</sub> will operate in the Forward Blocking State and it will be Turned ON when a Trigger Pulse is applied to SCR (thyristor) T<sub>1</sub>.

- It is clear from Voltage and Current Waveforms of Class-B Commutation shown in **Figure (89)** below, that if the **SCR (thyristor) T1** is **Turned ON** by applying a **Gate Pulse** and **Loads Current  $I_L$  or Anode Current  $I_A$**  flows through **SCR (thyristor) T1** and load for certain specified time duration. After the specified time period, **SCR (thyristor) T1** will be **Turned OFF** due to **Self-Commutation**.



■ Fig (89) Shown Voltage and Current Waveforms of Class-B Commutation.



- In the above process, the **SCR is Turned ON** for some time and then **automatically Turned OFF for some time**. This is a continuous process and the **desired frequency of ON/OFF depends on the values of L and C**. This type of commutation is mostly used in **Chopper Circuits**.

**to be continued .....**