

Silicon Controlled Rectifier (SCR)

Lecture – 18

TDC PART – I

Paper - II (Group - B)

Chapter - 5

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L.S. College, BRA Bihar University,
Muzaffarpur.**

Silicon Controlled Rectifier (SCR)

Lecture – 18

TDC PART – I

Paper - II (Group - B)

Chapter - 5


- **SCR Turning-OFF Methods (PART – 6)**
- **Lecture Content :-**
 - **(2) Forced Commutation**
 - **(III) Class-C Commutation (often called Complimentary Commutation)**

(III) Class-C Commutation (often called Complimentary Commutation)

- The **Class-C commutation** circuit diagram is shown in **Figure (90)** below. In this method, the **Main thyristor (SCR T1)** that is to be **Commutated** is connected in **Series** with the **Load Resistor (RL)**. An additional thyristor (**SCR TA**), called the **Auxiliary or Complementary SCR (thyristor)** is connected in **Parallel** with the **Main thyristor (SCR T1)**.

- As **Figure (90)** shows below, the **Class-C Commutation Circuit Diagram** which consists of two **SCRs (Thyristors)** such as main **SCR (Thyristor) T₁** and **Auxiliary SCR (Thyristor) T_A** and a **Commutation Capacitor (C)**. The **Load Resistance R_L** is connected in **Series** with **Main SCR (Thyristor) T₁**.

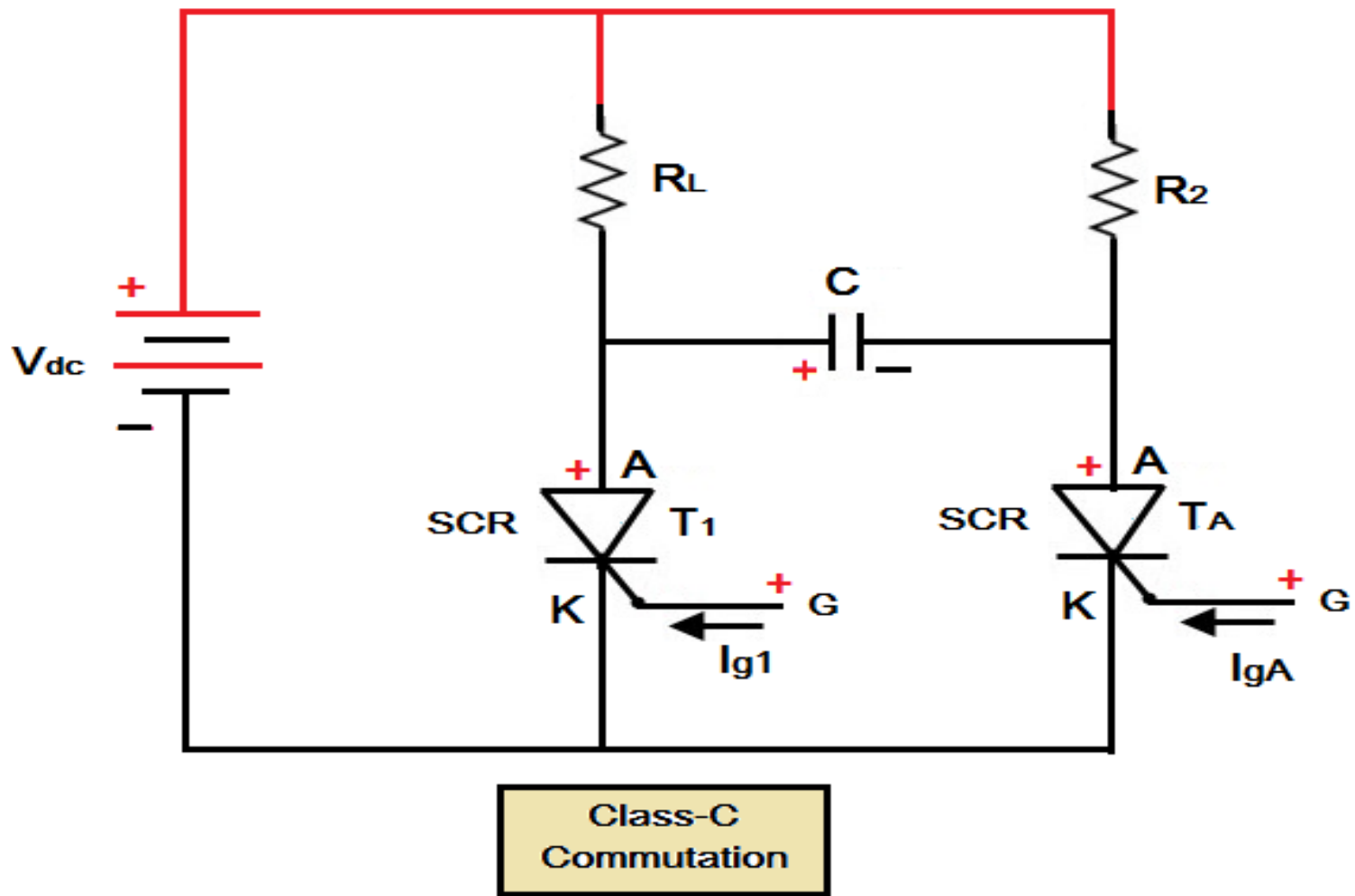- This **Class-C Commutation Technique** is also known as **Complementary Commutation** as the **commutation of Main SCR (Thyristor) T₁** occurs when the **Auxiliary SCR (Thyristor) T_A** is **Turned ON**. This **Class-C Commutation Process** is also known as **Complementary Impulse Commutation**.



- Fig (90) Shown the Class-C Commutation Circuit Diagram which consists of two SCRs and one Capacitor.

MODE - 0 :-

- Initially, both the **SCRs T1 and TA** are in **OFF State** and the **Voltage across Capacitor is Zero**.
The conditions of **SCR T1 and SCR TA** and **Capacitor (C)** may be represented by,
 - **T1 is in OFF State,**
 - **TA is in OFF State and**
 - **$V_C = 0$**

MODE - 1 :-

- When the **Triggering Pulse** is applied to the **Gate Terminal** of main **SCR T₁** at **$t = t_1$** , **SCR T₁** will be **Turned ON**. Therefore, two **Circuit Currents**, namely, **Load Current (I_L)** and **Capacitor Charging Current (I_C)** start flowing through the circuit.

■ The **Load Current (I_L)** follows through the following path :-


■ $V_{dc+} - R_L - T_1 - V_{dc-}$ and

■ the **Capacitor Charging Current (I_c)** flows through the path :-

■ $V_{dc+} - R_2 - C_+ - C_- - T_1 - V_{dc-}$

- At Steady State Condition, Capacitor (C) is fully charging to the Supply Voltage (V_{dc}) with the polarity as shown in **Figure (91)** below. The condition of SCR T1 and SCR TA and Capacitor (C) may be represented by,

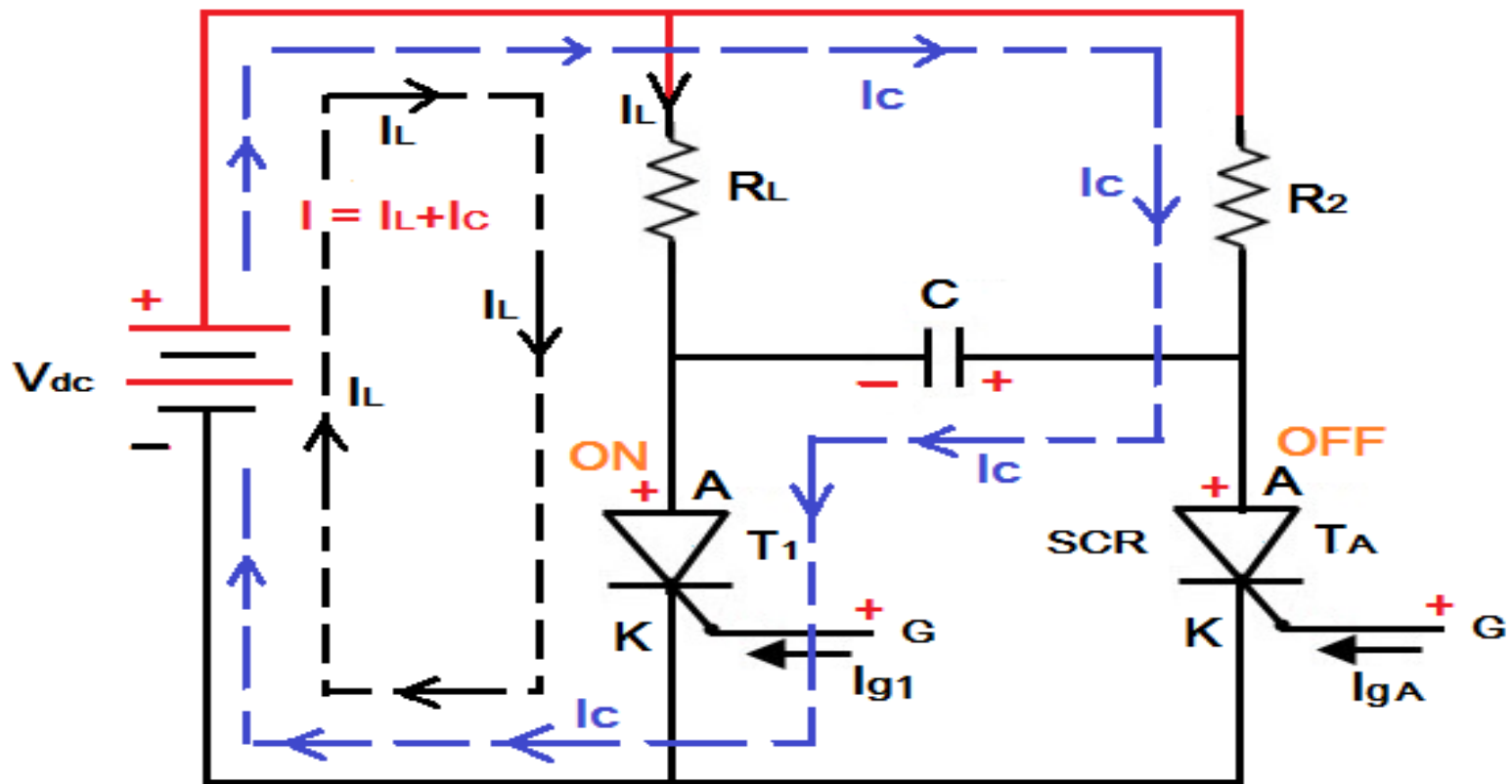- T1 is in ON State,
- TA is in OFF State and
- $V_C = V_{dc}$



Simplified Diagram
when SCR T_1 ON

- Fig (91) Shown the **Class-C Commutation** Simplified Circuit Diagram which consists of two SCRs and one Capacitor with SCR T_1 is in ON State and SCR T_A is in OFF State.


MODE - 2 :-

- When a **Triggering Pulse** is applied to **Auxiliary SCR T_A** at **$t = t_2$** , **SCR T_A** will be **Turned ON**.
As soon as **SCR T_A** is **Turned ON** and start **conducting**, a **Negative Polarity Voltage** of the **Capacitor (C)** is applied to **Anode (A)** of **SCR T₁** and simultaneously, the **Positive Polarity** of **Capacitor (C)** is applied to the **Cathode (K)**.
Subsequently, **SCR T₁** will be **Reverse Biased** and **Turned OFF** immediately.

- Therefore, the **Commutation of main SCR T₁** is possible by **Tuning ON** the **auxiliary SCR T_A**.
- Then the **Capacitor (C)** is charged through the load and its polarity becomes reverse. The **charging path of Capacitor (C)** is,
- $V_{dc+} - R_L - C_+ - C_- - T_{A(a-k)} - V_{dc-}$

■ At the end of this **MODE - 2 of Operation**, as shown in **Figure (92)** below the conditions of both **SCR T₁** and **SCR T_A** and **Capacitor (C)** may be represented by,

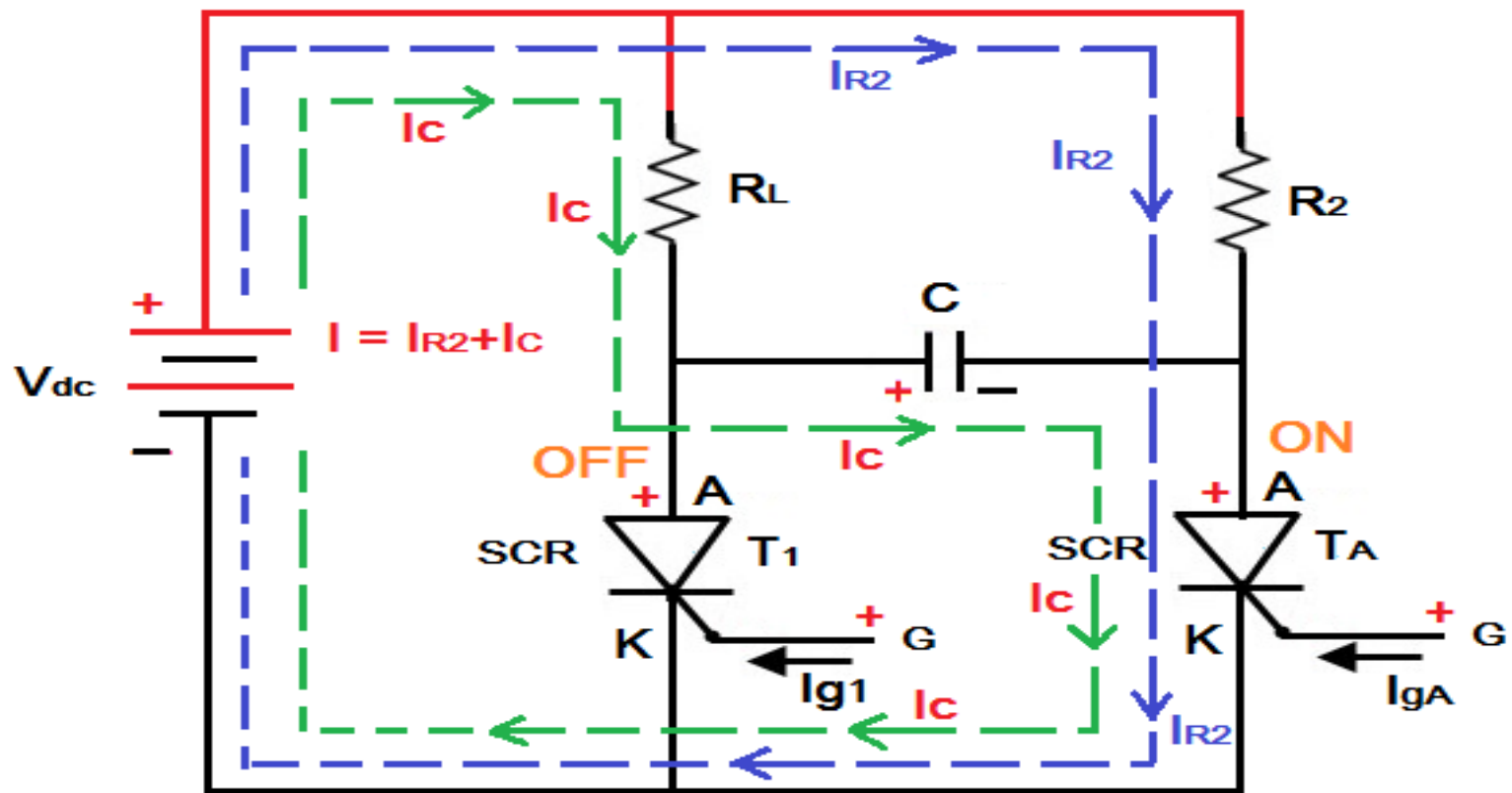- T₁ is in **OFF State**,
- T_A is in **ON state** and
- $V_C = -V_{dc}$




- Fig (92) Shown the Class-C Commutation Simplified Circuit Diagram which consists of two SCRs and one Capacitor with SCR T_1 is in OFF State and SCR T_A is in ON State.

MODE - 3 :-

- Again, when SCR T1 is Triggered and Turned ON at $t = t_2$. Then Auxiliary SCR TA will be Turned OFF immediately as Reverse Bias Voltage is applied across SCR TA and Capacitor (C) starts to charge in Reverse Direction. At the end of this MODE - 3 of Operations SCR T1 and SCR TA and Capacitor (C) may be represented by,
 - T1 is in ON State,
 - TA is in OFF State and
 - $V_C = V_{dc}$

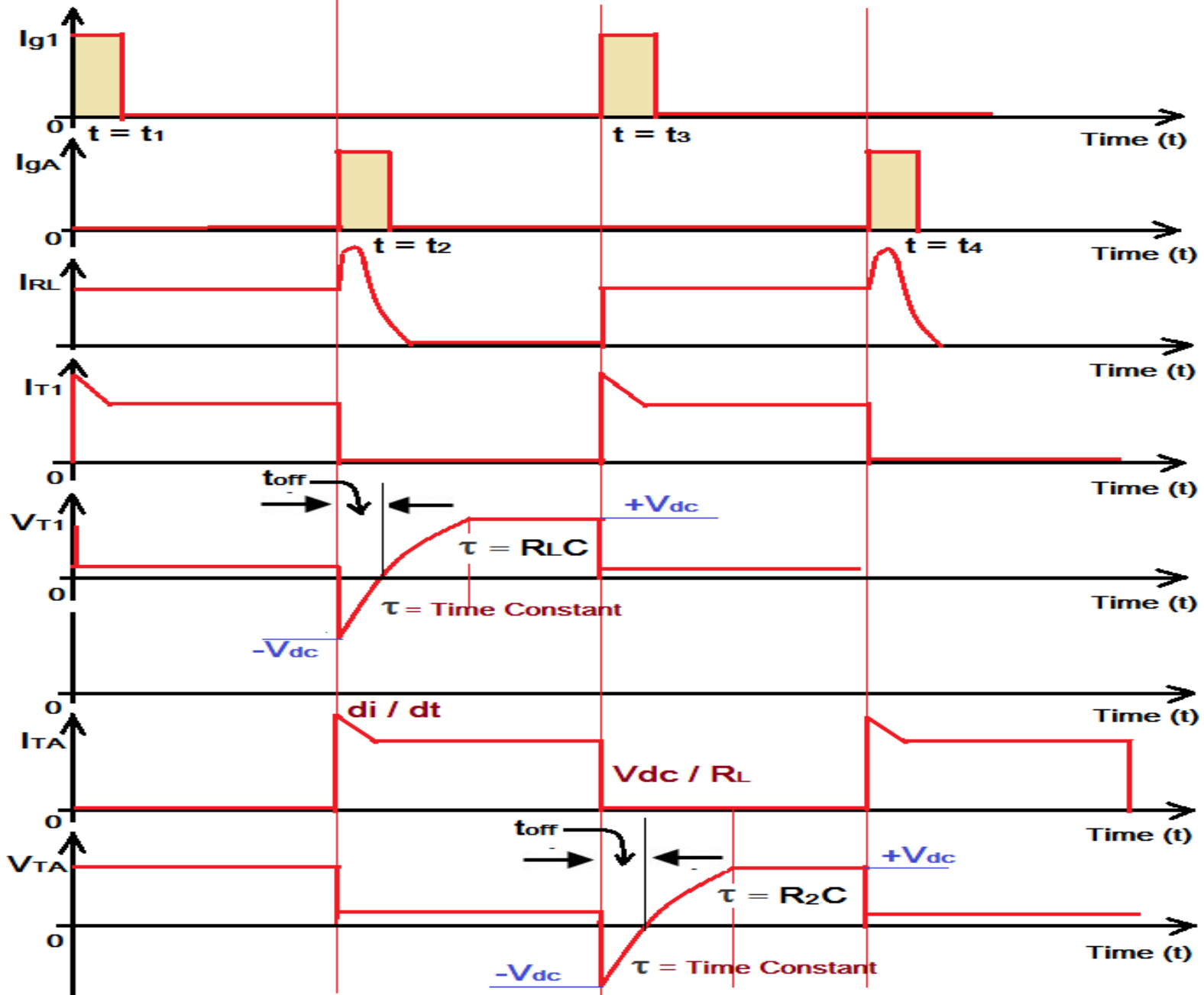- Therefore, this **MODE - 3 operations** is equivalent to **MODE - 1 operation**.
- The **Voltage and Current waveforms of Class-C Commutation** at the various points on the **Commutation Circuit** are shown in **Figure (93)** below.



■ Fig (93) Shown Voltage and Current Waveforms of Class – C Commutation

- This commutation is mainly used in **Single Phase Inverters** with a Centre Tapped Transformers. An example of this **Class-C of Commutation** is the well known **Mc Murray-Bedford Inverter**. With the aid of certain accessories, the **Class- C Commutation** is very useful at **Operating Frequencies below about 1000 Hz (1kHz)** and therefore this commutation technique is used in **Inverter**. The **Characteristics of Class-C Commutation** are **Sure and Most Reliable Commutation**.

to be continued