

Waveform Generation

Lecture - 17

(30/04/2021)

B.Sc (Electronics)

TDC PART - III

Paper – 6

Unit – 8

by:

Dr. Niraj Kumar

Assistant Professor (Guest Faculty)



Department of Electronics

L. S. College, BRA Bihar University, Muzaffarpur.

➤ **Transistor Bi-Stable Multivibrator Circuit Operation (PART – 3)**

The operation of the Bi-stable Multivibrator (BMV) circuit illustrated in Fig (3), (4) and (5) is as follows:-

When the **BMV Power supply $+V_{CC}$** is **switched ON** by closing the **Switch S**, both **Transistors Q1 and Q2 start conducting**. Then one transistor starts conducting slightly more than the other due to small differences in their operating characteristics of the transistors. This starts a series of events.

Assume arbitrarily that **Transistor Q1** initially **Conducts (ON)** more than **Transistor Q2**. This causes the **Collector voltage** of **Transistor Q1** to drop more rapidly than that of **Transistor Q2**.

If **Transistor Q1** is **Conducting (ON)**, then the fact that **Point A** is nearly **0 V** makes the **Base terminal** of **Transistor Q2** **negative** by the **Potential divider R₂ – R₄**. The resulting negative signal is fed to the **Base terminal** of **Transistor Q2** through **Resistor R₂** and drives it towards **Cut-OFF** and **HOLD Transistor Q2 Cut-OFF**.

As a result the **Collector voltage** of **Transistor Q2** rises towards **+V_{CC}**. This change in **Collector voltage** of **Transistor Q2** is fed to the **Base terminal** of **Transistor Q1** through **Resistor R₁**.

Similarly, with **Transistor Q2 Cut-OFF**, the **Potential divider R₁ – R₃** is designed to keep **Base terminal** of **Transistor Q1** at about **0.7 V**. It is ensuring that **Transistor Q1** to go into **Saturation (ON)**. So **Transistor Q1** will remain in **Saturation (ON)** and **Transistor Q2** in the **Cut-OFF (OFF)** condition.

Interestingly it is seen that **Transistor Q1** in **Saturation (ON)** and **HOLD Transistor Q2 Cut-OFF (OFF)** and **Transistor Q2** in **Cut-OFF (OFF)** and **HOLD Transistor Q1** in **Saturation (ON)**. This drives one **Transistor Q1** to the **Saturation (ON)** and the other **Transistor Q2** to the **Cut-OFF (OFF)**. **This is the First Initial Stable State of the Bi-stable Multivibrator** which is shown below in **Figure (3)**.

- **The above whole process can be understood in a different way, which is as follows:-**

When the **BMV power supply** $+V_{CC}$ are **Switched ON** by closing the **Switch S** of the circuit, currents in **Transistor Q1** and **Q2** begin to flow. And due to the difference in characteristics of the transistors, current in one is slightly larger than the other.

Suppose I_{C1} of the **Transistor Q1**, is larger than I_{C2} of the **Transistor Q2**. Larger I_{C1} will **reduce the voltage** of **Point A**, which in consequence **reduce** the **Base voltage** of **Transistor Q2**, and hence **decrease** in I_{C2} of the **Transistor Q2**.

Due to **decrease** in I_{C2} voltage of **Point B** will be **increased**, which will **increase** the **Base terminal voltage** of **Transistor Q1**, thereby further **increase** in I_{C1} . Ultimately **Transistor Q1** will be conducting at **Saturation (ON)** and **Transistor Q2** is in **Cut-OFF (OFF)**. On the other hand if initially I_{C2} is larger than I_{C1} , then finally **Transistor Q2** will be conducting at **Saturation (ON)** and **Transistor Q1** will be in **Cut-OFF (OFF)**.

If **Transistor Q1** is **Conducting (ON)**, then the **Potential (voltage)** of **Point A** is nearly **zero**. The **Negative supply** $-V_{BB}$ **reverse biases** the **Base-Emitter junction** of **Transistor Q2** by the **potential divider bias** through **Resistors R_2 and R_4** , so **Transistor Q2** is in **Cut-OFF (OFF) condition**, and thus the potential of **Point B** is $+V_{CC}$. Thus **Transistor Q1** is **forward bias** through the **Potential divider bias** from $+V_{CC}$ to $-V_{BB}$ ($R_1 - R_3$). So **Transistor Q1** will remain in **Saturation (ON)** and **Transistor Q2** in the **Cut-OFF (OFF) condition**.

Interestingly it is seen that **Transistor Q1** in **Saturation (ON)** and **HOLD Transistor Q2** in **Cut-OFF (OFF)** and **Transistor Q2** in **Cut-OFF (OFF)** and **HOLD Transistor Q1** in **Saturation (ON)**. This drives one **Transistor Q1** to the **Saturation (ON)** and the other **Transistor Q2** to the **Cut-OFF (OFF)**. **This is the**

First Initial Stable State of the Bi-stable Multivibrator which is shown below in

Figure (3).

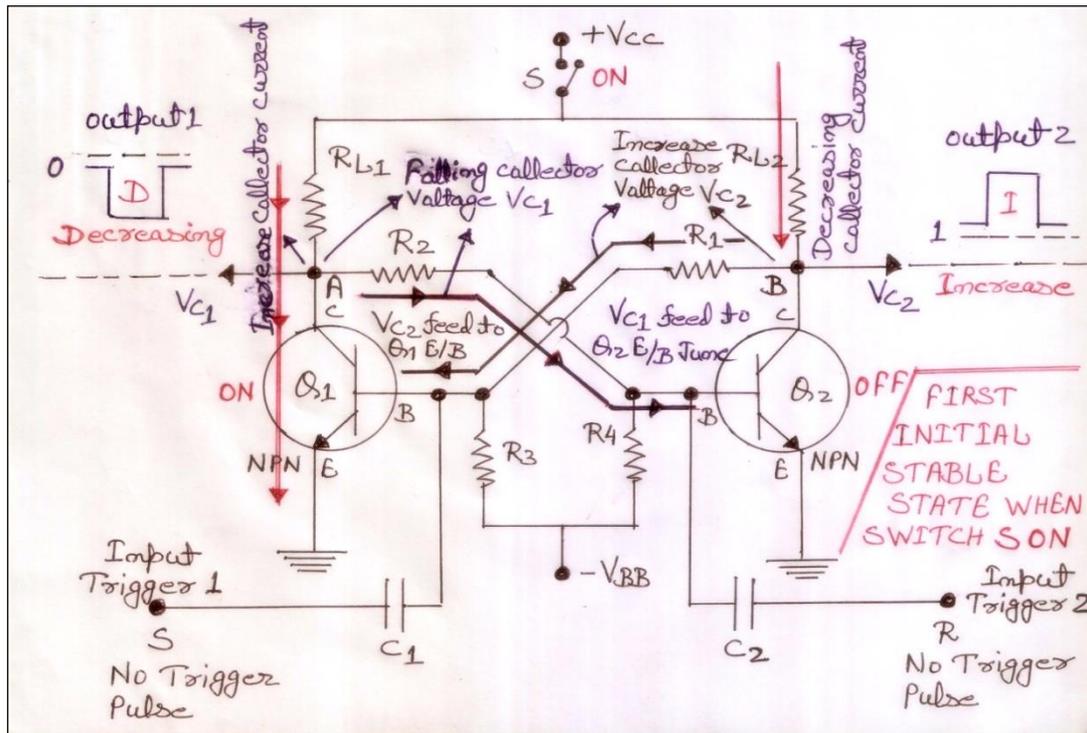


Fig. (3) Shown First Initial stable State of the Multivibrator when BMV Power Switch 'S' ON and No Trigger Inputs applied.

The **Bi-stable Multivibrator** can be driven from the **First Stable State** (Q1 **ON** and Q2 **OFF**) to the **other stable state** (Q1 **OFF** and Q2 **ON**) by applying either a **negative trigger pulse** to the **Base terminal** of Transistor Q1 through **Input Trigger 1 (SET)** or a **positive trigger pulse** to the **Base terminal** of Transistor Q2 through **Input Trigger 2 (RESET)**.

By applying a **negative trigger** at the **Base terminal** of Transistor Q1 or by applying a **positive trigger pulse** at the **Base terminal** of Transistor Q2, this **stable state** can be altered.

So, let us understand this by considering a **negative trigger pulse** at the **Base terminal** of Transistor Q1 through **Input Trigger 1 (SET)**.

Let a **negative trigger pulse** of short duration and sufficient magnitude be applied to the **Base terminal** of Transistor Q1 through Capacitor C1. This **negative trigger pulse reduces** the **forward bias** on the Transistor Q1 Base terminal hence it **reduces** the E/B junction voltage of Transistor Q1 then Transistor Q1 **Cut-OFF (OFF)** and causes a **reduction** in Transistor Q1 Collector current and, thereby, **increases** in Collector voltage V_{C1} of its collector terminal of Transistor Q1 at Point A.

Now this **increased** Collector voltage V_{C1} feed to E/B junction of Transistor Q2. The **rising** collector voltage appears across the **Emitter-Base (E/B) junction** of Transistor Q2 as it is connected to the **Collector terminal** of Transistor Q1 at Point A via Resistor R2. As **rising** Collector voltage of Transistor Q1, result Transistor Q2 **Saturated (ON)**, then collector current of Transistor Q2 **increases** and, therefore, its Collector voltage V_{C2} **decreased**.

The **decreasing** Collector voltage V_{C2} at Point B of the Transistor Q2 appears across the **Emitter-Base (E/B) junction** of Transistor Q1 through Resistor R1 where it **further Reverse Biases** the Emitter-Base (E/B) junction of Transistor Q1 to make Transistor Q1 **Cut-off (OFF)** then Collector current of Transistor Q1 to **decrease** and Collector voltage V_{C1} of Transistor Q1 to **increase** at Point A. After few cycles, the Transistor Q2 is driven into **Saturation (ON)** and Transistor Q1 to **Cut-OFF (OFF)**. This is the **Second Stable State** of the Bi-stable multivibrator. The circuit will now **remain in this Second Stable State (Q1 OFF and Q2 ON)**. **Second Stable State** when **negative trigger pulse** applied to the Transistor Q1 through **Input Trigger 1** is shown below in **Figure (4)**.

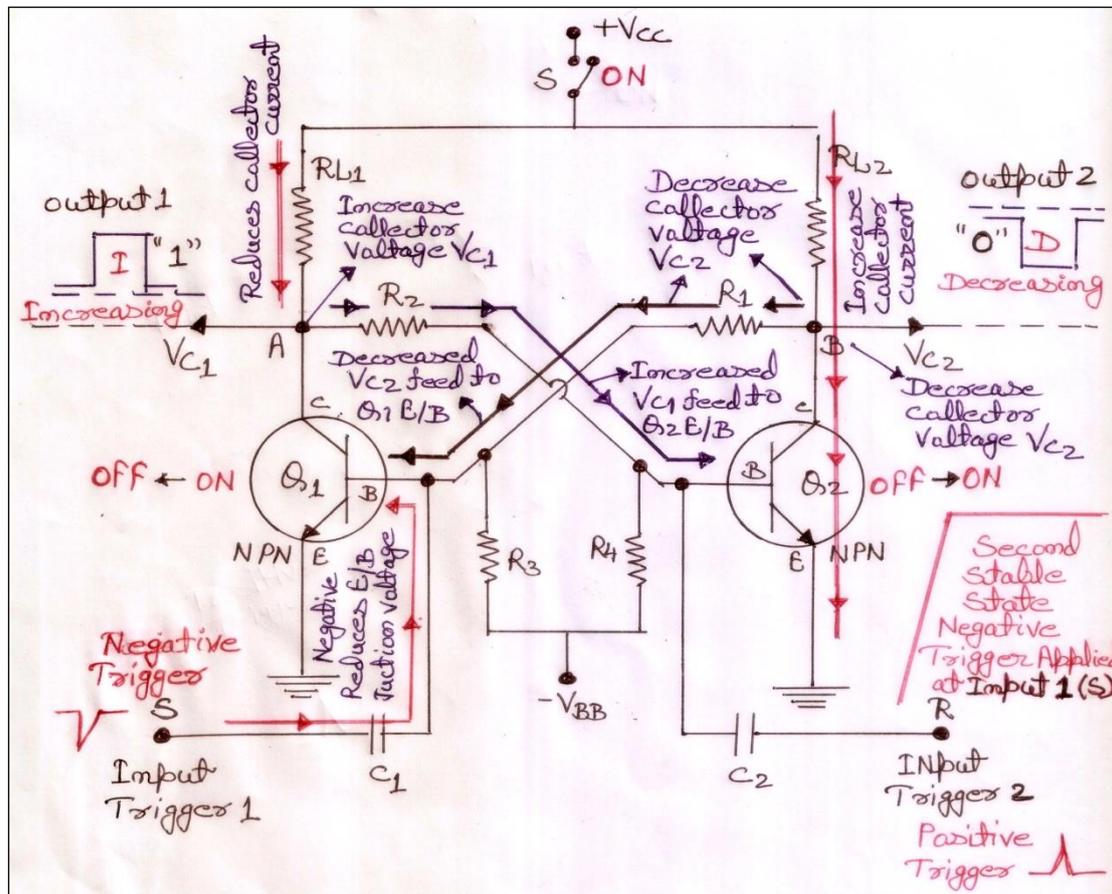


Fig. (4) Shown Second stable state when negative trigger pulse applied to the transistor Q1 through Input 1 or Positive trigger pulse applied to the transistor Q2 through Input 2.

Now, if this **Second Stable State** has to be changed again, and back to **Initial Stable State** where Transistor Q1 **Saturation (ON)** and Transistor Q2 **Cut-OFF (OFF)**, then a negative trigger pulse is applied to the Base terminal of Transistor Q2 through Input Trigger 2 or a positive trigger pulse is applied to the Base terminal of Transistor Q1 through Input Trigger 1. The above condition is shown below in Figure (5).

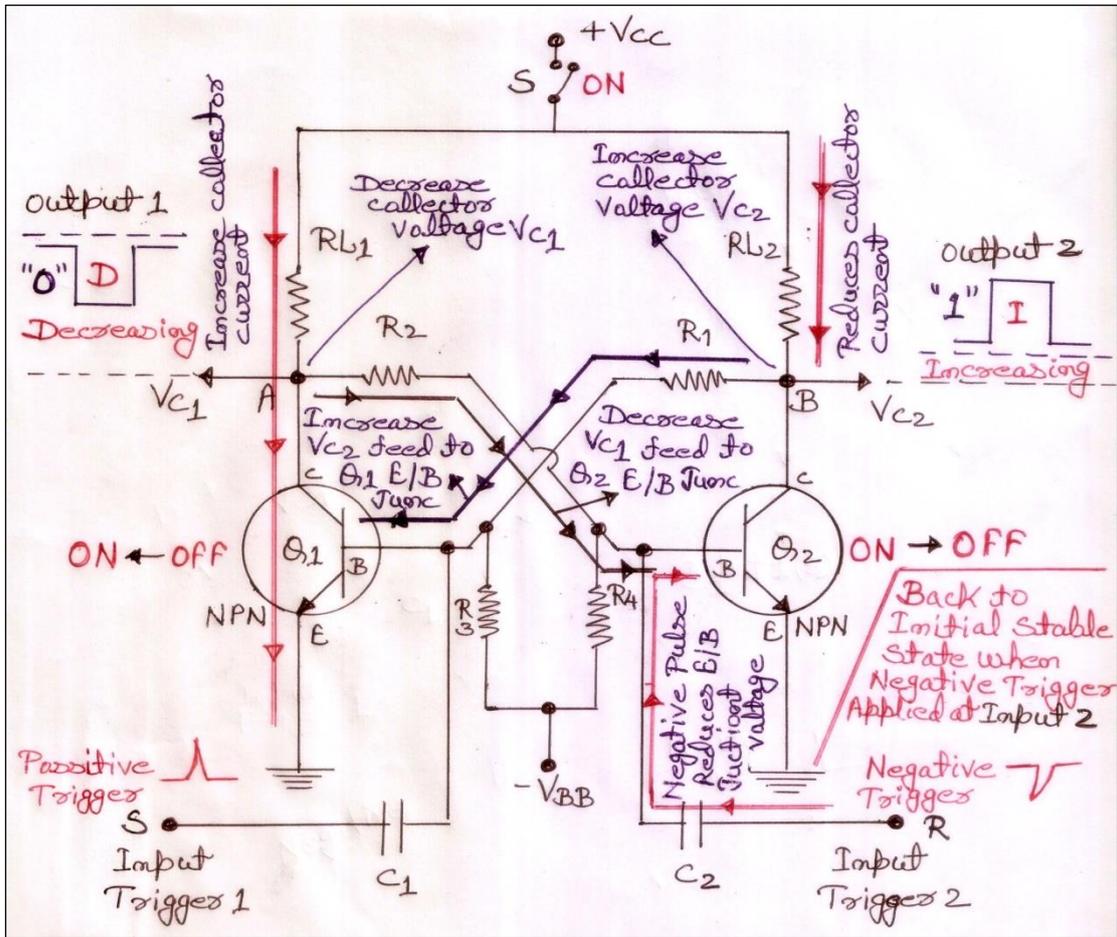


Fig. (5) Shown Back to initial stable state of BMV can be achieved when negative trigger pulse applied to the transistor Q2 through Input 2 or Positive trigger pulse applied to the transistor Q1 through Input 1.

⇒ Detailed of the Transistor Bi-Stable Multivibrator Output Waveforms, Its Advantage, Disadvantage and Applications are discussed in next **Lecture – 18**.

to be continued
