

Uni-Junction Transistor (UJT)

Lecture – 3

TDC PART – I
Paper – I (Group – B)
Chapter - 8

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L.S College, BRA Bihar University,
Muzaffarpur.**

(4) Theory of UJT Operation

- Initially imagine that the emitter supply voltage is turned down to zero then V_E is zero. Then the intrinsic stand-off voltage, reverse-biases the emitter diode. If V_D is the barrier voltage of the emitter diode, hence some reverse current I_E flows until, the value of V_E reaches a point at which

$$V_E = \eta V_{BB}$$

- This is the point where the curve touches the Y-axis then the total reverse bias voltage V_E is

$$V_E = V_A + V_D$$

- When V_{BB} is switched on, V_A is developed and *reverse-biases the junction*. If (silicon diode forward voltage drop) V_D is the barrier voltage of the **P-N junction**, then total reverse bias voltage is

$$V_E = V_A + V_D$$

From equation (5) $V_A = \eta V_{BB}$, then we get

$$V_E = \eta V_{BB} + V_D$$

Value of V_D for Si is 0.7 V.

$$V_E = \eta V_{BB} + V_D$$


$$V_E = \eta V_{BB} + 0.7V$$

- It is obvious that emitter junction will not become forward-biased unless its applied voltage V_E exceeds

$$V_E = (\eta V_{BB} + V_D) \text{ or}$$

$$V_E = \eta V_{BB} + 0.7V$$

- This value of V_E is called **peak-point voltage V_P** which is **shown in Fig. (7) and (8)**. When $V_E = V_P$, emitter (peak current), I_P starts to flow through R_{B1} to ground (*i.e.* B_1). The UJT is then said to have been **Fired or Turned ON**. Due to the flow of $I_E (= I_P)$ through R_{B1} , number of charge carriers in R_{B1} is increased which **reduces its resistance**. As η depends on R_{B1} , its value is also decreased.

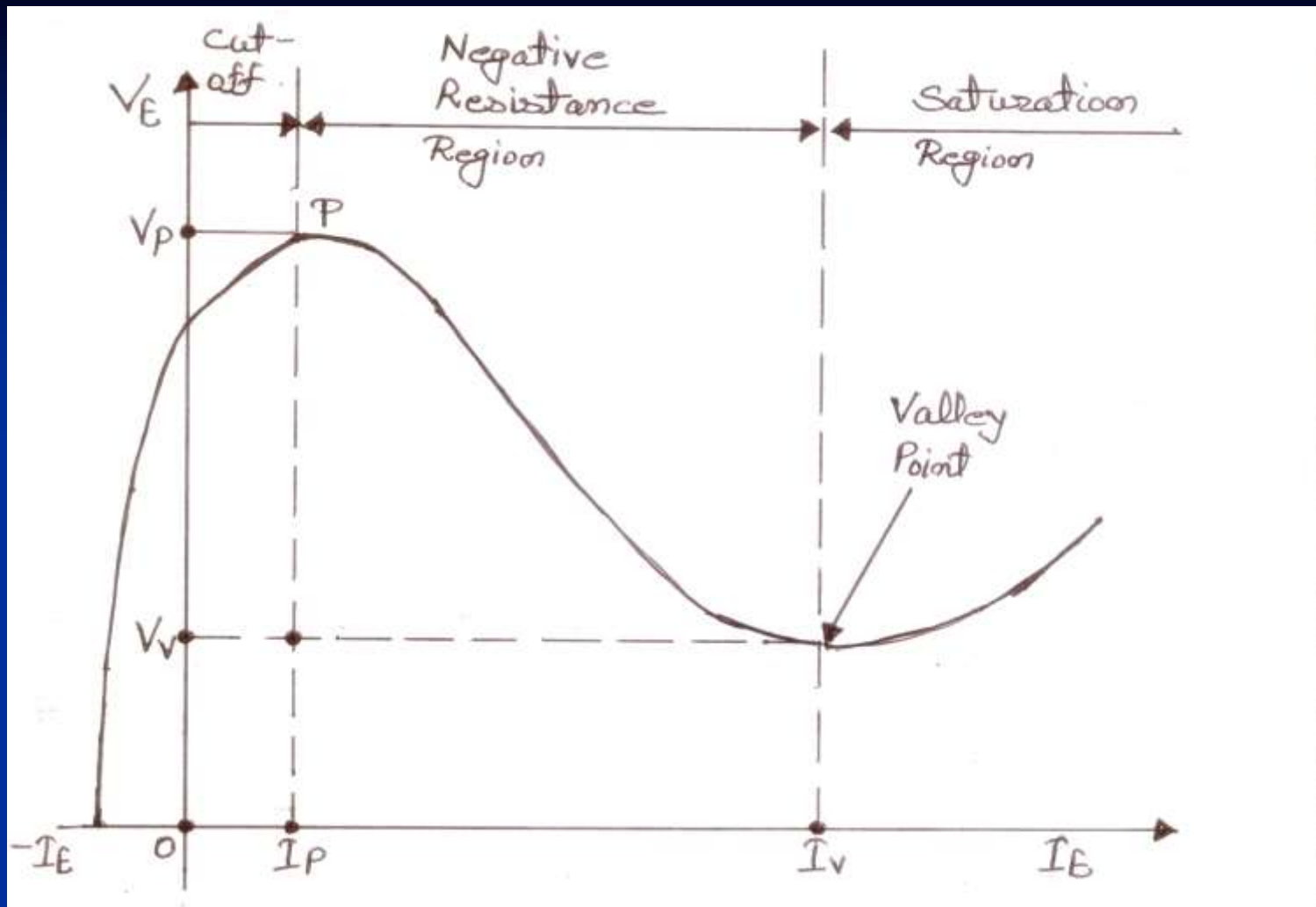

■ Fig. (8) Shown V-I Characteristics of UJT with Negative Resistance.

- Hence, we find that as V_E and hence I_E increases (beyond I_P), R_{B1} decreases, η decreases and V_A decreases. This decrease in V_A causes more emitter current to flow which causes a further reduction in R_{B1} , η and V_A . Obviously, the process is **regenerative**, V_A as well as V_E quickly drop as I_E increases. Since, V_E decreases when I_E increases, the **UJT Possesses Negative Resistance**. Beyond the valley point V_V , UJT is in **Saturation Region** and V_E increases very little with an increasing I_E . It is seen that only terminals **E** and **B₁** are the active terminals whereas **B₂** is the bias terminal *i.e.* it is meant only for applying external voltage across the UJT.

- Generally, **UJT** is triggered into conduction by applying a suitable positive pulse at its **Emitter Terminal E**. It can be brought back to **OFF** state by applying a **negative trigger pulse**. Three other important parameters for the **UJT** are **I_P** , **V_V** and **I_V** and are defined below:

- (1) **Peak-Point Emitter Current (I_P)** :- It is the emitter current at the peak point. It represents the minimum current that is required to trigger the device (UJT). It is inversely proportional to the inter-base voltage **V_{BB}** .
- (2) **Valley Point Voltage (V_V)** :- The valley point voltage is the emitter voltage at the valley point. The valley voltage increases with the increase in inter-base voltage **V_{BB}** .
- (3) **Valley Point Current (I_V)** :- The valley point current is the emitter current at the valley point. It increases with the increase in inter-base voltage **V_{BB}** .

(5) Special Features of UJT

■ The special features of a UJT are:-

- (1) A stable triggering voltage (**VP**)
- (2) Highly Stable Reliable Operation
- (3) Low Power Consumption
- (4) Easily Accessible and Cheap
- (5) A very low value of triggering current.
- (6) A high pulse current capability.
- (7) A negative resistance characteristic.
- (8) Low cost.

(6) Advantage of UJT

- (1) It is a Low cost device. The low cost per unit, combined with its unique characteristic, have warranted its use in a wide variety of applications.
- (2) It has excellent Negative Resistance characteristics.
- (3) UJT device has-a unique characteristic that when it is triggered, its emitter current increases regenerative (due to negative resistance characteristic) until it is restricted by emitter power supply.
- (4) It is a low-power absorbing device under normal operating conditions.

(7) UJT Applications

- One unique property of UJT is that it can be triggered by (or an output can be taken from) **any one of its three terminals**. Once triggered, the emitter current I_E of the UJT increases **regeneratively (By Regenerative Process)** till it reaches a limiting value determined by the external power supply.
- UJTs are most prominently used as relaxation oscillators. They are also used in Phase Control Circuits. In addition, UJTs are widely used to provide clock for digital circuits, timing control for various devices, controlled firing in thyristors, and sync pulsed for horizontal deflection circuits in CRO.


- Because of this particular behaviour, UJT is used in a variety of circuit applications. Some of which are:
 - 1) Phase control
 - 2) Switching
 - 3) Pulse generation,
 - 4) Sine wave generator
 - 5) To generate non sinusoidal oscillations.
 - 6) Sawtooth generator
 - 7) Timing and trigger circuits,
 - 8) Voltage or current regulated supplies.
 - 9) It can be used as trigger device for SCR's and TRIAC's.
 - 10) UJT widely used in electronic beepers, SMPS, inverters, blinkers,
 - 11) UJT widely used in voltage controlled oscillators.

(8) UJT Application as a Relaxation Oscillator

- An oscillator is a device that produces a waveform by its own, without any input. Though some dc voltage is applied for the device to work, it will not produce any waveform as input. A relaxation oscillator is a device that produces a non-sinusoidal waveform on its own. This waveform depends generally upon the charging and discharging time constants of a capacitor in the circuit. This non-sinusoidal waveform produced by UJT Relaxation Oscillator also known as Sawtooth waveform.

Construction and Working

- The **emitter E** of UJT is connected with a **resistor R1** and **capacitor C** as shown in Fig (9) below. The **R1C time constant** determines the timings of the output waveform of the relaxation oscillator. Here the **bases B1** are connected with a resistor **R2**. The **dc voltage supply VBB** is given. The **fig (9)** which is shown in next slide, shows how to use a UJT as a relaxation oscillator.
- Initially, the voltage across the **capacitor C** is zero.
 $V_C = 0$
- The UJT is in **OFF condition**. The **resistor R1** provides a path for the **capacitor C** to charge through the voltage applied.

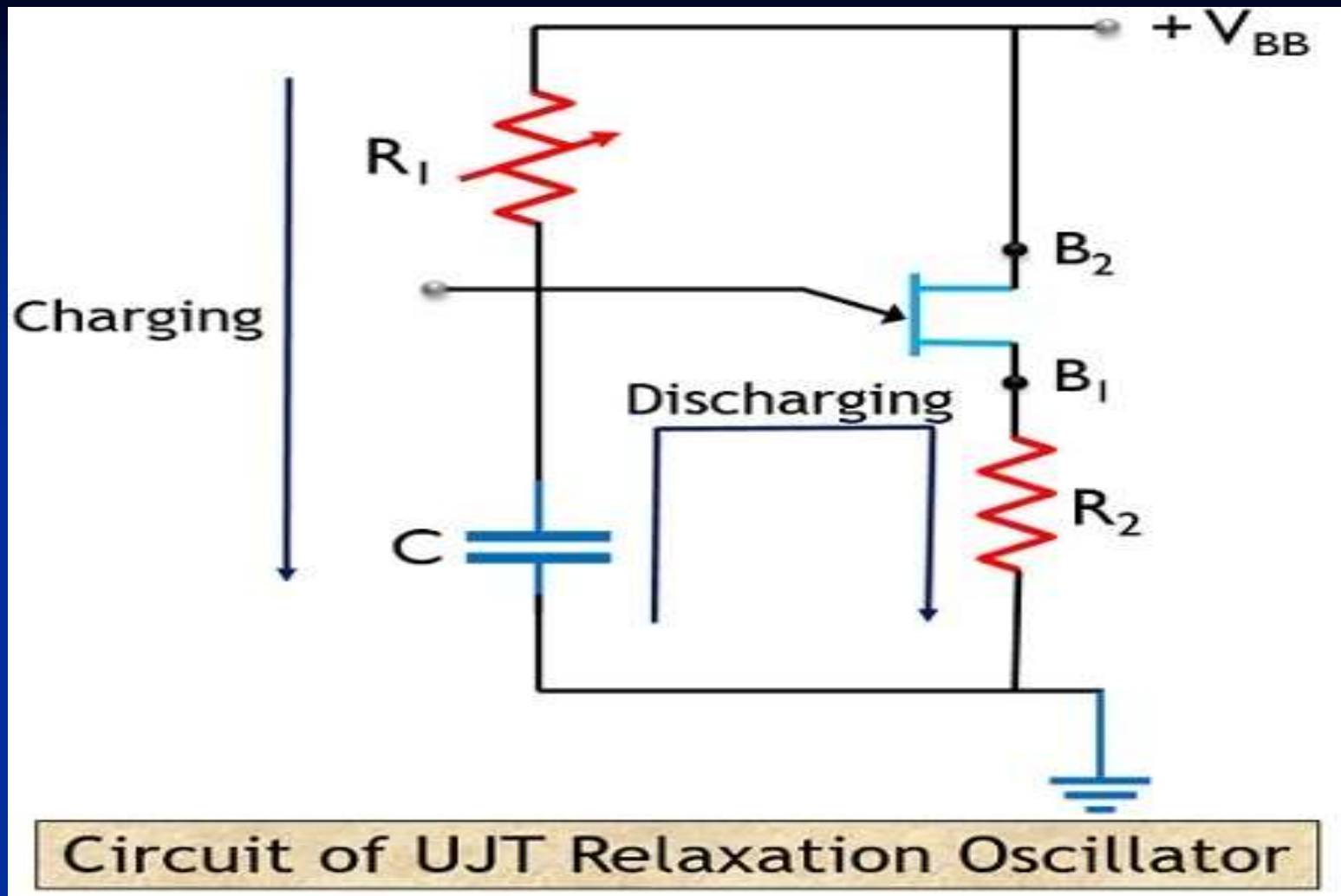


- Fig (9) Shown a Uni-junction transistor relaxation oscillator circuit diagram.

- The **capacitor C** charges according to the voltage

$$V = V_0 (1 - e^{-t / R_1 C})$$

- The **capacitor C** usually starts charging through Resistor **R1** and continues to charge until the maximum voltage **VBB**. But in this circuit, when the voltage across **capacitor C** reaches a value, which enables the **UJT** to **turn ON** (the **peak voltage VP**) then the **capacitor C** stops to charge and starts discharging through Resistor **R2** and **switching device** it self **UJT** present in the circuit.
- Now, this discharging continues until the minimum voltage which turns the **UJT OFF** (the **valley voltage VV**). This process **continues** and the **voltage across** the **capacitor C** and Resistor **R2** the following waveform is observed and **indicated on a graph** which is shown in **Fig (10)** in next slide.

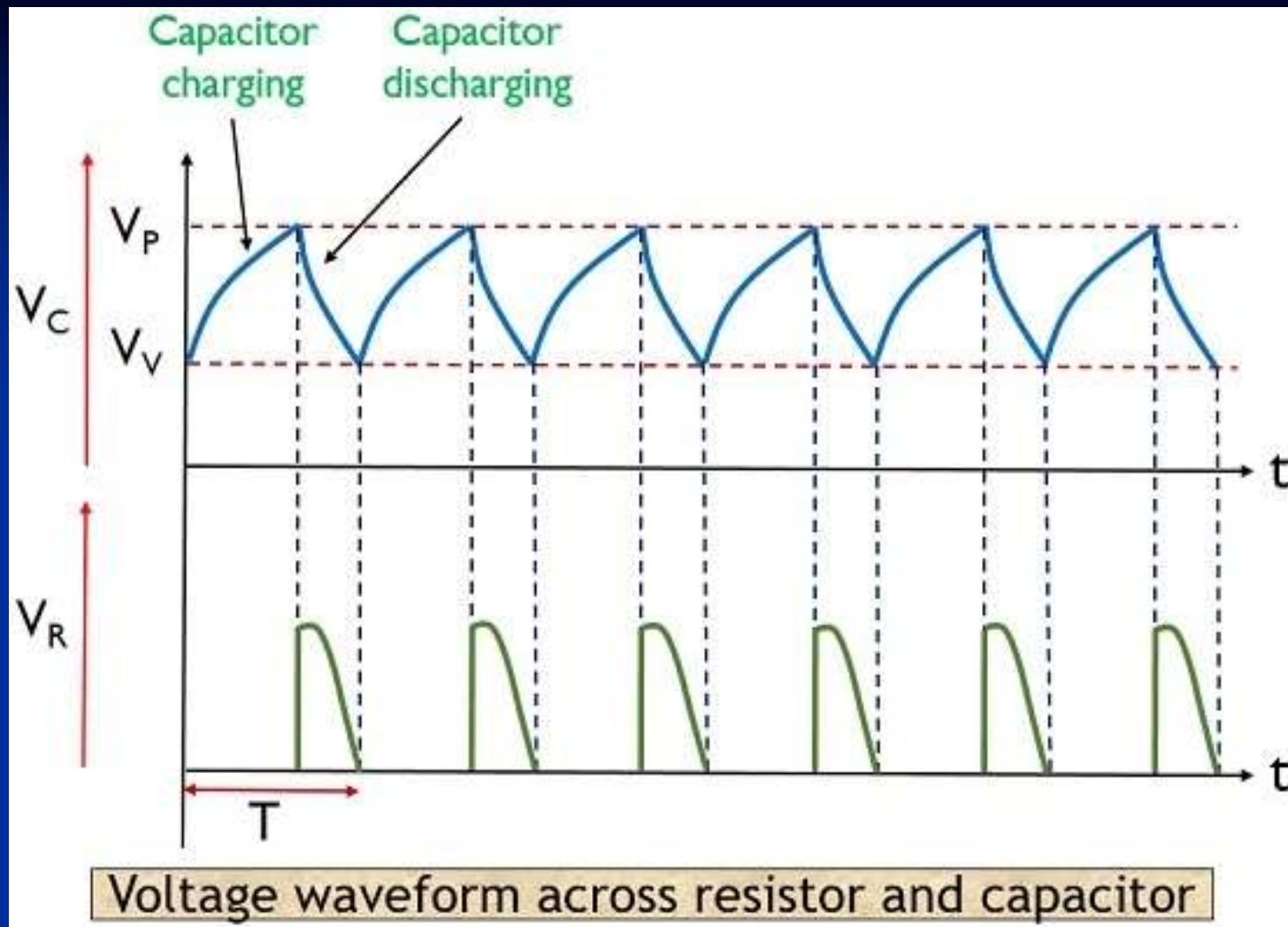

- **Fig. (10)** Shown relaxation oscillator (sawtooth) output voltage waveforms across capacitor and resistor.

- If the capacitor is charged to the voltage V_P in time T , we can write,

$$V_P = V_{BB} (1 - e^{-t / R_1 C})$$

$$\eta = 1 - e^{-t / R_1 C}$$

$$T = R_1 C \ln [(1 / 1 - \eta)]$$

Above equation gives the time period of the relaxation oscillator.

- For calculating the oscillating frequency we can use the following formula,

$$f = 1 / T$$

$$f = 1 / R_1 C \ln [(1 / 1 - \eta)]$$

- The standard value of the stand-off ratio for a typical UJT device is between 0.4 and 0.6. Thus considering the value of $\eta = 0.5$, and substituting it in the above equation we get:

$$f = 1 / R_1 C \ln [(1 / 1 - 0.5)]$$

$$f = 1.44 / R_1 C \ln 2$$

$$f = 1.44 / R_1 C$$

$$f = 1.5 / R_1 C$$

- So, the **charge** and **discharge** of capacitor produces the sweep waveform as shown in **Fig (10)** in previous slide. The **charging** time of **Capacitor C** produces **increasing sweep** and the **discharging** time of **Capacitor C** produces **decreasing sweep**. The **repetition** of this cycle forms a continuous sweep output waveform. As the output is a non-sinusoidal waveform and due to this relaxing state of the oscillator hence this circuit is said to be working as a relaxation oscillator.

to be continued