

Paper 1, TDC Part-1
Chapter– 1, Introduction to Passive Elements
Inductor Lecture 3

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics


L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Introduction to Passive Elements- Inductor

Energy Stored in Inductor

NOTE 8 PRO
D CAMERA

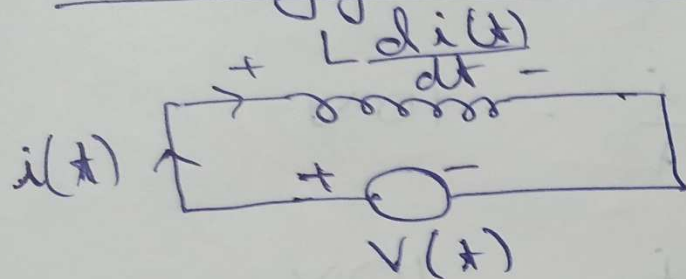

$$p(t) = \frac{L di(t)}{dt} \times i$$

Energy supplied to the inductor in time " dt " ($dt \rightarrow 0$)

$$dw = L \frac{di}{dt} \times i \times dt = L i di$$

So energy supplied to inductor


$$w = L \int_0^I i di = \frac{1}{2} L I^2$$

This energy is stored in magnetic field (magnetic lines of force). Therefore what energy has been supplied by voltage source is not lost.

Introduction to Passive Elements- Inductor

REDMI NOTE 8 PRO


So

$$2A \quad L = 0.5H$$


then

$$W = \frac{1}{2} L I^2 = \frac{1}{2} \times 0.5 \times 2^2 = 1 \text{ Joule}$$

Now let us look

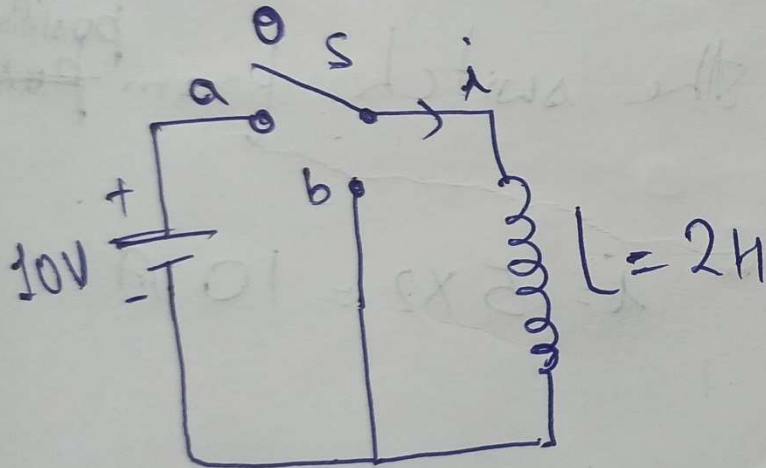


Before $t < 0$ the switch is open i.e. it at position '0'. At $t = 0$ the switch moved to the position 'a' then we

$$\text{have } i(0^-) = 0 = i(0) = i(0^+)$$

Introduction to Passive Elements- Inductor

EDM NOTE 8 PRO
QUAD CAMERA

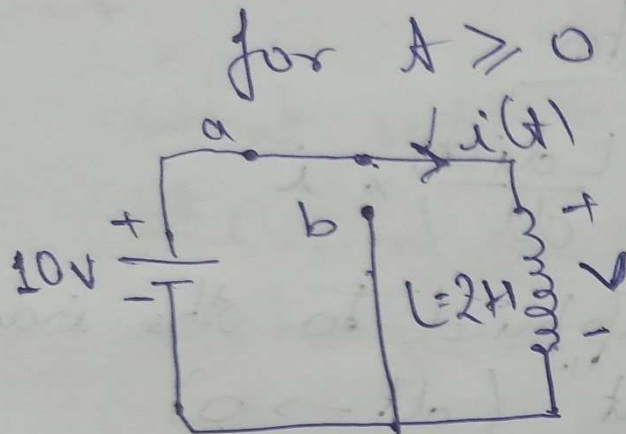

$$V = L \frac{di}{dt} = 10V$$

$$\text{or, } 2 \frac{di}{dt} = 10V$$

$$di = 5 dt$$

Integrating both side we have,

$$i = 5A + K \quad (i) \text{ where } K \text{ is const.}$$

Now at $t=0$ we have $i=0$ so putting these value in eqn. (i) we get.


$$0 = 5 \times 0 + K$$

Introduction to Passive Elements- Inductor

$$0 = 5 \times 0 + K$$

$$K = 0$$

$$\text{So, } i = 5t$$

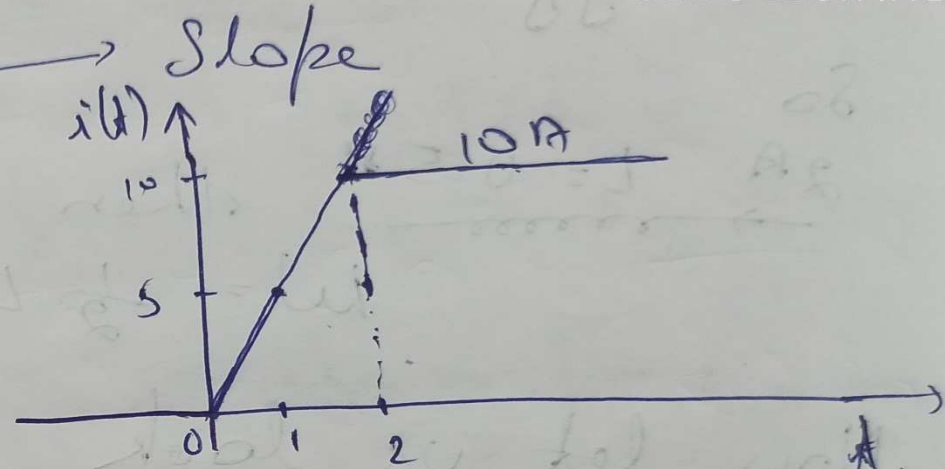


Now at $t = 2$ s move the switch from ~~position 'a'~~ to 'b'

at $t = 2$ s we have $i = 5 \times 2 = 10$ A

and for $t \geq 2$
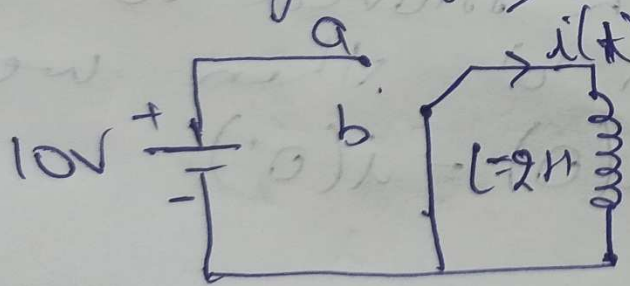
$$\text{So } i(t = 2\text{ s}) = 10 \text{ A}$$




Introduction to Passive Elements- Inductor

$$\text{Now, } L \frac{di}{dt} = 0 \Rightarrow \frac{di}{dt} = 0$$

this means ~~i~~ i must be constant for $t \geq 2$


so for $t > 2$

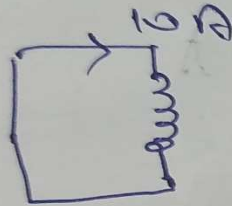

Energy stored in the inductor at $t \geq 2$

$$W = \frac{1}{2} \times L i^2 = \frac{1}{2} \times 2 \times 100 = 100 \text{ J}$$

R-L series Ckt:->

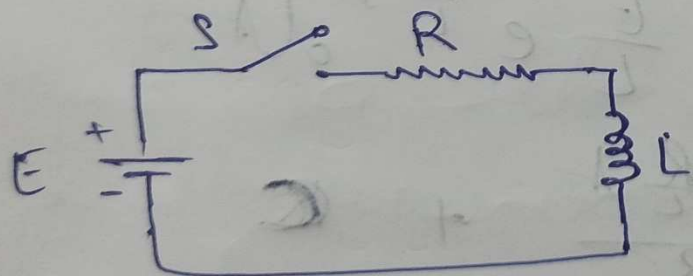


for $t < 0$ $S \rightarrow$ opened

$$\text{so } i(0^-) = 0 = i(0)$$

At $t = 0$ S is closed

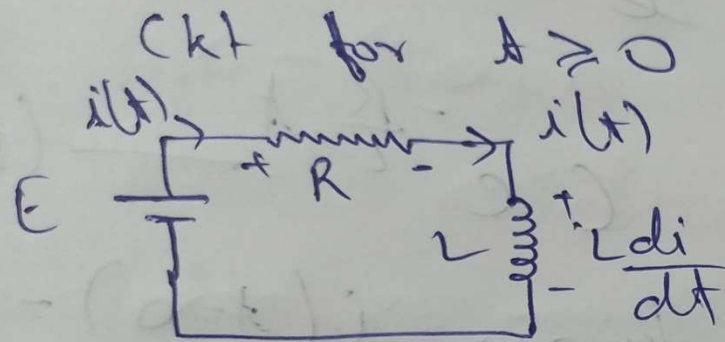Introduction to Passive Elements- Inductor



$$i(0^+) = i(0) = i(0^-) = 0$$

Now applying KVL in above ckt we have

$$-E + Ri + L \frac{di}{dt} = 0$$

$$\text{or } Ri + L \frac{di}{dt} = E \longrightarrow \text{1st Order LDE}$$

Dividing above eqn. by L on both side

$$\frac{di}{dt} + \frac{R}{L} i = \frac{E}{L} \quad \text{--- (A)}$$

Here we get Integrating factor $e^{\frac{R}{L} t}$

Introduction to Passive Elements - Inductor

For any query contact- 9771474020

Thank You

To be Contd..