

Paper 1, TDC Part-1
Chapter– 1, Introduction to Passive Elements
Inductor Lecture 4

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Introduction to Passive Elements- Inductor

So multiplying eqn (A) by $e^{\frac{R}{L}t}$ i.e. we get,

$$e^{\frac{R}{L}t} \frac{di}{dt} + \frac{R}{L} e^{\frac{R}{L}t} i = \frac{E}{L} e^{\frac{R}{L}t}$$

$$\frac{d}{dt} (e^{\frac{R}{L}t} \cdot i) = \frac{E}{L} e^{\frac{R}{L}t}$$

$$\text{or, } d(e^{\frac{R}{L}t} \cdot i) = \frac{E}{L} e^{\frac{R}{L}t} dt$$

Now integrating both side we get

$$\int d(e^{\frac{R}{L}t} \cdot i) = \int \frac{E}{L} e^{\frac{R}{L}t} dt$$

Introduction to Passive Elements- Inductor

$$e^{\frac{R}{L}t} \cdot i = \frac{E}{L} \times \frac{e^{\frac{R}{L}t}}{\frac{R}{L}} + C$$

So, we get

$$i(t) = \frac{E}{R} + C e^{-\frac{R}{L}t} \quad (B)$$

Now at $t=0$ we know $i(t=0)=0$

So from eqn. (B) we have

$$0 = \frac{E}{R} + C e^0$$

$$\text{or, } C = -\frac{E}{R}$$

Finally we have


$$i(t) = \frac{E}{R} - \frac{E}{R} e^{-\frac{R}{L}t}$$

Introduction to Passive Elements- Inductor

$$i(t) = \frac{E}{R} (1 - e^{-\frac{R}{L}t})$$

EDMI NOTE 8 PRO
I QUAD CAMERA

$$i(t = \infty) = \frac{E}{R}$$

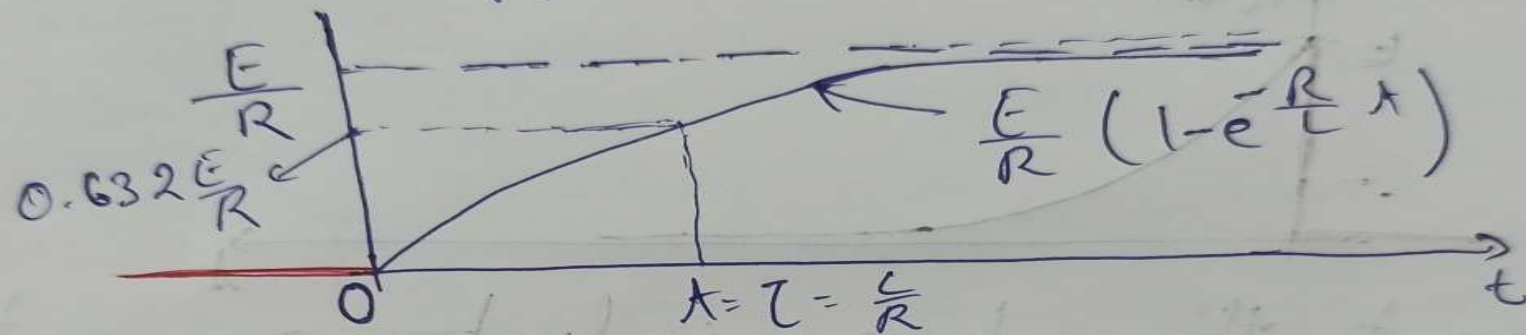

$$\frac{L}{R} = \tau = \text{time const.}$$

$$i(t) = \frac{E}{R} (1 - e^{-t/\tau})$$

$$\text{So, } i(t = \tau) = \frac{E}{R} (1 - e^{-\tau/\tau}) = \frac{E}{R} (1 - e^{-1})$$

$$= 0.632 \frac{E}{R}$$

Introduction to Passive Elements- Inductor

So, After a few time constant current will reach 99%. i.e. it will reach steady state.

Now Voltage across the inductor is.

$$V_L(t) = L \frac{di}{dt} = L \frac{d}{dt} \left[\frac{E}{R} - e^{-t/\tau} \right]$$

$$= 0 - \frac{L \times E}{R} \frac{d e^{-t/\tau}}{dt}$$


$$= \frac{EL}{R} \times \frac{1}{\tau} e^{-t/\tau}$$

$$= E e^{-t/\tau} \quad \text{at } \tau = \frac{L}{R}$$


Introduction to Passive Elements- Inductor

$$V_L(0^-) = 0$$

$$V_L(0^+) = E e^{-0/\tau} = E$$

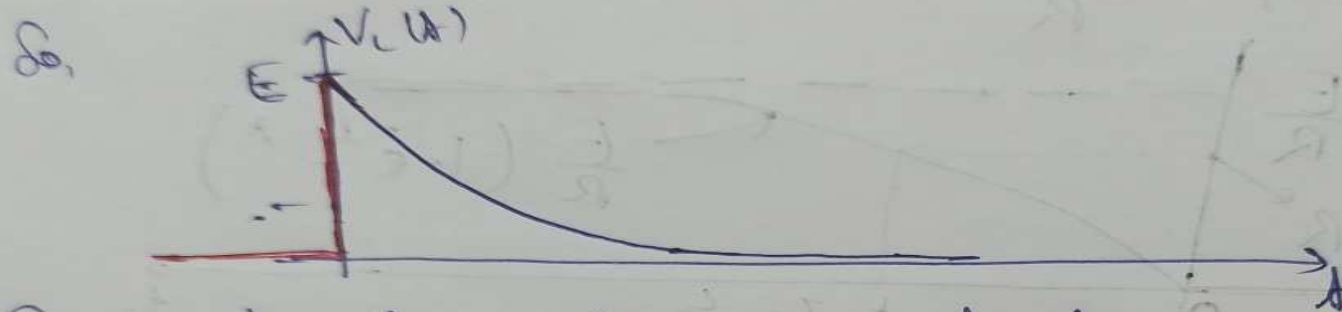

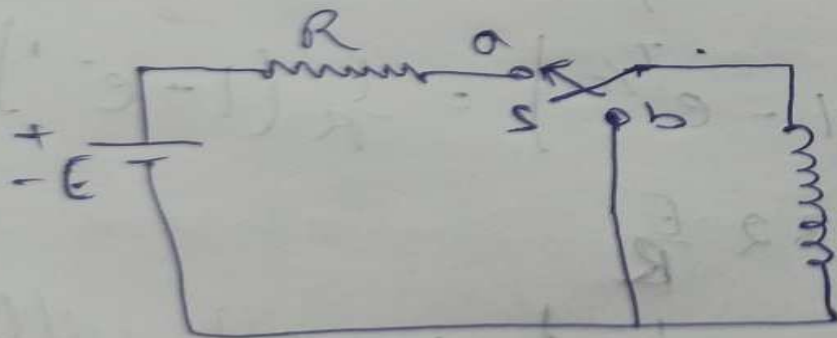Current through an inductor can not have a step jump however voltage can have a step jump.



at $t < 0$, switch is open and there is no current so $i(0^-) = 0$

Introduction to Passive Elements- Inductor

Now at $t = 0$ the switch is closed i.e. it moves to position 'a' then we have already seen that

$$i(t) = \frac{E}{R} (1 - e^{-t/\tau}) \quad \text{where } \tau = L/R$$

After few time constant the


$$i(t) = \frac{E}{R}$$

then energy stored in Inductor will be

$$= \frac{1}{2} L \left(\frac{E}{R} \right)^2$$

Introduction to Passive Elements- Inductor

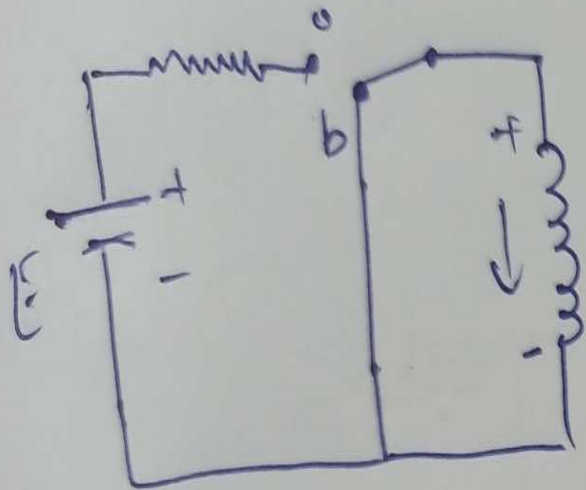Now when the switch is moved to position 'b' we have ckt. like



$$V = 0 = L \frac{di(t)}{dt}$$

$$i(t) = \frac{E}{R}$$

$$\text{So the energy is } \frac{1}{2} L \left(\frac{E}{R}\right)^2$$

Introduction to Passive Elements - Inductor

For any query contact- 9771474020

Thank You

To be Contd..