

# **Communication**

## **Lecture - 9**

**Dr. Tarun Kumar Dey**

**Professor in Physics**

**HOD , Electronics ,L.S College; BRA Bihar University,**

**Muzzaffarpur.**

**Online platform : [meet.findmementor.com](https://meet.findmementor.com)**

## Generation of Amplitude Modulation( Modulator ) :


An amplitude – modulated carrier can be obtained by passing the output of a carrier frequency oscillator through an amplifier whose gain is varied by the modulating signal .

This amplifier is called an **amplitude- modulated amplifier** or simply a **modulator** .

The circuit diagram of such an amplifier in CE mode of connection as shown in figure below .

The carrier and the modulation voltages are fed into the base and the emitter respectively .

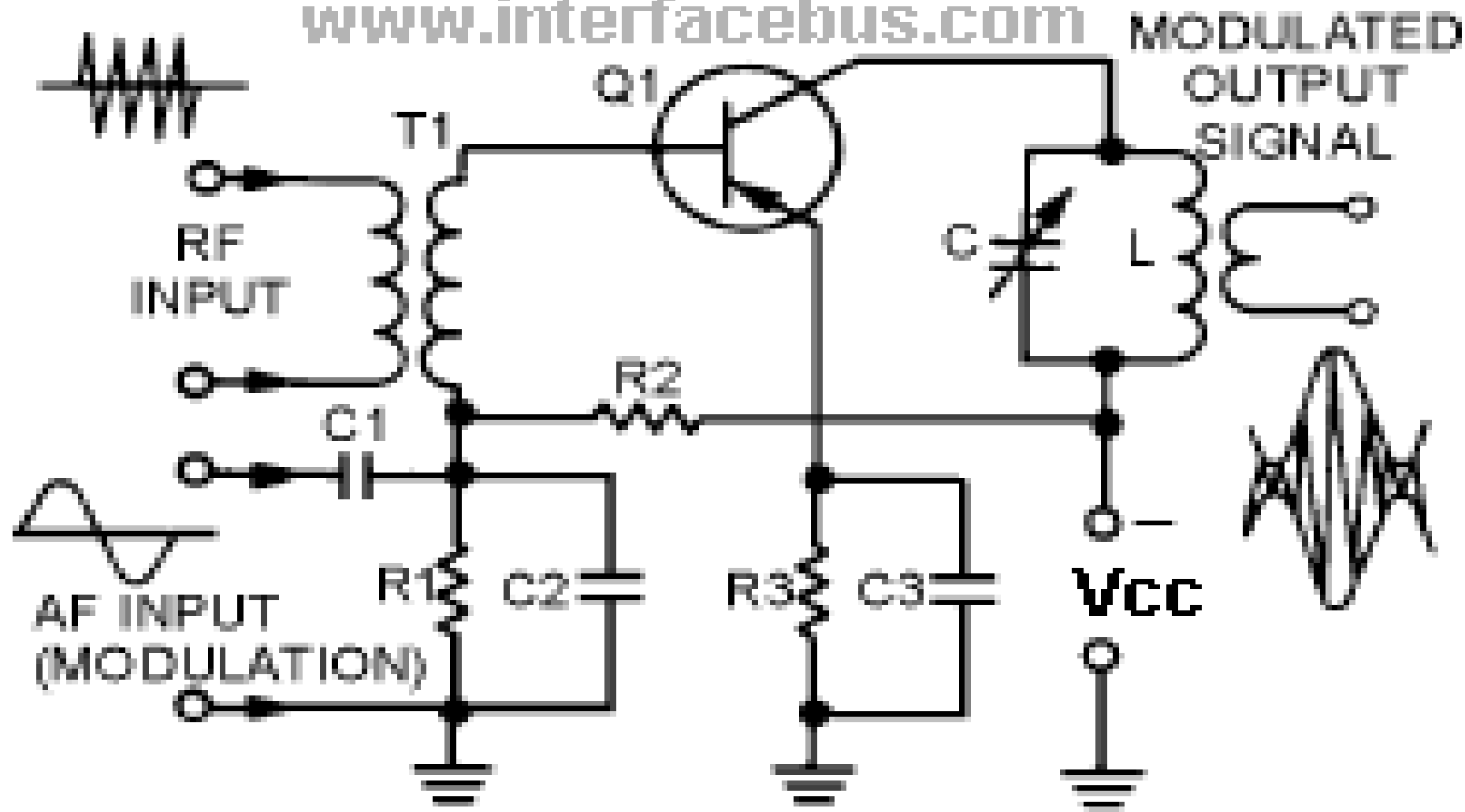The resistors  $R_1$  ,  $R_2$  and  $R_3$  and the supply voltage  $V_{CC}$  establish the DC operating point of the amplifier . The capacitors  $C_1$  ,  $C_2$  and  $C_3$  are chosen as to bypass the carrier wave only .



The gain of a transistor amplifier is highly dependent upon the quiescent emitter current .

Since the modulation is injected at the emitter, the total emitter current follows the instantaneous modulating signal and is given by

$$i_E = I_E + K_1 E_m \text{Cos } \omega_m t \quad (1)$$

where  $I_E$  is the quiescent value of the emitter current and  $K_1$  is a constant .

Amplitude modulation results if  $K_1 E_m$  is smaller than  $I_E$  .

As the voltage amplification of the amplifier  $A_V$  is a function of the total emitter current  $i_E$

we get

$$A_V = K_2 i_E = K_2 ( I_E + K_1 E_m \text{Cos } \omega_m t ) \quad (2)$$

$K_2$  is a another constant .

Since the input to the another amplifier is carrier voltage

$$e_c = E_c \text{Cos } \omega_c t$$

the output voltage  $V_o = A_V E_c \text{Cos } \omega_c t$  (3)

substituting for  $A_v$  from Eq.(2) in Eq.(3) we get

$$\begin{aligned}V_o &= K_2 ( I_E + K_1 E_m \text{Cos } \omega_m t ) E_c \text{Cos } \omega_c t \\&= K_2 I_E E_c \text{Cos } \omega_c t + K_1 K_2 E_c E_m / 2 [ \text{Cos } (\omega_c + \omega_m )t + \\&\quad \text{Cos } (\omega_c - \omega_m )t ] \\&= K_2 I_E [ E_c \text{Cos } \omega_c t + K_1 K_2 E_c E_m / 2 I_E \{ \text{Cos } (\omega_c + \omega_m )t + \\&\quad \text{Cos } (\omega_c - \omega_m )t \} ] \\&= K [ E_c \text{Cos } \omega_c t + m E_c / 2 [ \text{Cos } (\omega_c + \omega_m )t + \text{Cos } (\omega_c - \omega_m )t ] \quad (4)\end{aligned}$$



Where  $K = K_2 I_E$  and  $m = K_1 E_m / I_E$

Equation ( 4) represents an amplifier – modulated wave .

Since distortion is always present in an amplifier , signals of unwanted frequencies also appear at the output .

The tuned circuit at collector of the modulator stage eliminates these undesirable signals.

## Amplitude Modulated Carrier Wave

