

# Transistor Biasing Lecture-33

TDC PART -3

PAPER 6(GROUP B)

Chapter -6

BY:

DR. NAVIN KUMAR

(ASSISTANT PROFESSOR)

(GUEST FACULTY)

Department of Electronics

L.S COLLEGE, BRA Bihar University, Muzaffarpur.



# Transistor

- A **transistor** is a semiconductor device used to amplify or switch electronic signals and electrical power. It is composed of semiconductor material usually with at least three terminals for connection to an external circuit.

# BIASING


- **Biasing** is the setting of initial operating conditions (current and voltage) of an active device in an amplifier.
- Many electronic devices, such as diodes, transistors and vacuum tubes, whose function is processing time-varying (AC) signals, also require a steady (DC) current or voltage at their terminals to operate correctly.

# Transistor Biasing

- **Biasing** is the process of providing DC voltage which helps in the functioning of the circuit.
- A **transistor** is biased in order to make the emitter base junction forward **biased** and collector base junction reverse **biased**, so that it maintains in active region, to work as an amplifier



# TYPES OF BIASING

- Base Resistor method
  - Collector to Base bias
  - Biasing with Collector feedback resistor
  - Voltage-divider bias
- 



# MOST EFFICIENT

- Out of all these configurations voltage divider **bias** is the **best**, as the stability of this circuit with respect to change in beta, change in saturation current, change in base emitter voltage is more as compared to other configurations.
- 