

Communication Systems

Lecture - 9

Dr. Tarun Kumar Dey,

Associate professor. Department of Physics

L.S College; BRA Bihar University,

Muzzaffarpur.

Youtube channel - Tarun Kumar Dey

Online Course Link - <https://findmementor.com/>

Generation of Amplitude Modulation(Modulator) :


An amplitude – modulated carrier can be obtained by passing the output of a carrier frequency oscillator through an amplifier whose gain is varied by the modulating signal .

This amplifier is called an **amplitude- modulated amplifier** or **simply a modulator** .

The circuit diagram of such an amplifier in CE mode of connection as shown in figure below .

The carrier and the modulation voltages are fed into the base and the emitter respectively .

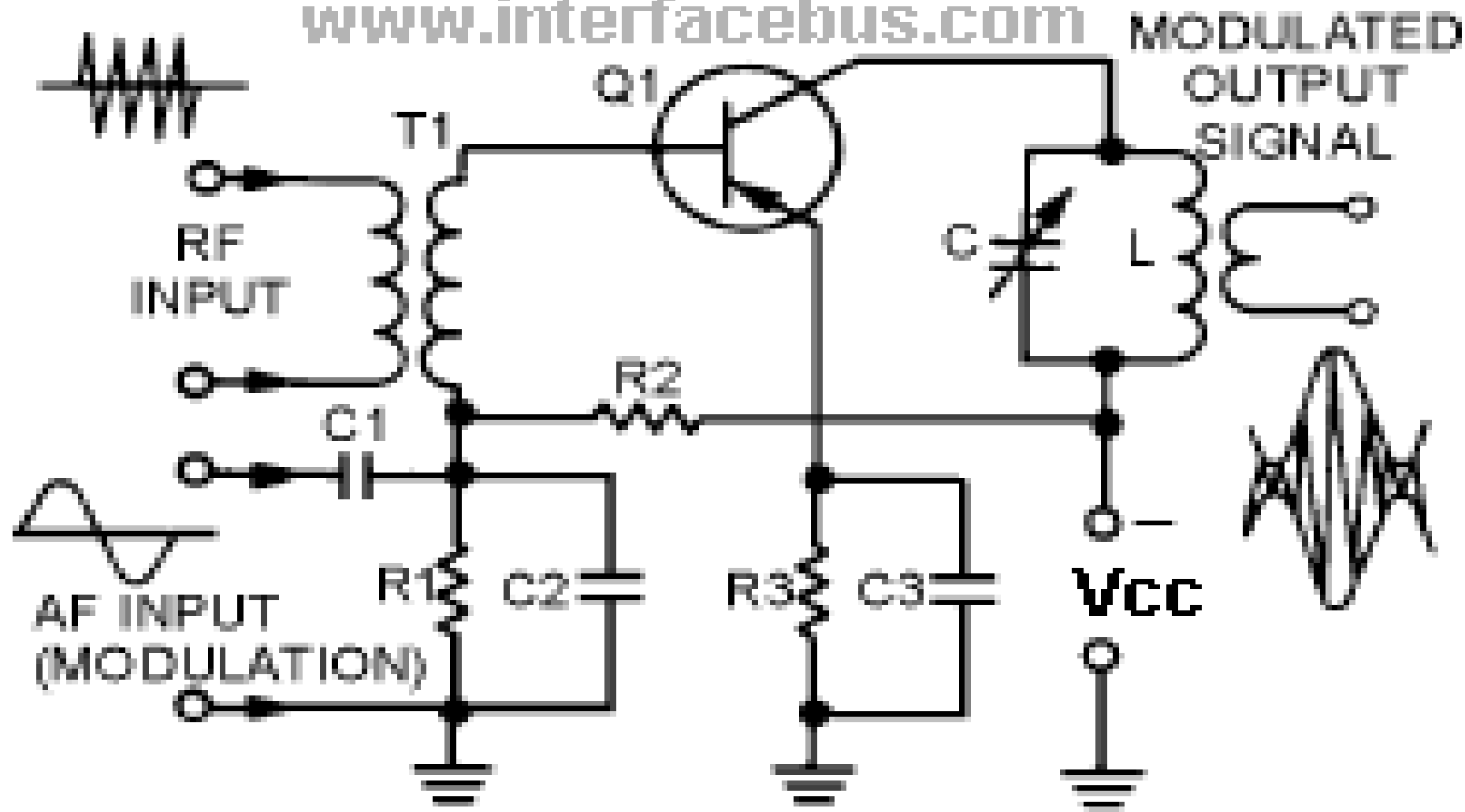The resistors R_1 , R_2 and R_3 and the supply voltage V_{CC} establish the DC operating point of the amplifier . The capacitors C_1 , C_2 and C_3 are chosen as to bypass the carrier wave only .



The gain of a transistor amplifier is highly dependent upon the quiescent emitter current .

Since the modulation is injected at the emitter, the total emitter current follows the instantaneous modulating signal and is given by

$$i_E = I_E + K_1 E_m \text{Cos } \omega_m t \quad (1)$$

where I_E is the quiescent value of the emitter current and K_1 is a constant .

Amplitude modulation results if $K_1 E_m$ is smaller than I_E .

As the voltage amplification of the amplifier A_V is a function of the total emitter current i_E

we get

$$A_V = K_2 i_E = K_2 (I_E + K_1 E_m \text{Cos } \omega_m t) \quad (2)$$

K_2 is a another constant .

Since the input to the another amplifier is carrier voltage

$$e_c = E_c \text{Cos } \omega_c t$$

the output voltage $V_o = A_V E_c \text{Cos } \omega_c t \quad (3)$

substituting for A_v from Eq.(2) in Eq.(3) we get

$$\begin{aligned} V_o &= K_2 (I_E + K_1 E_m \text{Cos } \omega_m t) E_c \text{Cos } \omega_c t \\ &= K_2 I_E E_c \text{Cos } \omega_c t + K_1 K_2 E_c E_m / 2 [\text{Cos } (\omega_c + \omega_m)t + \\ &\quad \text{Cos } (\omega_c - \omega_m)t] \\ &= K_2 I_E [E_c \text{Cos } \omega_c t + K_1 K_2 E_c E_m / 2 I_E \{ \text{Cos } (\omega_c + \omega_m)t + \\ &\quad \text{Cos } (\omega_c - \omega_m)t \}] \\ &= K [E_c \text{Cos } \omega_c t + m E_c / 2 [\text{Cos } (\omega_c + \omega_m)t + \text{Cos } (\omega_c - \omega_m)t] \end{aligned} \quad (4)$$

Where $K = K_2 I_E$ and $m = K_1 E_m / I_E$

Equation (4) represents an amplifier - modulated wave .

Since distortion is always present in an amplifier , signals of unwanted frequencies also appear at the output .

The tuned circuit at collector of the modulator stage eliminates these undesirable signals.

Amplitude Modulated Carrier Wave

