

Paper 1, TDC Part-1
Chapter– 4, Circuit Theorems
Lecture - 11

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Circuit Theorem

Star – Delta Transformation: -

Sometimes in a circuit passive elements are neither connected in parallel nor in series. They may be connected in star (Y) form or delta (Δ). To solve those type of networks which is having star or delta connection of passive elements, it is required to do necessary transformation that is star network into its equivalent delta network or delta network to star network.

These type of connection are especially useful in 3 phase circuits.

The replacement of star connection by its equivalent delta connection is called Star-Delta transformation

Circuit Theorem

While the replacement of delta connection by its equivalent star connection is called Delta-Star transformation.

The two connections are equivalent or identical to each other if the impedance is measured between any pair of lines irrespective of whether delta is connected between the lines or its equivalent star is connected between that lines.

A single star or delta connection of elements requires 3 passive elements to form the connection.

Circuit Theorem

Star-Delta Transformation :-
Star Connection of resistor

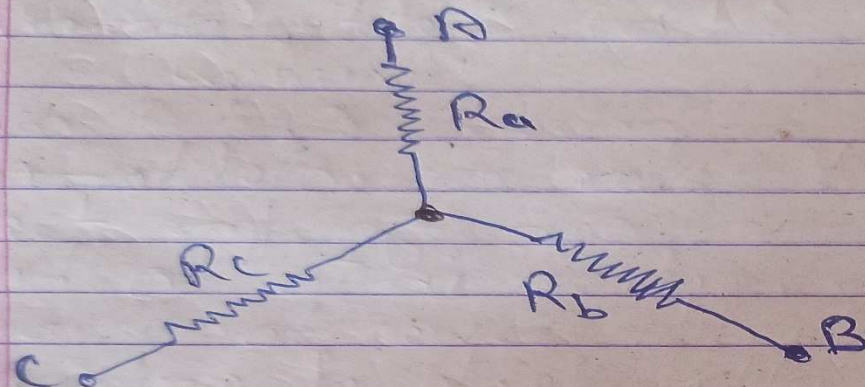


figure 1(a) Star connection of Resistor

One end of all three resistors are connected ~~at a same~~ together and other end of each resistor is connected to other element or other terminal to form 'Y' like pattern as shown in above figure 1(a).

Delta-~~Star~~ Connection of resistor :-

In a delta connection all three resistors are connected such that one end of resistor is connected to one end of

Circuit Theorem

Other resistor and all resistors are connected to each other. The Δ connection of resistors is shown in figure 1(b).


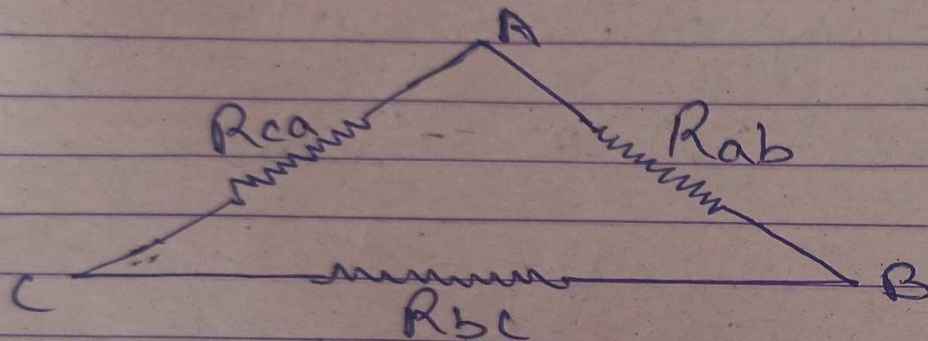


Figure 1(b) Delta Connection of Resistors.

Whenever we get star or delta connection in a network we can go for transformation of one connection into other as per the requirement. Due to this transformation the task of analysing the network become easy.

Circuit Theorem

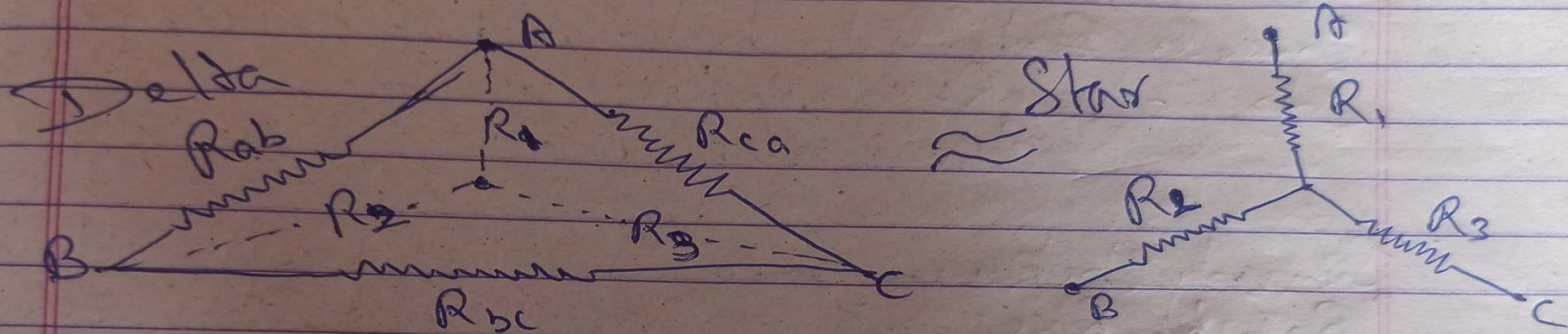Delta to Star Transformation :-
Let us consider a delta connection as shown below.



The delta network is having resistors R_{ab} , R_{bc} & R_{ca} connected between terminal 'A', 'B' & 'C' respectively. The equivalent star connection is having resistors R_1 , R_2 & R_3 . Now let us find value of R_1 , R_2 & R_3 in terms of R_{ab} , R_{bc} & R_{ca} to find the equivalence Y network, of corresponding delta network.

Circuit Theorem

Equivalent resist. between A & B of delta n/w
is given as, $R_{ab} \parallel (R_{bc} + R_{ca})$
$$= \frac{R_{ab} (R_{bc} + R_{ca})}{R_{ab} + R_{bc} + R_{ca}} \quad \text{--- (i)}$$

So when we look into delta n/w through
terminal A & B we see that R_{bc} & R_{ca}
will be in series and R_{ab} will appear
parallel to series connection of $(R_{bc} + R_{ca})$

Similarly equival. resist. between B & C terminal

Circuit Theorem

R_{ab} & R_{ca} will be series and R_{bc} will be then in parallel to series connection of $(R_{ab} + R_{ca})$.

So,

Equival. Resist. between B & C can be given as:

$$= \frac{R_{bc} (R_{ab} + R_{ca})}{R_{bc} + (R_{ab} + R_{ca})} \quad \text{--- (2)}$$

Similarly between terminal A & C we will have R_{ab} & R_{bc} are in series and this series of $(R_{ab} + R_{bc})$ will be in parallel with R_{ca} so,

Equivalent resistance between C & A can be given as,

$$= \frac{R_{ca} (R_{ab} + R_{bc})}{R_{ca} + R_{ab} + R_{bc}} \quad \text{--- (3)}$$

Circuit Theorem

Now consider the star connection,
Req Resist. between terminal A & B is,
 $= R_1 + R_2$ ————— (4)

Similarly Eq. Resist. between terminal B & C is,
 $= R_2 + R_3$ ————— (5)

Similarly Eq. Resist. between terminal C & A is,
 $= R_3 + R_1$ ————— (6)

Using these 6 eqns. we will find R_1 , R_2 , & R_3 in terms of R_{AB} , R_{BC} & R_{CA}

Circuit Theorem

Now equating eqn. (1) & (4) we get,

$$\frac{R_{ab}(R_{bc} + R_{ca})}{R_{ab} + R_{bc} + R_{ca}} = R_1 + R_2 \quad \text{--- (7)}$$

Similarly equating eqn. (2) & (5) we get,

$$\frac{R_{bc}(R_{ab} + R_{ca})}{R_{bc} + R_{ab} + R_{ca}} = R_2 + R_3 \quad \text{--- (8)}$$

and equating eqn. (3) & (6) we get,

$$\frac{R_{ca}(R_{ab} + R_{bc})}{R_{ca} + R_{ab} + R_{bc}} = R_3 + R_1 \quad \text{--- (9)}$$

Circuit Theorem

Now subtracting eqn. 8 from eqn. 7 we get

$$\frac{R_{ab}(R_{bc} + R_{ca}) - R_{bc}(R_{ab} + R_{ca})}{R_{ab} + R_{bc} + R_{ca}} = R_1 + \cancel{R_2} - \cancel{R_2} - R_3$$

$$\text{or } \frac{R_{ab} \cdot R_{ca} - R_{bc} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} = R_1 - R_3 \quad \text{--- (10)}$$

Now adding eqn. 9 & 10 we get,

$$\frac{R_{ca}R_{ab} + \cancel{R_{ca}R_{bc}} + R_{ab} \cdot R_{ca} - \cancel{R_{bc} \cdot R_{ca}}}{R_{ab} + R_{bc} + R_{ca}} = R_1 + \cancel{R_3} + R_1 - \cancel{R_3}$$

$$\Rightarrow \frac{2 R_{ab} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} = 2 R_1$$

Circuit Theorem

$$So R_1 = \frac{R_{ab} R_{ca}}{R_{ab} + R_{bc} + R_{ca}}$$

So if we look into the ckt now, then find out that R_1 resistor of star connection is connected to point A. and R_{ab} & R_{ca} are the resistor of Delta connection which is also connected to point A. of Delta connection,

~~Therefore we can say that,~~
In similar way we can find R_2 & R_3 in terms of R_{ab} , R_{bc} & R_{ca} .

Circuit Theorem


In similar way we can find R_2 & R_3 in terms of R_{ab} , R_{bc} & R_{ca} .

$$R_2 = \frac{R_{bc} \times R_{ab}}{R_{ab} + R_{bc} + R_{ca}} ; R_3 = \frac{R_{ca} \times R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$


So we can remember the formula for Delta to star transformation as "multiplication of 2 resistors which ~~not~~ were initially connected to that particular point divided by addition of all 3 resistors connected in Delta ~~the~~ connection.

Circuit Theorem

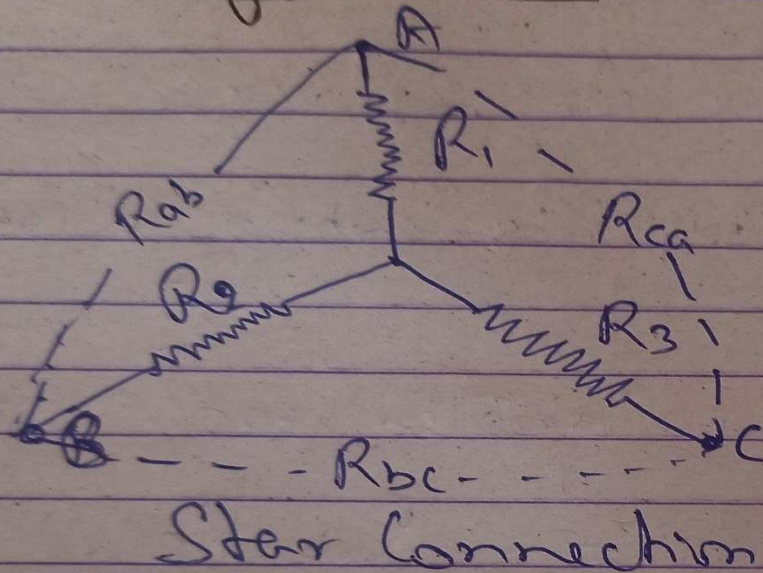Star Connection to Delta Connection transformation :-



$\approx$

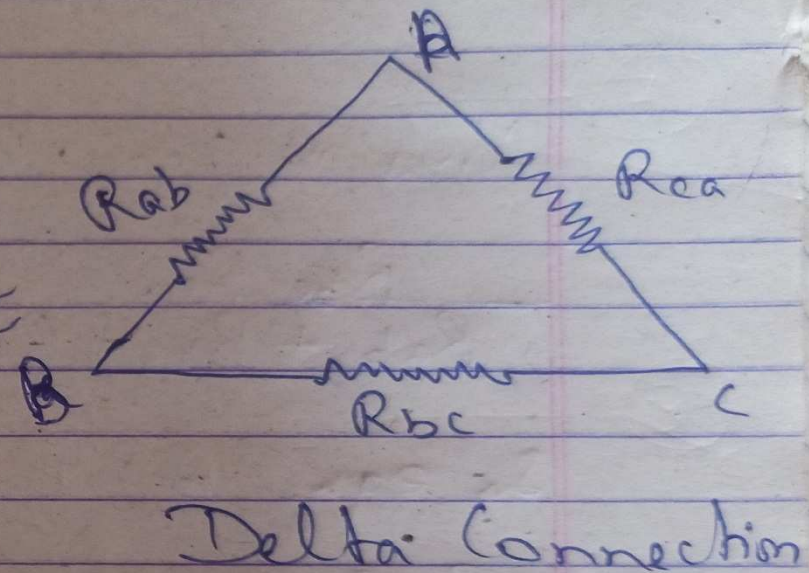

As we have seen in Delta to Star transformation,

$$R_1 = \frac{R_{ab} \times R_{ca}}{R_{ab} + R_{bc} + R_{ca}} ; R_2 = \frac{R_{bc} \times R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

Circuit Theorem

$$R_1 = \frac{R_{ab} \times R_{ca}}{R_{ab} + R_{bc} + R_{ca}} ; R_2 = \frac{R_{bc} \times R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_3 = \frac{R_{ca} \times R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

Now lets find,

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{ab}^2 R_{bc} R_{ca}}{(R_{ab} + R_{bc} + R_{ca})^2} + \frac{R_{bc}^2 R_{ab} R_{ca}}{(R_{ab} + R_{bc} + R_{ca})^2} + \frac{R_{ca}^2 R_{ab} R_{bc}}{(R_{ab} + R_{bc} + R_{ca})^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{ab} R_{bc} R_{ca} (R_{ab} + R_{bc} + R_{ca})}{(R_{ab} + R_{bc} + R_{ca})^2}$$

Circuit Theorem

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{ab} R_{bc} R_{ca}}{(R_{ab} + R_{bc} + R_{ca})} \quad \text{--- (A)}$$

Now in eqn. A we can replace,

$$\frac{R_{bc} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} \text{ by } R_3 \text{ which is value of } R_3$$

So eqn. A can be written as,

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_{ab} R_3$$

$$\text{So } R_{ab} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$
$$\text{or } R_{ab} = \frac{R_1 R_2}{R_3} + R_2 + R_1$$

Circuit Theorem

So we can ~~remember~~ remember this formula of delta to star connection as the resistor connected between terminal AB of Delta i.e. R_{AB} can be given as ~~addition~~ ^{the} multiplication of each 2 resistors of star connection divided by the resistor connected at terminal C of star connection,

$$\text{Hence } R_{BC} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$\& R_{CA} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

Circuit Theorem

In next lecture we will discuss some problems on Star-Delta Transformation. For any query or problem discuss on What's App or contact on number available.

THANK YOU