

Paper 1, TDC Part-1
Chapter– 4, Circuit Theorems
Lecture - 8

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Circuit Theorem

Today we will see few more problems on Maximum power transfer theorem.

Q 1)

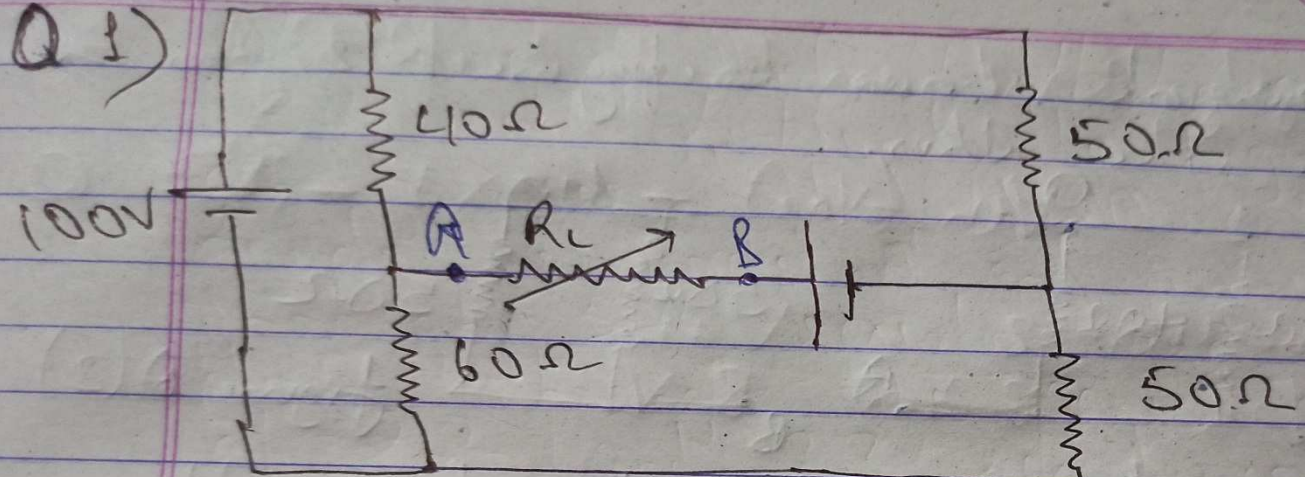


fig A(1)


for what value of R_L maximum power will transfer and also find P_{max} ?

Soln. As we know that for maximum power transfer R_L should equal to R_{th} .

Circuit Theorem


We know that for maximum power transfer R_L should equal to R_{th} .

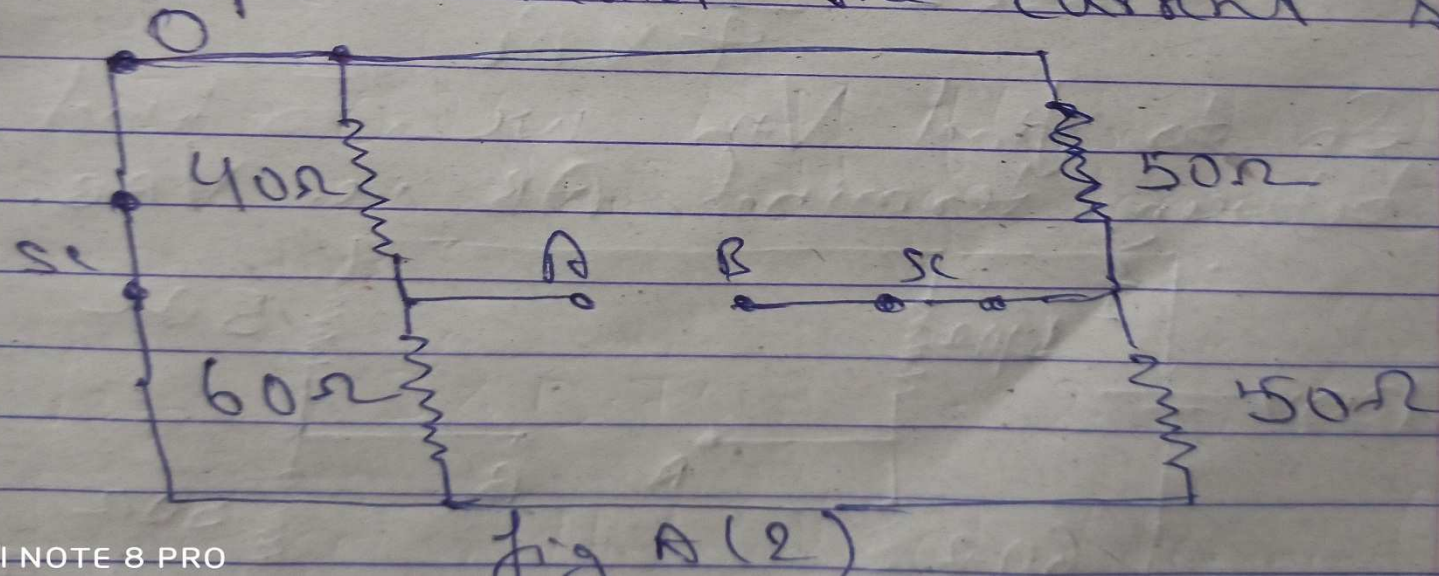So to calculate R_{th} we will look in to the circuit from terminal AB by removing R_L . as shown below we will also short circuit the voltage sources and open circuit the current sources.



Circuit Theorem

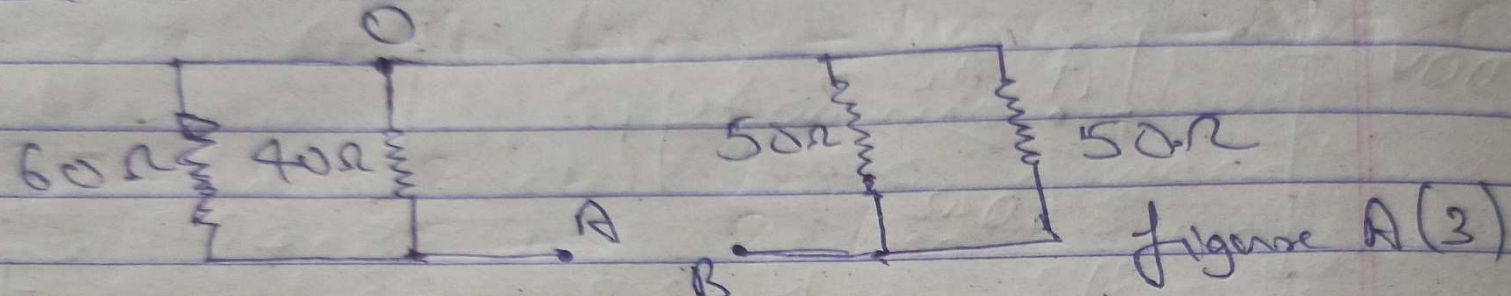The network shown in figure A(2) can be seen like this.



$$\text{So } R_{th} = (60\Omega \parallel 40\Omega) + (50\Omega \parallel 50\Omega)$$

$$= \frac{60 \times 40}{100} + \frac{50 \times 50}{100}$$

$$= 24 + 25\Omega$$

$$= 49\Omega$$

So for maximum power transfer the value of R_L should be 49Ω .


Circuit Theorem

So for maximum power transfer the value of R_L should be 29Ω .

Now to find P_{max} we should have the


$$P_{max} = \frac{V_{th}^2}{4 \times R_L}$$

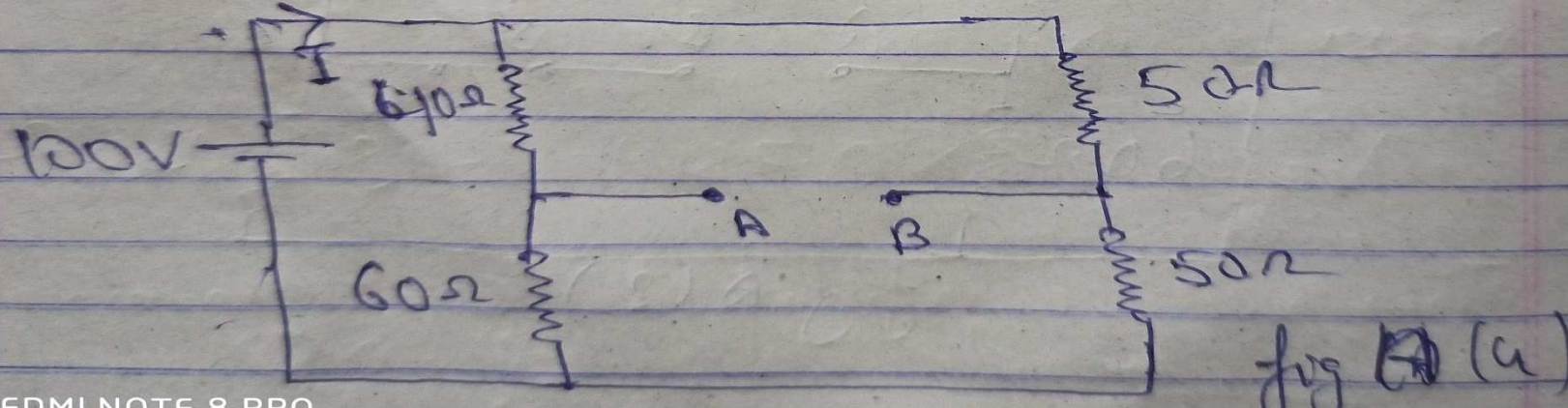So to find V_{th} we have to find voltage between terminal AB i.e. V_{AB} .



Circuit Theorem

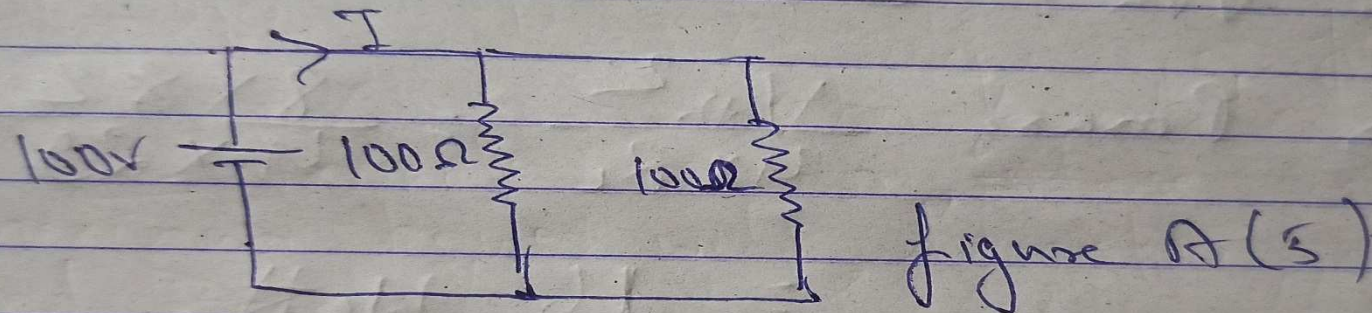As from the circuit shown in figure A(4) we see that terminal A-B is open so no current will flow. and hence the resistors ~~100~~ $60\ \Omega$ are in series. Also $50\ \Omega$ & $50\ \Omega$ are in series. so the ckt. can be,



We see! that now $100\ \Omega$ & $100\ \Omega$ are ||. So

$$I_2 = \frac{100\text{ V}}{\left(\frac{100 \times 100}{100 + 100}\right) \Omega} = \frac{200 \times 100}{100 \times 100} \text{ A}$$


$$I = 2 \text{ A}$$

Circuit Theorem

$$I = 2A$$

This current will distribute equal among the $(40\Omega \parallel 60\Omega)$ & $(50\Omega \parallel 50\Omega)$.

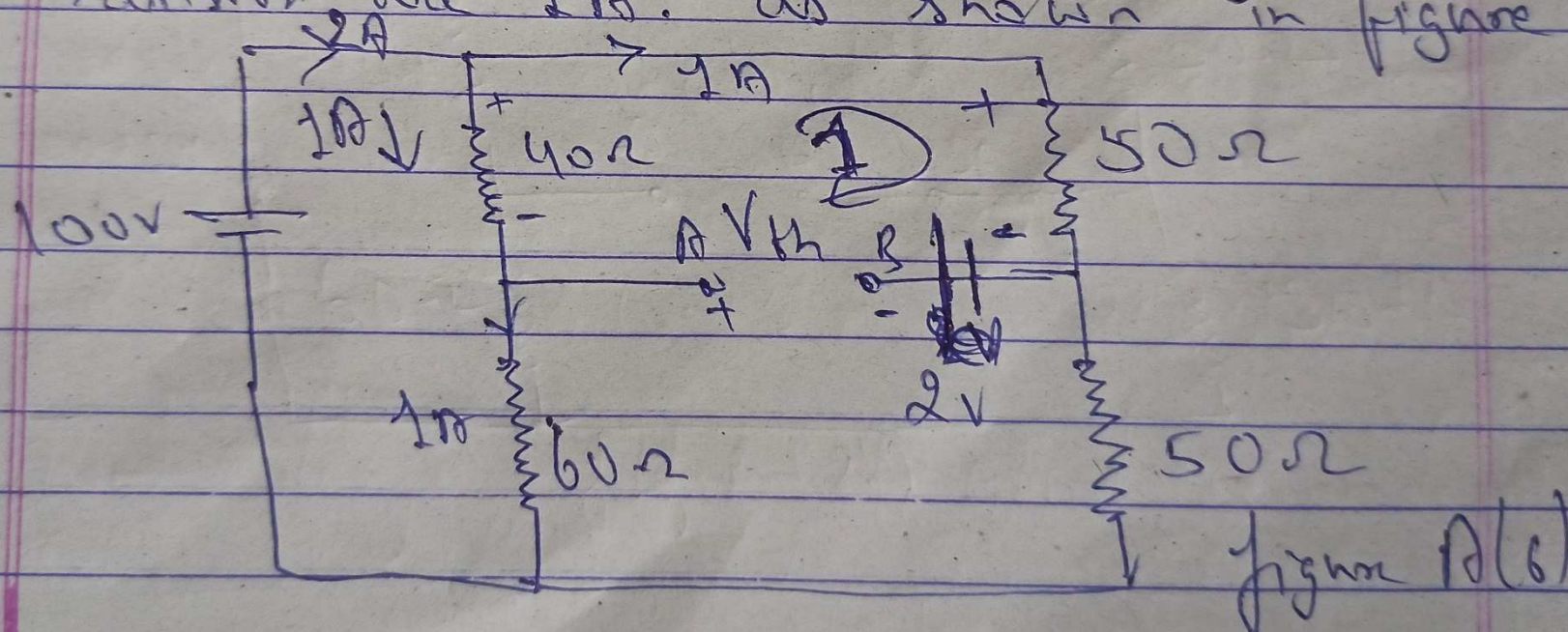So current ~~following~~ ^{through} flowing 40Ω & 50Ω resistor are $1A$. as shown in figure below



Circuit Theorem

Applying KVL in loop 1 of figure A(d)
we have,

$$50 \times 1 - V_{th} (V_{AB}) - 40 \times 1 - 2V = 0$$

$$\text{on } 50 - 40 - 2 = V_{th}$$

$$\text{on } V_{th} : \cancel{8} \text{ m } 8 \text{ V.}$$

$$\text{So } P_{max} = \frac{V_{th}^2}{4 \times R_L} = \frac{8 \times 8.2}{4 \times 49} =$$

$$= \frac{16}{49} \text{ Watt.}$$

Circuit Theorem

Q2) Find the value of R_L for which the n/w shown below provide maximum power to load resistor. Also calculate P_{max} .

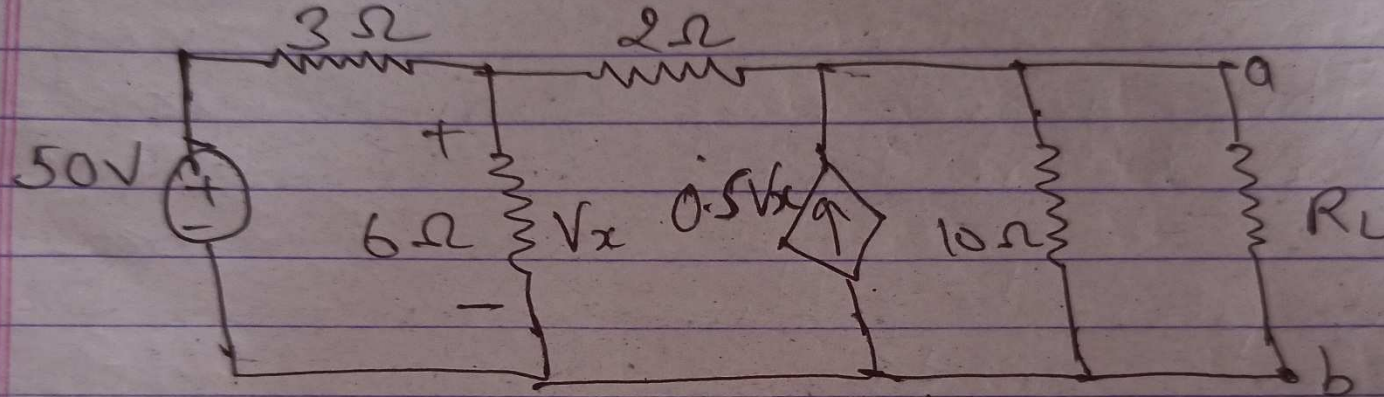


figure B(1)

Soln: As we know that for maximum power to transfer by the n/w, load resistor R_L is,

$$R_L = R_{th}$$

As the n/w consist of voltage dependent current source so we use the following

Circuit Theorem

formula, $R_{th} = \frac{V_{th}}{I_N}$ where V_{th} is ~~the~~

where V_{th} is Thevenin's voltage and I_N is Norton's current.

but let's see here, to find I_N we have to short terminal a & b by removing R_L .

Now, drawing n/w by short circuiting the terminal AB.

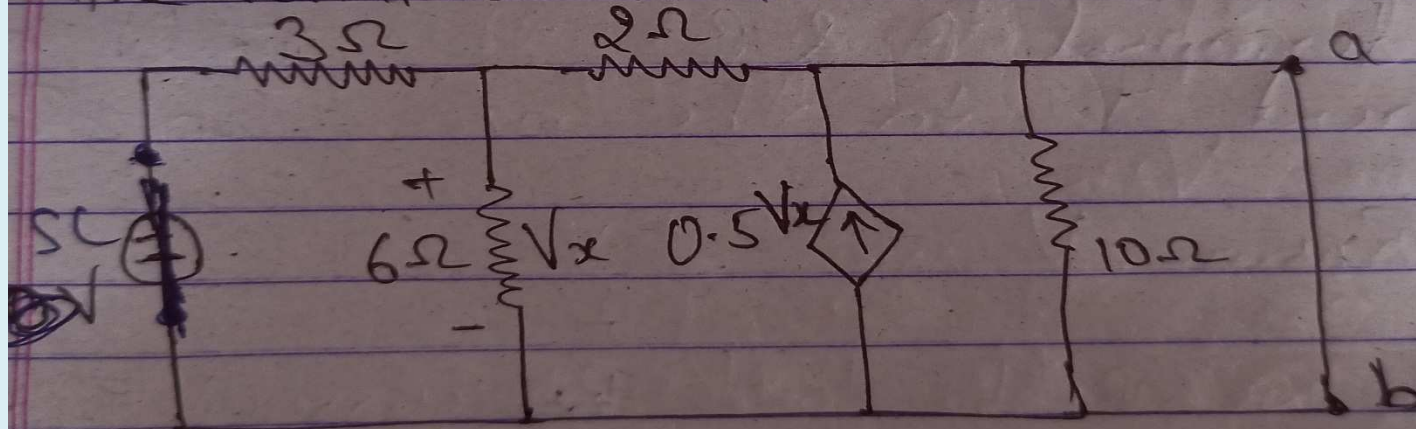


figure B(2)

Circuit Theorem

figure 0 (2)

Now as we have shorted terminal a & b so the resistor of 10Ω which is 11Ω to terminal a & b will become inactive so no current flow through this and also voltage dependent current source

$\diamond 0.5V_x$ will become inactive so we can not ~~use~~ short terminal a & b. So to find V_{th} we have ~~to~~ use another method here that is ~~source~~ we will use test source at terminal a & b and draw the circuit.

TE 8 PRO
CAMERA

Circuit Theorem

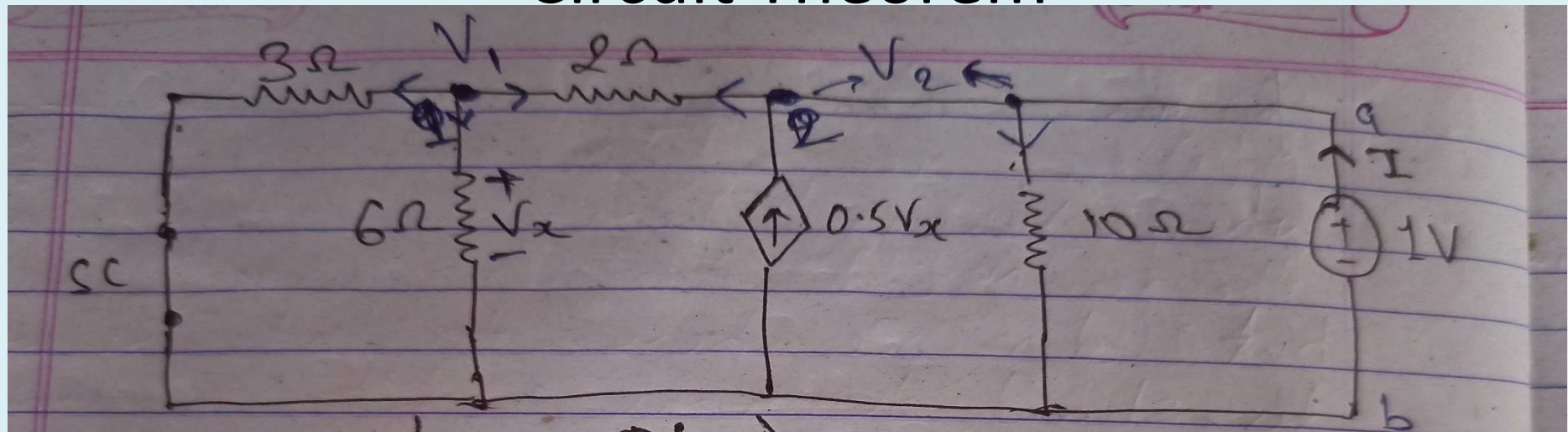


Figure B(3)

Here we have connected test source of '1V' at terminal A & B, this will deliver current I to the n/w, so R_{th} will be,

$$R_{th} = \frac{V}{I} = \frac{1V}{I}$$

Now we will find I by using KVL in the loop.

Circuit Theorem

$$R_{th} = \frac{V}{I} = \frac{1V}{1}$$

Now we will find ~~R_{th}~~ current I , for that we will use node analysis method here, for that we have 2 nodes here where we can apply KCL, let the voltage at terminals are V_1 & V_2 as shown in figure B(3).

Applying KCL at node 1, here all current are out going so, we can write equation as below,

$$\frac{V_1}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0 \quad \text{--- (1)}$$

and

V_1 is the voltage drop in 6Ω

Circuit Theorem

resistor which is V_x so,

$$V_1 = V_x$$

and voltage at node 2 i.e. V_2 is voltage between terminal a & b, so,

$$V_2 = 1 \text{ V.}$$

putting value of V_1 & V_2 in eqn. (1) we get.

$$\frac{V_x}{3} + \frac{V_x}{6} + \frac{V_x - 1}{2} = 0$$

$$\Rightarrow \frac{2V_x + V_x + 3V_x - 3}{6} = 0$$

$$\Rightarrow 6V_x - 3 = 0$$

$$V_x = \frac{3}{6} = 0.5 \text{ V.}$$

Circuit Theorem

$$V_x = \frac{3}{6} = 0.5 \text{ V.}$$

Now applying KCL at node 2, here two current is outgoing one is towards 2Ω & other is in 10Ω resistor, while there are 2 incoming currents I & $0.5V_x$ so

KCL at node 2 is,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{10} = 0.5V_x + I$$

$$\frac{1 - V_x}{2} + \frac{1}{10} = 0.5V_x + I$$

$$\frac{1 - 0.5}{2} + 0.1 = 0.5 \times 0.5 + I$$

$$\Rightarrow I = 0.25 + 0.1 - 0.25 = 0.1 \text{ A}$$

Circuit Theorem

$$\text{So, } R_{th} = \frac{1}{i} = \frac{10}{0.1} = 10 \Omega$$

So the value of $R_L = R_{th} = 10 \Omega$ for maximum power to transfer,

$$\text{Now, } P_{max} = \frac{V_{th}^2}{4 \times R_L}$$

To find V_{th} we again draw the ckt. of figure B(1) by removing R_L and find open terminal voltage at A & B,

$$V_{AB} = V_{th}$$



Circuit Theorem

$V_{AB} = V_{th}$

Figure B(4)

So V_{th} is voltage across 10Ω resistor.
 To find V_{th} we apply KVL in loop 1
 2 & 3 of n/w shown in figure B(4).

Let current I_1 , I_2 & I_3 flow in loops
 1, 2 & 3 respectively, so, applying KVL
 in loop 1,

$$3I_1 + 6I_1 - 6I_2 = 50 = 0$$

$$9I_1 - 6I_2 = 50 \quad \text{--- (ii)}$$

Circuit Theorem

Now applying KVL in loop 2,

$$2I_2 + 6I_2 - 6I_1 = 0$$

$$8I_2 - 6I_1 = 0$$

$$\text{or } 4I_2 = 3I_1$$

putting value of I_1 in eqn. (i) we have

$$12I_2 - 6I_2 = 50$$

$$6I_2 = 50 \quad 25$$

$$I_2 = \frac{25}{3}$$

$$I_1 = \frac{4 \times 25}{3 \times 3} = \frac{100}{9}$$

Circuit Theorem

$$I_1 = \frac{4 \times 25}{3 \times 3} = \frac{100}{9}$$

Now,

$$0.5 V_x = I_3 - I_2 \quad \text{--- (iii)}$$

and $V_x = 6(I_1 - I_2)$

$$V_x = 6 \left(\frac{100}{9} - \frac{25}{3} \right) \quad \text{putting value of } I_1 \text{ \& } I_2$$

$$V_x = \frac{6 \times 25}{3} = \frac{50}{3}$$

Now, putting value of V_x in eqn. (iii) we get

$$0.5 \times \frac{50}{3} = I_3 - \frac{25}{3}$$

$$\Rightarrow I_3 = \frac{50}{6} + \frac{25}{3} = \frac{100}{6} + \frac{50}{3}$$

Circuit Theorem

$$V_{th} = \cancel{50 \times 10} \quad 10 \text{ } \Omega_3$$
$$= 10 \times \frac{50}{3} = \frac{500}{3} = 166.67 \text{ V}$$

$$\text{Now } P_{max} = \frac{\left(\frac{500}{3}\right)^2}{4 \times 10}$$

$$= \frac{\cancel{500} \times \cancel{500} \quad 125}{9 \times \cancel{4} \times \cancel{10}}$$

$$= \frac{6250}{9} = 694.44 \text{ Watt.}$$

$$P_{max} = 694.44 \text{ Watt.}$$